

becomes very large and amplify it to full voltage values. Sense amps are used primarily to speed up the read process or to avoid the energy overhead of fully discharging the large capacitance of the bitlines.

When the bitcell is holding data, its wordline is low, so M_2 and M_5 are off. In order to hold its data properly, the back-to-back inverters must maintain bi-stable operating points. The best measure of the ability of these inverters to maintain their state is the bitcell's Static Noise Margin (SNM) [135]. The SNM is the maximum amount of voltage noise that can be introduced at the outputs of the two inverters such that the cell retains its data. SNM quantifies the amount of voltage noise required at the internal nodes of a bitcell to flip the cell's contents.

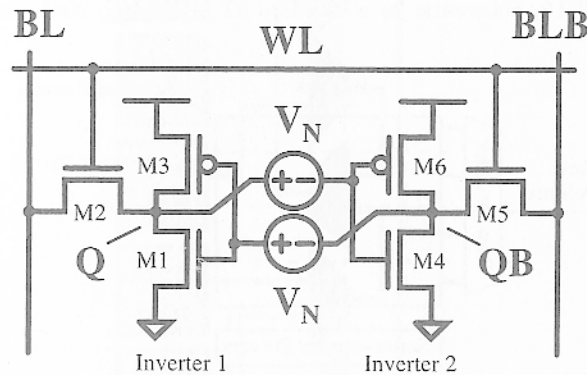


Fig. 7.18. Schematic for 6T bitcell showing voltage noise sources for finding SNM [135]. (© 2005 IEEE)

Figure 7.18 shows a conceptual setup for modeling SNM [135]. Noise sources having value V_N are introduced at each of the internal nodes in the bitcell. As V_N increases, the stability of the cell changes. Figure 7.19 shows the most common way of representing the SNM graphically for a bitcell holding data. The figure plots the VTC of Inverter 2 from Figure 7.18 and the inverse VTC from Inverter 1. The resulting two-lobed curve is called a "butterfly curve" and is used to determine the SNM. The SNM is defined as the length of the side of the largest square that can be embedded inside the lobes of the butterfly curve [135]. To understand why this definition holds, consider the case when the value of V_N increases from 0. On the plot, this causes the VTC^{-1} for Inverter 1 in the figure to move downward and the VTC for Inverter 2 to move to the right. As V_N increases, the metastable point moves closer to one of the stable points in the plot (the lower-right point in this example). Once both curves move by the SNM value, the metastable point becomes coincident with one stable point, and the curves meet at only two points. Any further noise flips the cell.

 


Fig. 7.19. The length of the side of the largest embedded square in the butterfly curve is the SNM. When both curves move by more than this amount (e.g. $V_N=SNM$), then the bitcell is mono-stable, losing its data.

 


Fig. 7.20. Schematic of the 6T bitcell at the onset of a read access. WL has just gone high, and both BLs are precharged to V_{DD} . The voltage dividing effect across M_4 and M_5 pulls up node Q_B , which should be 0V, and degrades the SNM.

Although the SNM is certainly important during hold, cell stability during active operation represents a more significant limitation to SRAM operation. Specifically, at the onset of a read access, the wordline is '1' and the bitlines are still precharged to '1' as Figure 7.20 illustrates. The internal node of the bitcell that represents a zero gets pulled upward through the access transistor due to the voltage dividing effect across the access transistor (M_2, M_5) and drive transistor (M_1, M_4). This increase in voltage severely degrades the SNM during the read operation (read SNM). Figure 7.21 shows example butterfly