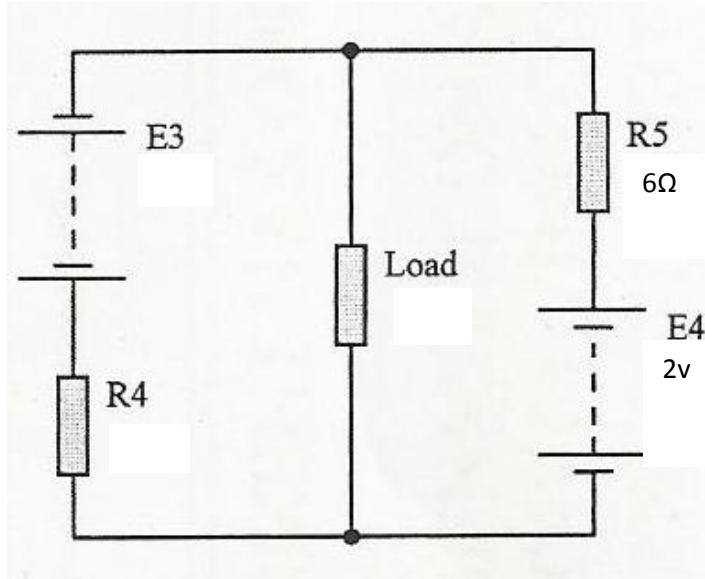


Circuit Two Kirchoffs Law



Loop A B C D

$$3v = 3\Omega I_1 + 1\Omega (I_1 - I_2)$$

$$3v = 3\Omega I_1 + 1I_1 - I_2$$

$$3v = 4\Omega I_1 - 1I_2 \quad \text{----- } (1)$$

Loop B E F C

$$2v = 6\Omega I_2 + 1\Omega I_1 (I_2 - I_1)$$

$$2v = 1\Omega I_1 + 7\Omega I_2 \quad \text{----- } (2)$$

$$3v = 4\Omega I_1 - 1\Omega I_2 \quad \text{----- } (1) \times 1$$

$$2v = -4\Omega I_1 + 7\Omega I_2 \quad \text{----- } (2) \times 4$$

$$3v = 4\Omega I_1 - 1\Omega I_2$$

$$8v = -16\Omega I_1 + 28\Omega I_2$$

$$11v = 27\Omega I_2$$

$$I_2 = \frac{11v}{27\Omega} = 0.407a$$

Sub I_2 into equation (1)

$$3v = 4\Omega I_1 - 1\Omega I_2 (0.407a)$$

$$3v = 4\Omega I_1 + 0.407a$$

$$3v + 0.407a = 4\Omega I_1$$

$$I_1 = 3v + \left(\frac{0.407a}{4\Omega}\right) = 0.851a$$

$$I_1 - I_2 = 0.851a - 0.407a = 0.444a$$