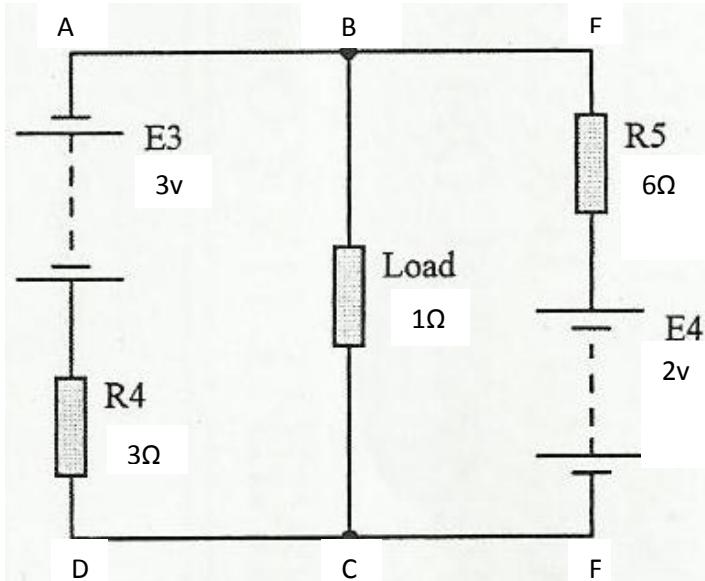


Circuit Two Kirchoff's Law



Loop A B C D

$$3V = 3\Omega I_1 + 1\Omega (I_1 - I_2)$$

$$3V = 3\Omega I_1 + 1I_1 - I_2$$

$$3V = 4\Omega I_1 - 1I_2 \quad \text{----- } \textcircled{1}$$

Loop B E F C

$$2V = 6\Omega I_2 + 1\Omega (I_2 - I_1)$$

$$2V = -1\Omega I_1 + 7\Omega I_2 \quad \text{----- } \textcircled{2}$$

$$3V = -4\Omega I_1 - 1\Omega I_2 \quad \text{----- } \textcircled{1} \times 1$$

$$2V = -1\Omega I_1 + 7\Omega I_2 \quad \text{----- } \textcircled{2} \times 4$$

$$3V = -4\Omega I_1 - 1\Omega I_2$$

$$8V = -1\Omega I_1 + 28\Omega I_2$$

$$11V = 27\Omega I_2$$

$$I_2 = \frac{11V}{27\Omega} = 0.407a$$

Sub I_2 into equation $\textcircled{1}$

$$3V = 4\Omega I_1 - 1\Omega I_2 (0.407a)$$

$$3V + 0.407V = 4\Omega I_1$$

$$I_1 = \frac{3V}{4\Omega} + \frac{0.407V}{4\Omega} = 0.851a$$

$$I_1 - I_2 = 0.851a - 0.407a = 0.444a$$