

---


# Current Reference & Voltage Reference

---



**Sougata Kumar Kar**  
Dept. of Electrical Engg.,  
Indian Institute of Technology Kharagpur

# Current and Voltage Reference

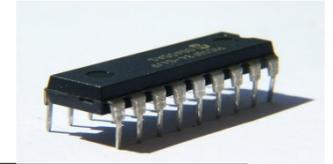


## ❑ Reference Vs Source

- Reference is more *precise* and *stable* than source.
- Source must be capable of driving Load.
- Reference is more complex

## ❑ Properties

- Independent of PVT (*Process-Voltage-Temperature*) variation
- Independent of output Voltage or Current
- Independent of Noise and other Interference
- Easy to design / tune

# Power Supply Dependency

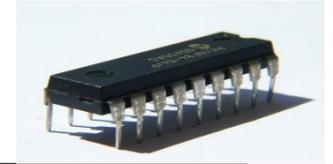

## □ How to characterize ?


**Sensitivity :** 
$$S_{V_{DD}}^{I_{REF}} = \frac{\partial I_{REF}/I_{REF}}{\partial V_{DD}/V_{DD}} = \frac{V_{DD}}{I_{REF}} \left( \frac{\partial I_{REF}}{\partial V_{DD}} \right)$$

## Power supply Dependence :

$$\frac{\partial I_{REF}}{I_{REF}} = \left( S_{V_{DD}}^{I_{REF}} \right) \frac{\partial V_{DD}}{V_{DD}}$$



- So the fractional change in the reference current is equal to the sensitivity times fractional change in the supply voltage
- *Ideally this sensitivity to be zero for Power Supply Independence*

# Need of Current Reference

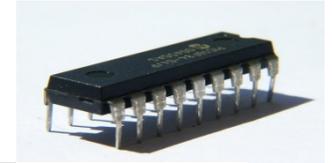

- ❑ Required in different places in IC, e.g.- Op-amp, Comparator, Oscillator etc.
- ❑ Generate one current reference and used in multiple places by current mirror principle.
- ❑ Saves area and power.



# Some Crude Current References

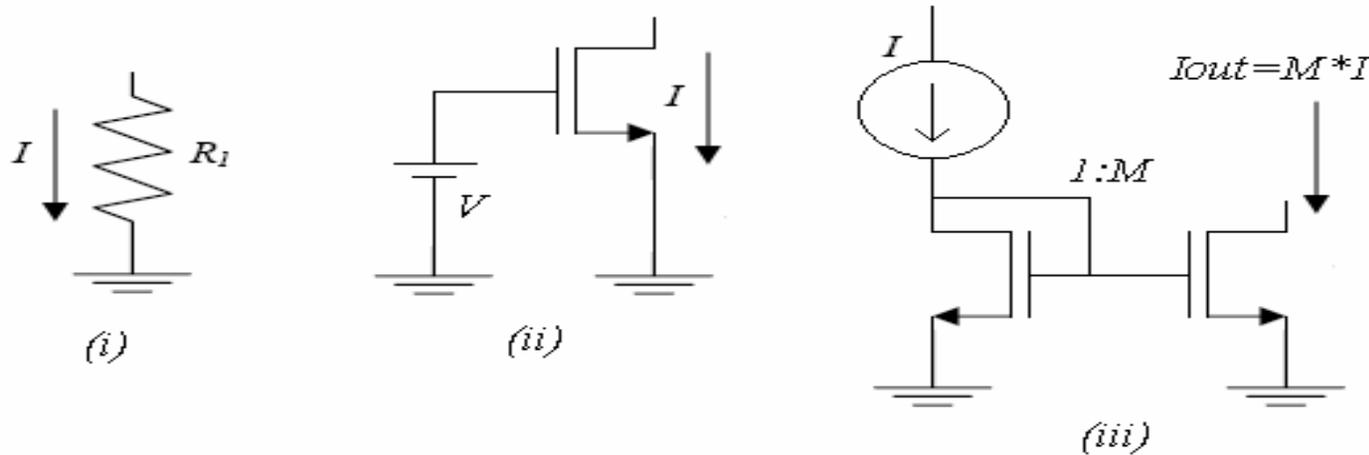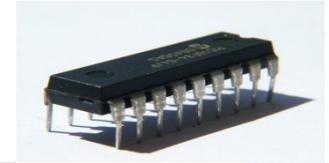

## ❑ Problems-

- (i) Not independent of VDD, Resistor should be accurate.
- (ii) Need reference voltage  $V$ , difficult to control current – strong function of  $V_{gs}$ , more sensitive to Process variation.
- (iii) Need Stable  $I$ . Easy to adjust current, less sensitive to Process variation



# Resistance Biasing

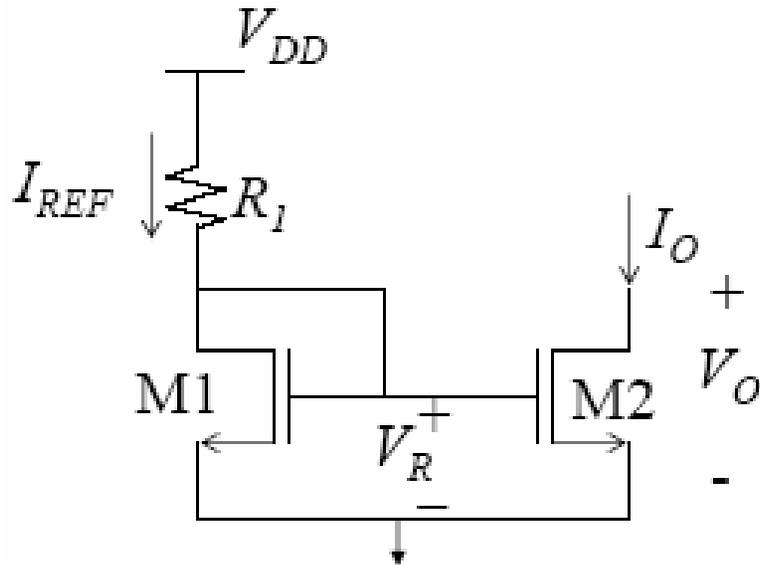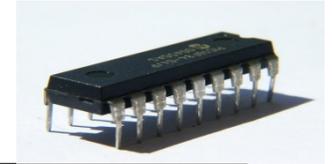

$$I_o = \frac{V_{DD}}{R_1 + \frac{1}{g_{m1}}} \frac{W_2}{W_1}$$
$$\Delta I_o = \frac{\Delta V_{DD}}{R_1 + \frac{1}{g_{m1}}} \frac{W_2}{W_1}$$
$$S_{V_{DD}}^{I_{REF}} = 1$$

- ❑  $I_o$  – much sensitive to  $V_{DD}$
- ❑ How to make it less sensitive to  $V_{DD}$  ?

# Threshold Referenced Current Reference

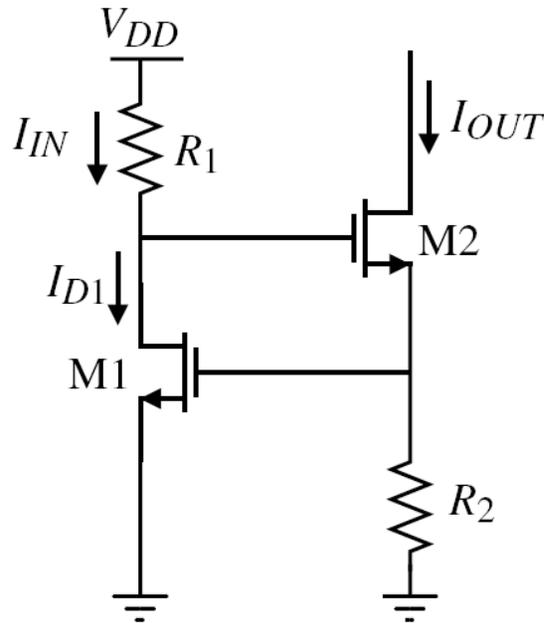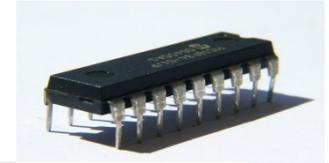

$$I_{OUT} = \frac{V_{GS1}}{R_2} = \frac{V_T + \sqrt{\frac{2I_{IN}}{K'(W_1/L_1)}}}{R_2}$$

$$\approx \frac{V_T}{R_2} \text{ if } V_T > V_{ON1}$$

The sensitivity of  $I_{OUT}$  with respect to  $V_{DD}$  is




$$S_{V_{DD}}^{I_{OUT}} = \left( \frac{V_{ON1}}{I_{OUT}R_2} \right) S_{V_{DD}}^{I_{IN}} = \left( \frac{V_{ON1}}{2V_{GS1}} \right) S_{V_{DD}}^{I_{IN}}$$

For example, if  $V_T = 1\text{V}$ ,  $V_{ON1} = 0.1\text{V}$  and  $S_{V_{DD}}^{I_{IN}} \approx 1$ , then

$$S_{V_{DD}}^{I_{OUT}} = \left( \frac{0.1}{2 \cdot 1.1} \right) = 0.045$$

- ❑ Supply dependency much less
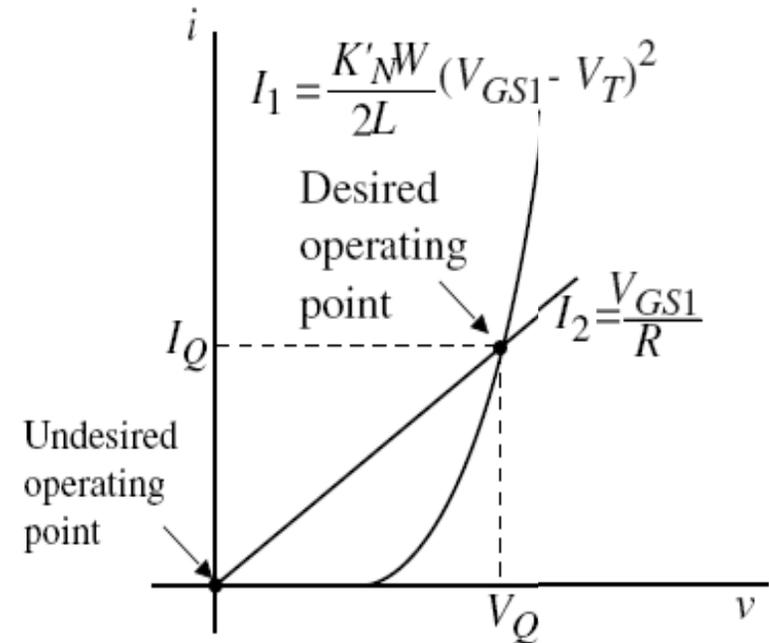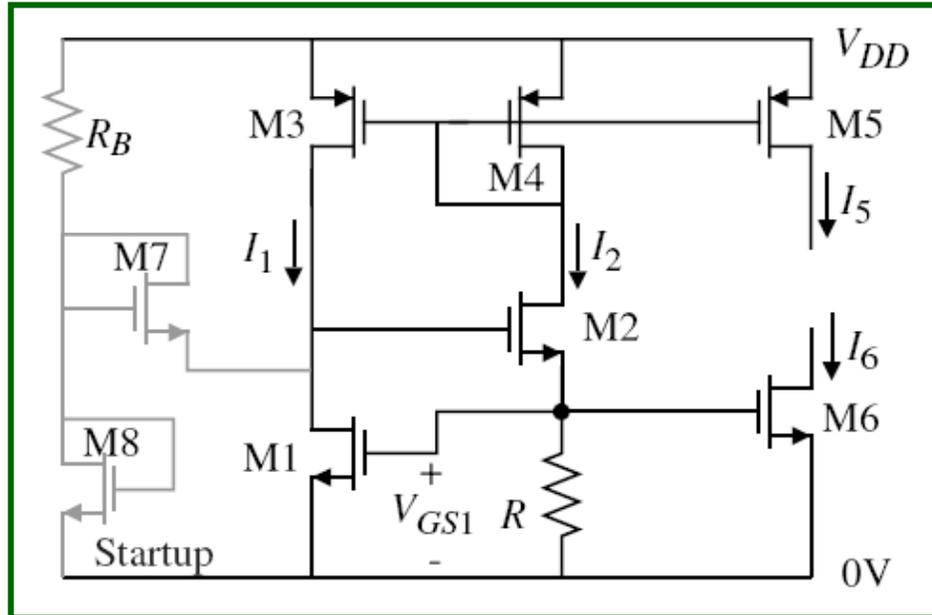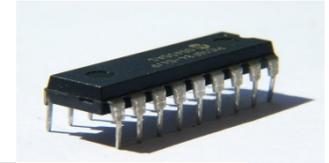
# Self Biasing Threshold Current Reference I





If  $M3 = M4$ , then  $I_1 \approx I_2$ . However, the M1-R loop gives  $V_{GS1} = V_{T1} + \sqrt{\frac{2I_1}{K_N'(W_1/L_1)}}$

Solving these two equations gives  $I_2 = \frac{V_{GS1}}{R} = \frac{V_{T1}}{R} + \left(\frac{1}{R}\right) \sqrt{\frac{2I_1}{K_N'(W_1/L_1)}}$

The output current,  $I_{out} = I_1 = I_2$  can be solved as  $I_{out} = \frac{V_{T1}}{R} + \frac{1}{\beta_1 R^2} + \frac{1}{R} \sqrt{\frac{2V_{T1}}{\beta_1 R} + \frac{1}{(\beta_1 R)^2}}$

**❑ Two current level supported, need a start-up circuit**



# Self Biasing Current Reference II

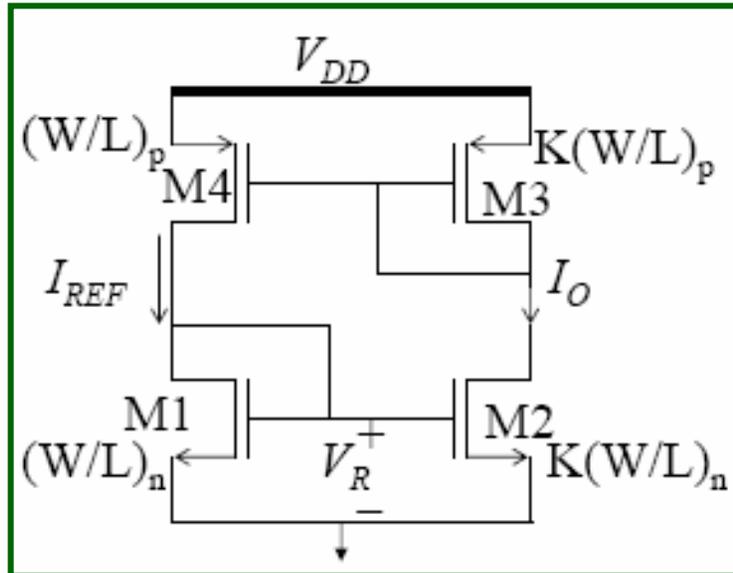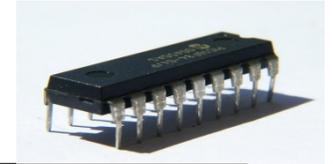

- ❑  $I_{REF}$  is bootstrapped to  $I_O$
- ❑  $I_O = K I_{REF}$
- ❑ Supply dependent

- ❑ If all the transistors are in saturation the circuit can support any current !!!
- ❑ Then how to fix the current ?

# Self Biasing Current Reference II

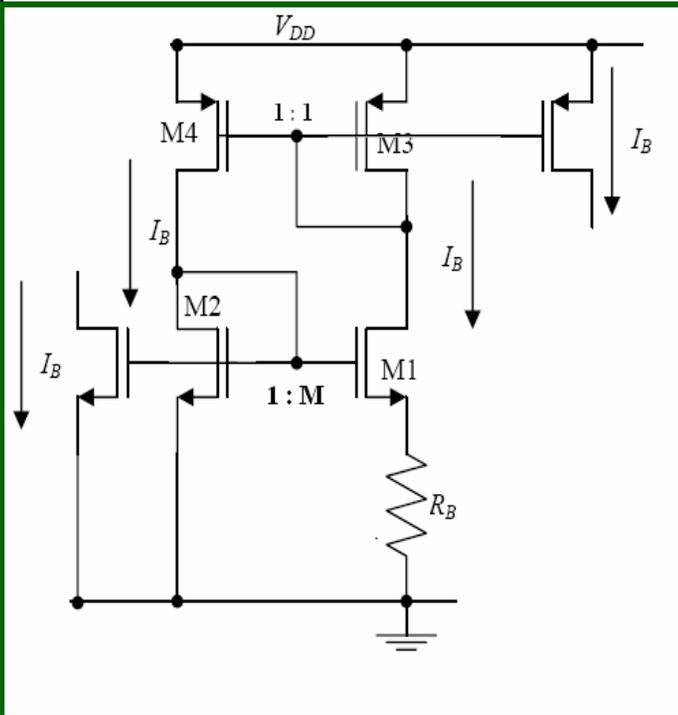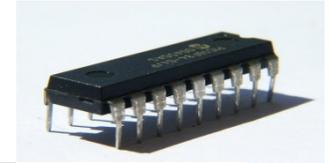

From the circuit,

$$\Rightarrow I_B R_B + V_{GS1} = V_{GS2}$$

$$\Rightarrow I_B R_B + V_{THN1} + \sqrt{\frac{2I_B}{\mu_N C_{ox} \left(\frac{W}{L}\right)_1}} = V_{THN2} + \sqrt{\frac{2I_B}{\mu_N C_{ox} \left(\frac{W}{L}\right)_2}}$$

By neglecting the body effect,  $V_{TH1} = V_{TH2}$  and the above equation is rewritten as




$$\Rightarrow I_B R_B = \sqrt{\frac{2I_B}{\mu_N C_{ox} \left(\frac{W}{L}\right)_2}} - \sqrt{\frac{2I_B}{\mu_N C_{ox} \left(\frac{W}{L}\right)_1}} \quad \left(\text{Assuming } I_B \neq 0\right)$$

$$\Rightarrow I_B = \frac{2}{R_B^2 \cdot \mu_N C_{ox} \left(\frac{W}{L}\right)_2} \cdot \left(1 - \sqrt{\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}}\right)^2 = \frac{2}{R_B^2 \cdot \mu_N C_{ox} \left(\frac{W}{L}\right)_2} \cdot \left(1 - \sqrt{\frac{1}{M}}\right)^2$$

which is independent of  $V_{DD}$ .



- Current uniquely defined
- Supply Independent
- Temperature Dependent

# Self Biasing Current Reference II

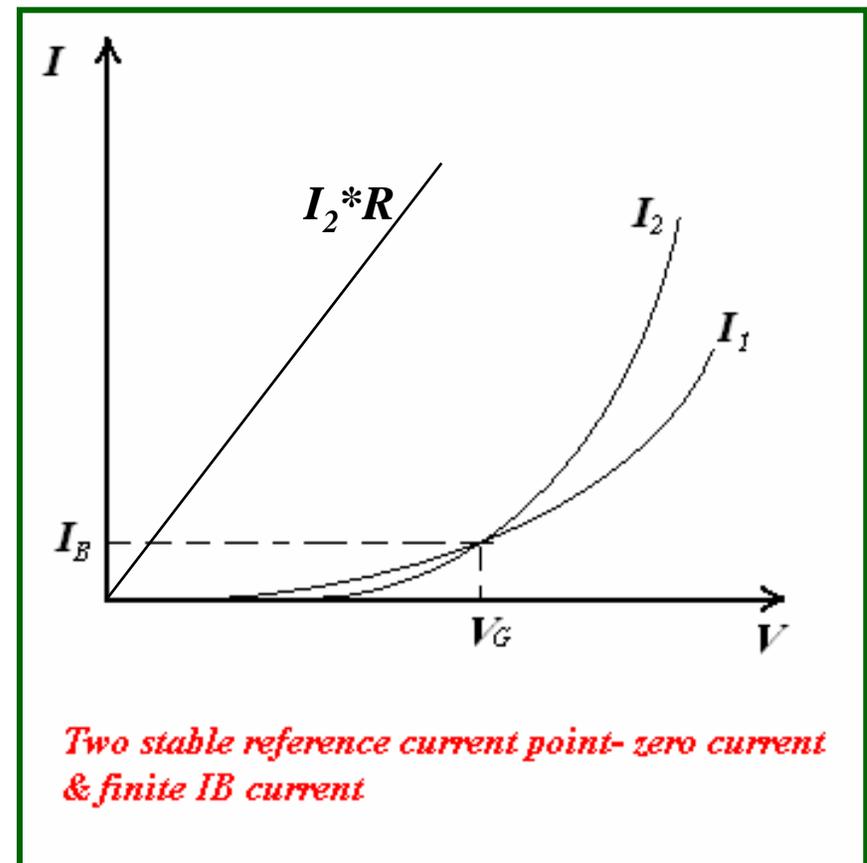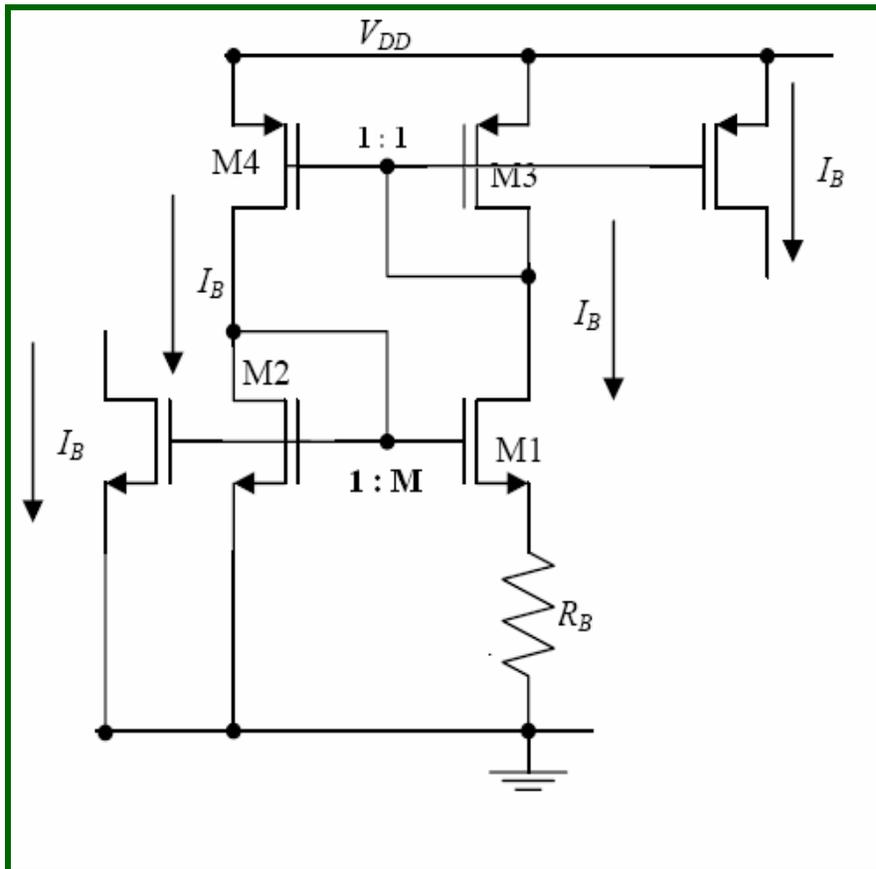
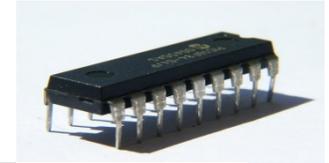


- ❑ Two meeting points – two stable reference current – zero and finite  $I_B$   
How to fix ?
- ❑ Slope more – more stable
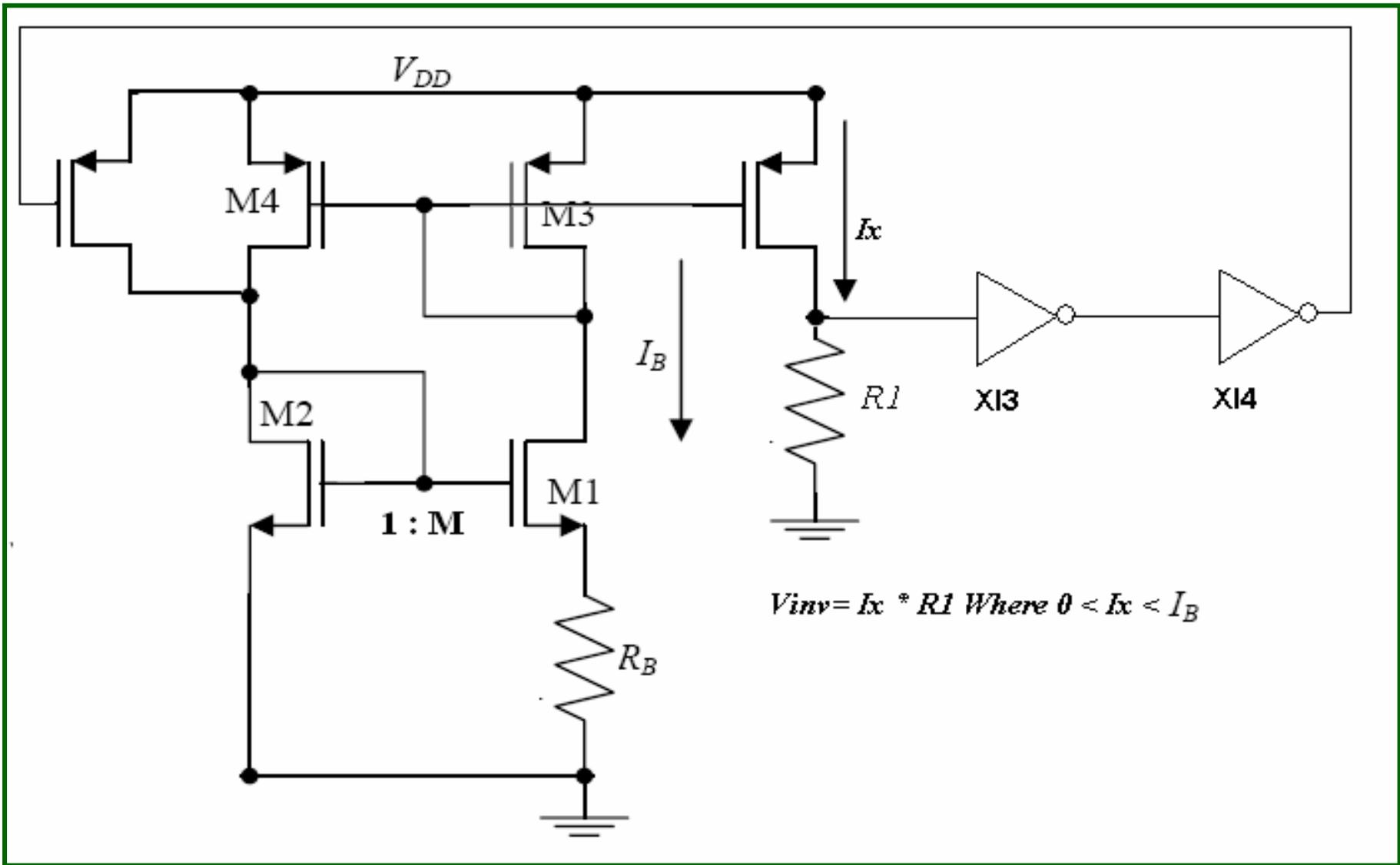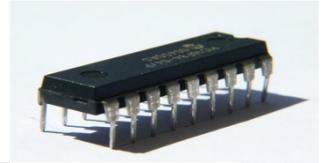
# Self Biasing Current Reference II - Startup





# Stability and Feedback

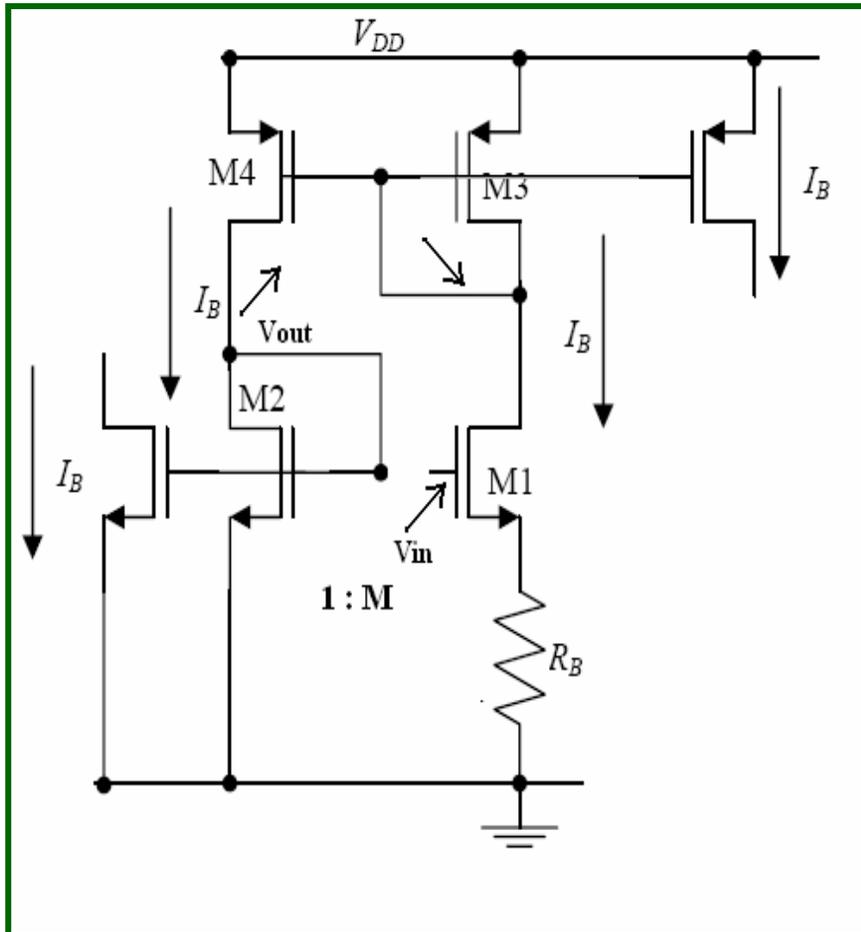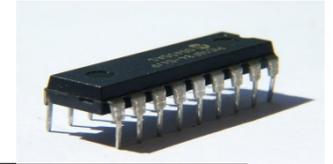

- ❑ Break the loop and find loop gain and polarity
- ❑ What type of feedback it is ?

# Loop Gain of the positive feedback

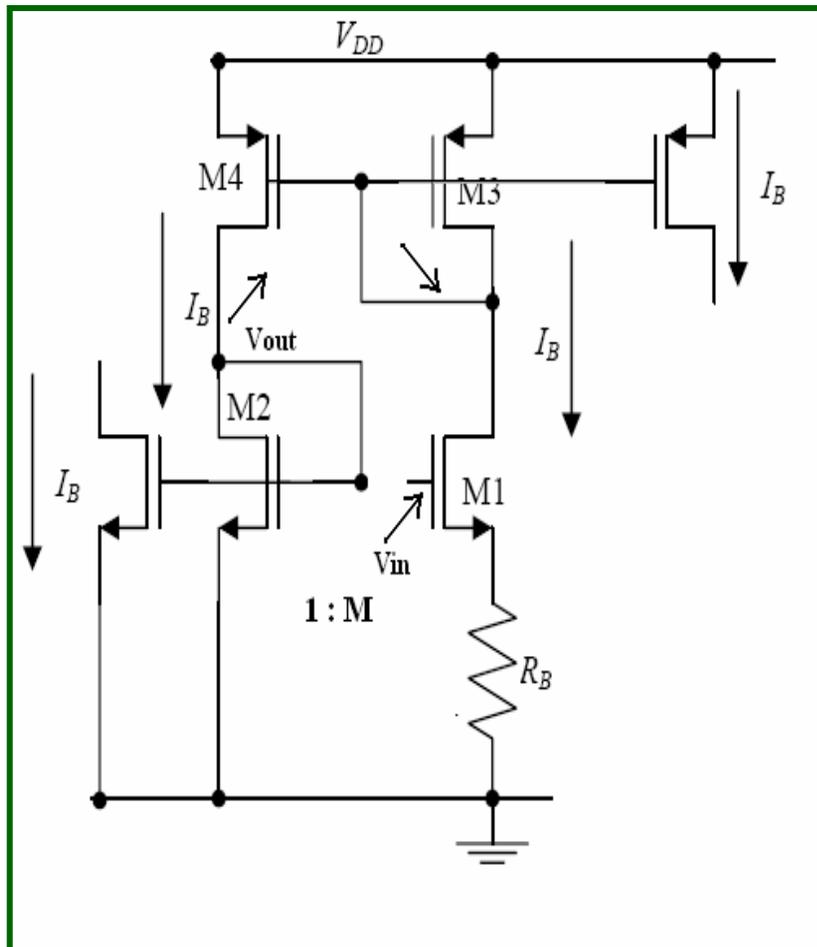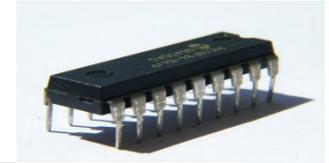

$$A_v = \frac{g_{m1}}{1 + g_{m1} * R_B} * \frac{1}{g_{m3}} * g_{m4} * \frac{1}{g_{m2}}$$

$$g_m = \sqrt{2I_D * \mu * C_{ox} \left( \frac{W}{L} \right)}$$





$$g_{m3} = g_{m4} \quad g_{m1} = g_{m2} \sqrt{M}$$

$$A_v = \frac{g_{m2} \sqrt{M}}{1 + g_{m2} * R_B \sqrt{M}} * \frac{1}{g_{m2}} = \frac{\sqrt{M}}{1 + g_{m2} * R_B \sqrt{M}}$$

$$= \frac{\sqrt{M}}{2\sqrt{M} - 1} = \frac{1}{2 - \frac{1}{\sqrt{M}}}$$

$$M > 1 \quad A_v < 1$$

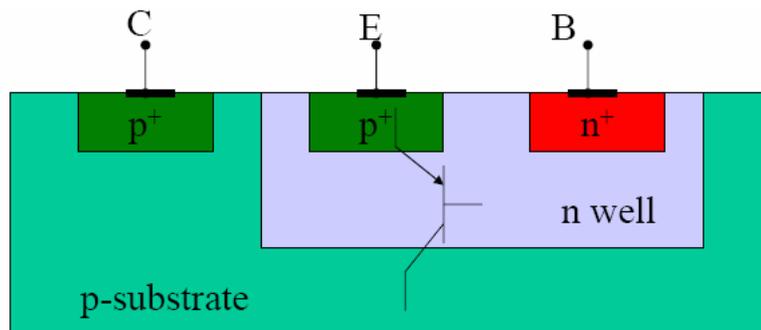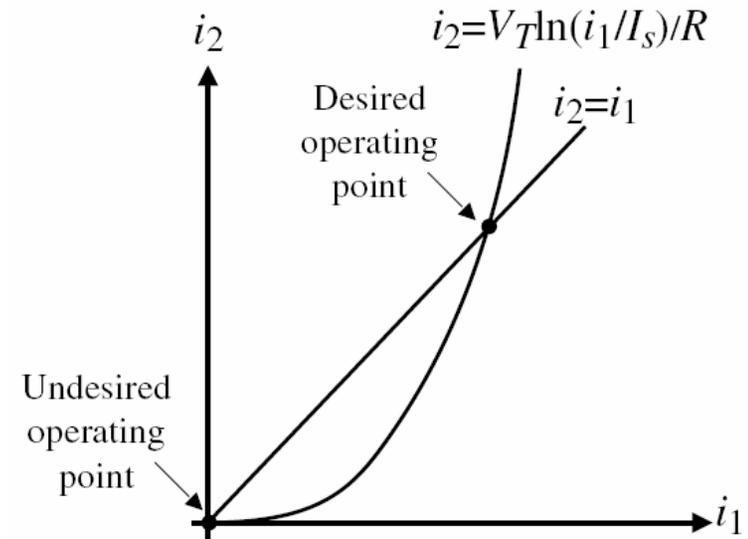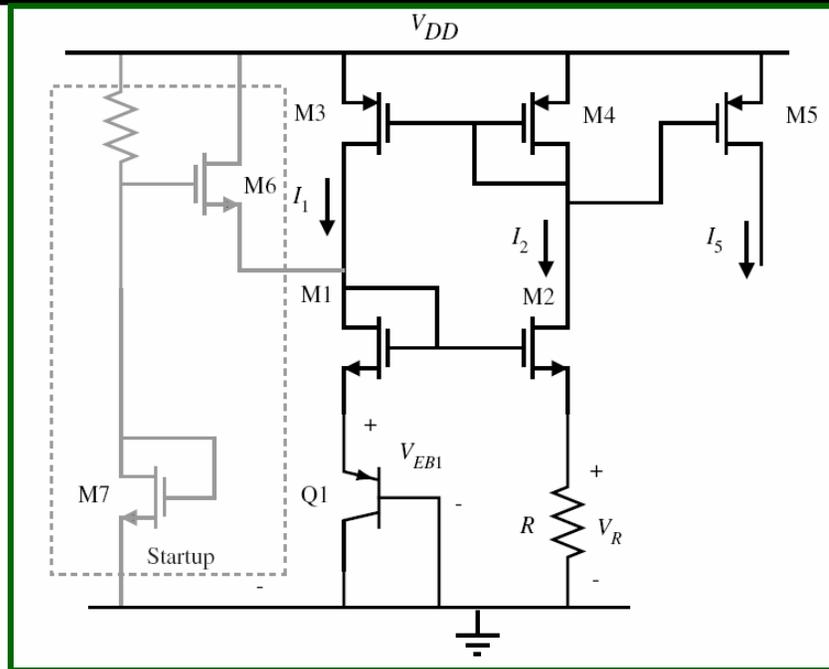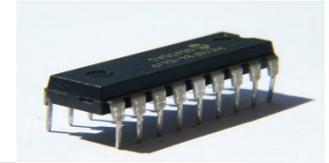
# $V_{BE}$ Referenced Current Reference III



- ❑ Parasitic bipolar devices in CMOS process
- ❑ *pnp* for p-substrate, *npn* for n-substrate

The p-substrate, connected to most negative potential (Gnd) acts as a collector whereas n-well and  $p^+$  region act as base & emitter
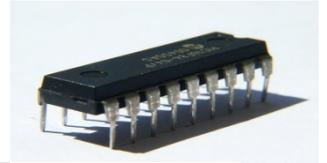
# Voltage Reference: Applications & Properties





## □ Applications:

- Error amplifier, comparator, A/D and D/A converters.


## □ Properties :

- Independent of PVT.
- Low area.
- Easy to design / tune.


# Some Crude Voltage References

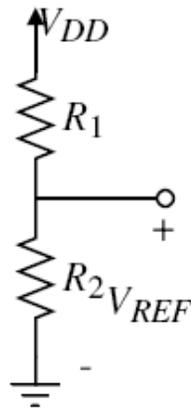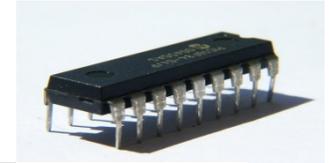


Resistor voltage divider.

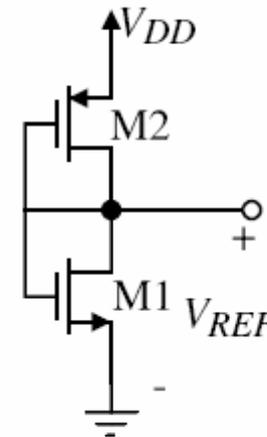


Active device voltage divider.

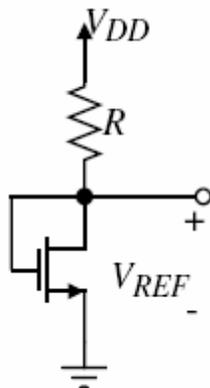

MOSFET – Resistance Voltage reference

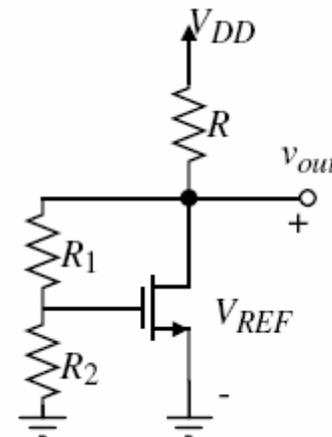

# Temperature Independent Reference

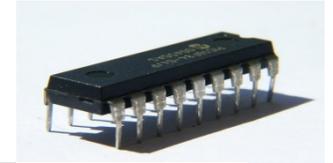

- ❑ **Concept : Generate the reference by combining two voltages of which one has negative temperature coefficient and the other one has a positive temperature coefficient**


$$V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$$

If  $\frac{\partial V_1}{\partial T} = -ve$  and  $\frac{\partial V_2}{\partial T} = +ve$


So that  $\alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0$

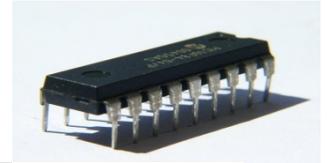**Candidate :**


- ❑  $V_{BE}$  of BJT / Diode or  $V_{TH}$  of MOSFET for - ve temp. coefficient
- ❑  $\Delta V_{BE}$  between two different  $V_{BE}$ s or resistors for + ve temp. coefficient



# Band-gap Reference

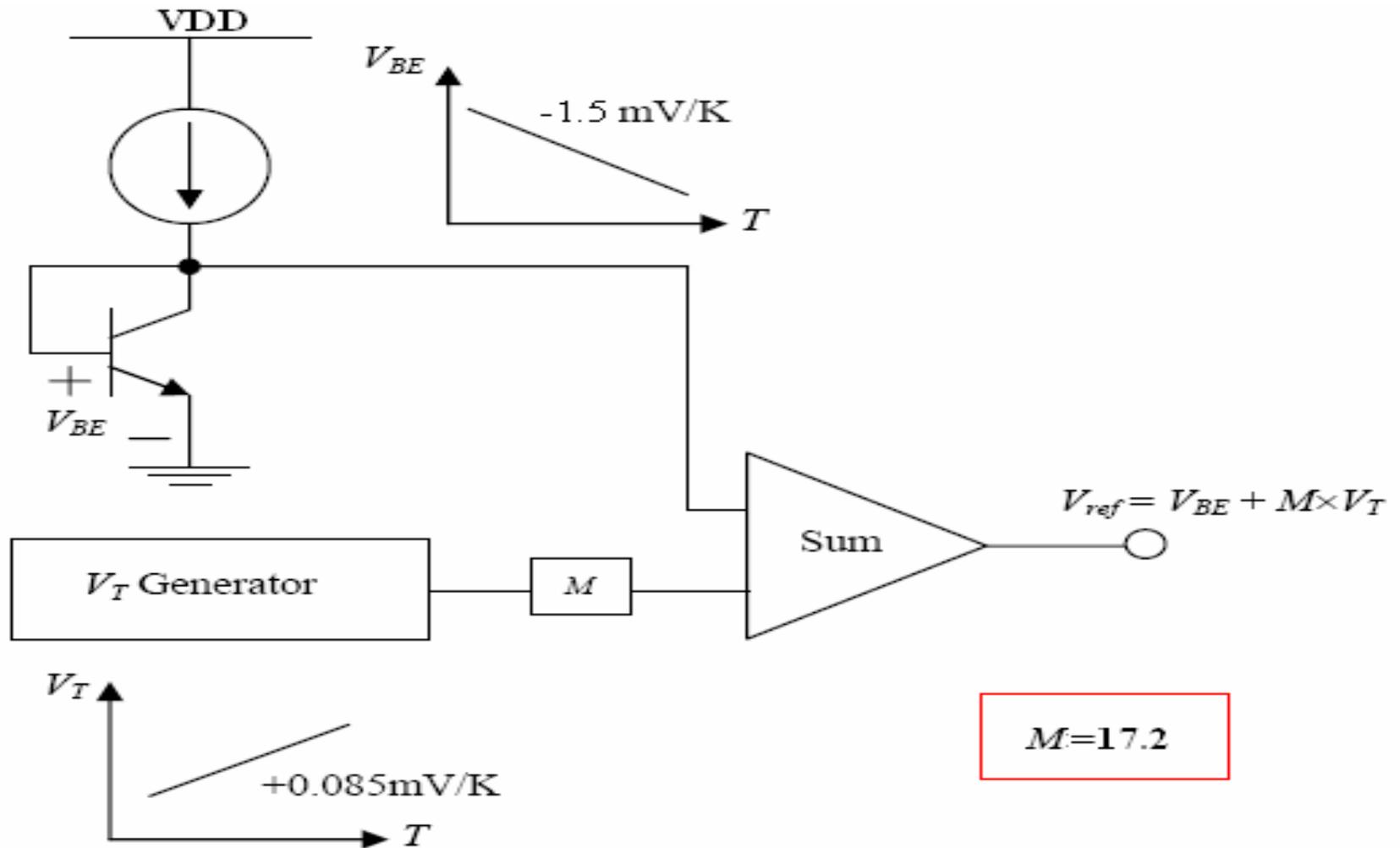

❑ Why it is called Band gap reference ?

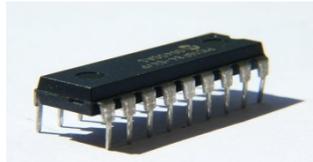

# Negative TC Voltage


- $I_C = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$  and  $I_s \propto T^{(4+M)} \exp\left(\frac{-E_g}{kT}\right)$

- $V_{BE} = V_T \ln\left(\frac{I_C}{I_s}\right)$


- $\left. \frac{\partial V_{BE}}{\partial T} \right|_{\text{constant } I_C} = \frac{V_{BE} - (4+M)V_T - V_G}{T}, V_G = \frac{E_g}{q}$

with  $V_{BE} \approx 800mV$ ,  $\frac{\partial V_{BE}}{\partial T} \approx -1.5mV / ^\circ K @ T = 300K$

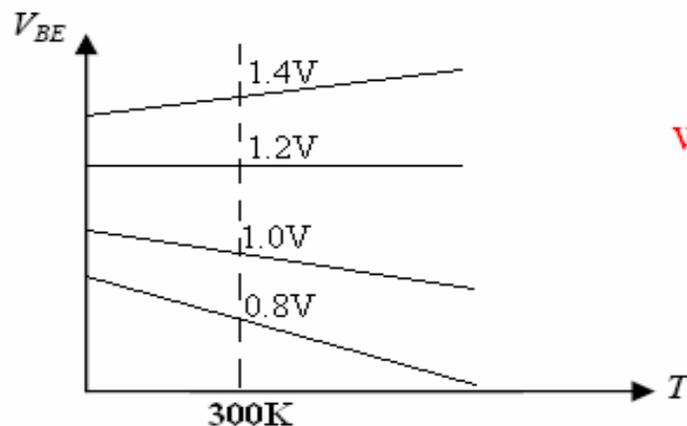- $\frac{\partial V_{BE}}{\partial T}$  is dependent on  $V_{BE}$ . For different  $V_{BE}$  Temperature dependency will be-




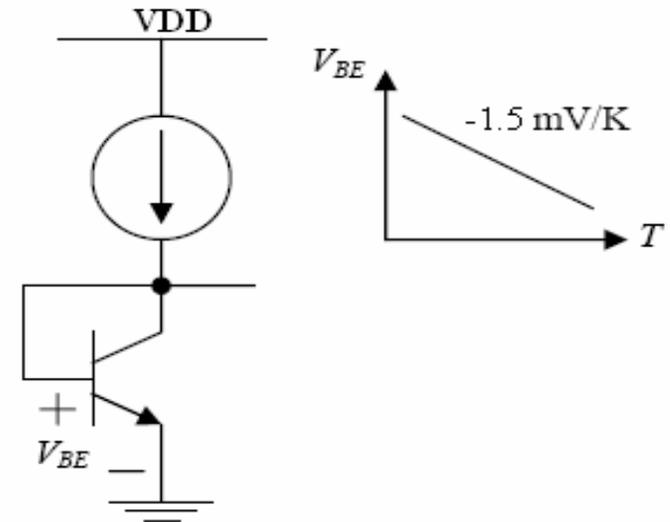When  $V_{BE}$  is 1.2V then,  $TC=0$ . But, What is the problem?






# Positive TC Voltage

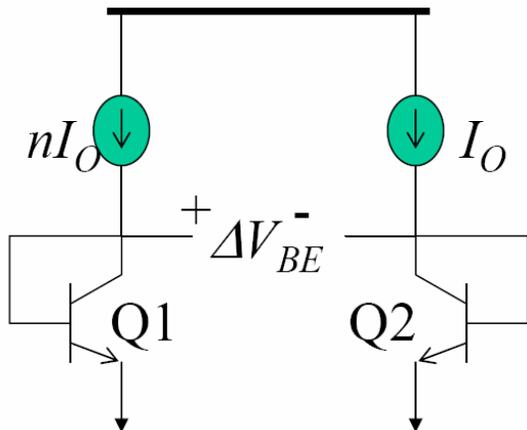


$$\begin{aligned} \Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nI_O}{I_S} - V_T \ln \frac{I_O}{I_S} \\ &= V_T \ln n = \frac{kT}{q} \ln n \\ \frac{\partial \Delta V_{BE}}{\partial T} &= \frac{k}{q} \ln n \\ &= +0.087 \ln n \text{ mV/}^\circ\text{K} \end{aligned}$$

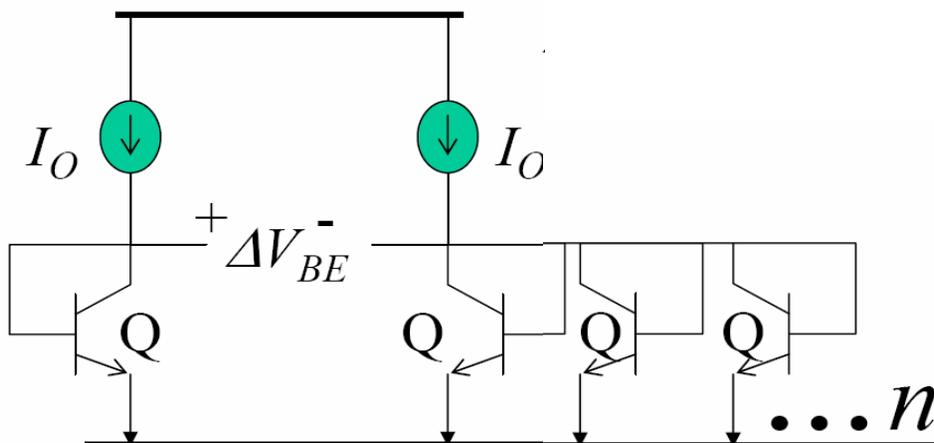□ So  $\Delta V_{BE}$  is a PTAT (Proportional To Absolute Temperature) source



□ Practical implementation by realizing 1 unit transistor for Q1 and n unit transistors in parallel for Q2 and forcing equal current  $I_0$

# Band gap Ref-Implementation

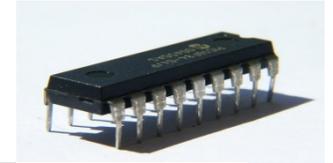

$$V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$$

Choose  $V_1 = V_{BE}$  and  $V_2 = \Delta V_{BE}$ ,  $\alpha_1 = 1$  and  $\alpha_2 = 1$

$$V_{REF} = V_{BE} + V_T \ln(n)$$

Since  $dV_{BE}/dT = -1.5\text{mV}/^\circ\text{K}$ , Choose  $n$  such that

$$0.087 \ln(n) = 1.5 \Rightarrow \ln(n) = 17.2 \Rightarrow n = 30749347$$


$$V_{REF} = V_{BE} + 17.2V_T$$

For  $V_{BE} = 0.75\text{V}$  and  $T = 300^\circ\text{K}$ ,  $V_{REF} = 1.19\text{V}$


Note:  $V_{REF}$  can also be expressed as

$$V_{REF} \approx \frac{E_g}{q} + (4 + m)V_T$$

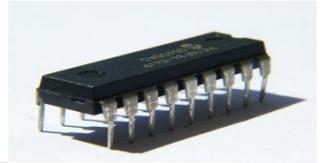□ If  $T \rightarrow 0$ ,  $V_{REF} \rightarrow E_g/q$ , Therefore BGR



# Band gap Ref-Implementation I

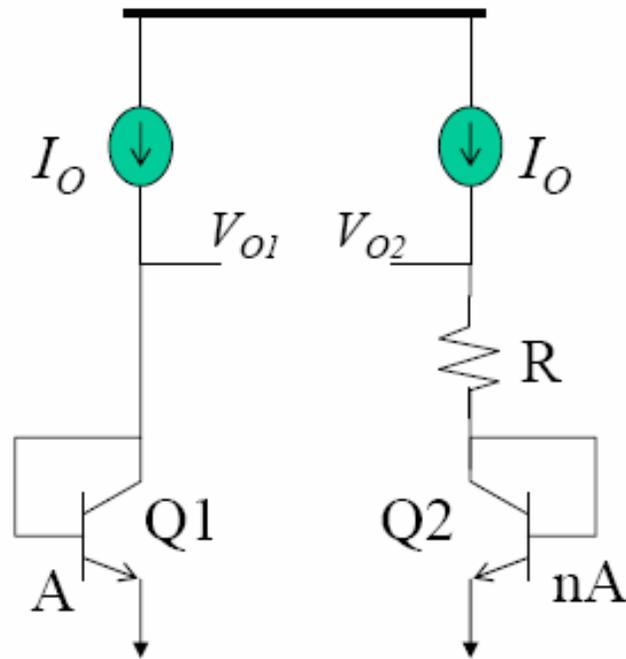

*Q1 is unit transistor with area A  
Q2 has n unit transistors in parallel  
The current in one unit of Q2 is  $I_O/n$*

Suppose that  $V_{O1}$  and  $V_{O2}$  are made equal by some external means

Then,

$$V_{BE1} = RI_O + V_{BE2}$$

$$RI_O = V_{BE1} - V_{BE2} = V_T \ln n$$



$$V_{O2} = V_{BE2} + V_T \ln n$$

which is the required reference

**Need a mechanism for  $V_{O1} = V_{O2}$**

**$\ln n = 17.2$  results in impractical n and hence should some how scaled properly**

# Band gap Ref-Implementation I

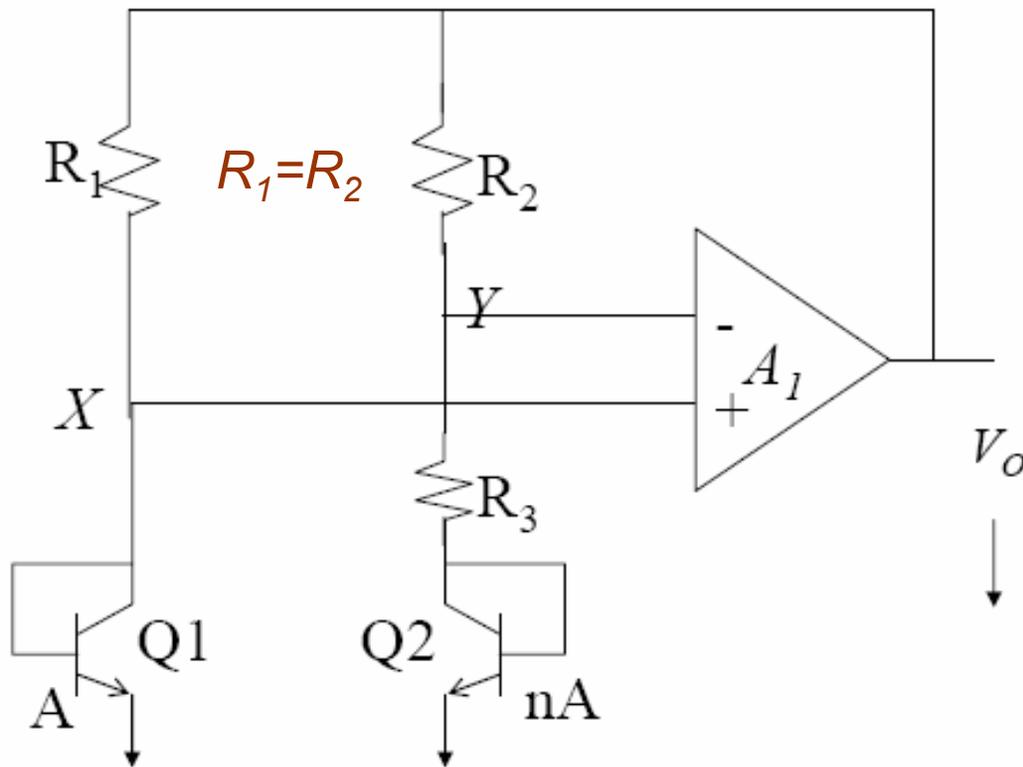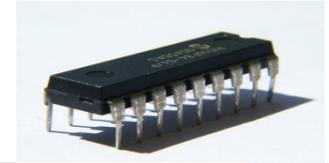

The OPAMP forces  $V_X = V_Y$

$$V_{BE1} - V_{BE2} = V_T \ln n$$

This results in a current through the right branch


$$I_{R3} = V_T \ln n / R_3$$

$$V_O = V_{BE2} + \frac{V_T \ln n}{R_3} (R_2 + R_3)$$


$$V_O = V_{REF} = V_{BE2} + V_T \ln n \left( 1 + \frac{R_2}{R_3} \right)$$

If  $R_2/R_3 = 10$ , then  $n=5$

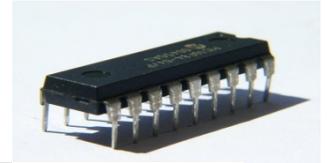□ The Op-amp output  $V_O$  is the desired reference voltage



# Different feed backs

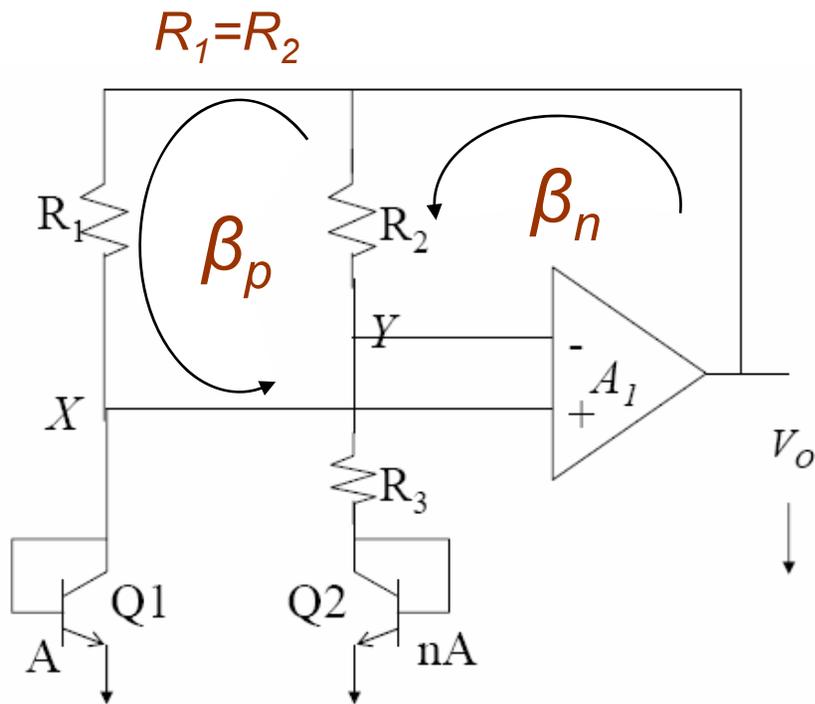

$$\beta_n = \frac{R_3 + 1/g_{m2}}{R_2 + R_3 + 1/g_{m2}} \quad \beta_p = \frac{1/g_{m1}}{R_1 + 1/g_{m1}}$$

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = \frac{\ln(N)}{R}$$


$$\beta_n = \frac{1 + R_3 * g_{m2}}{(R_1 + R_3)g_{m2} + 1} = \frac{1 + \ln(N)}{18.2}$$

$$\beta_p = \frac{1}{1 + R_1 * g_{m1}} = \frac{1}{18.2 - \ln(N)}$$


- ❑ For stable operation  $\beta_n$  must be greater than  $\beta_p$  ; negative feedback should dominate positive feedback




# Band gap reference: Results

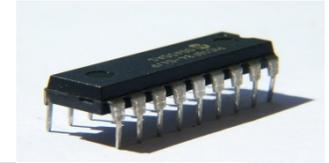

## (1) Tempco at $V_{DD} = 3.3V$


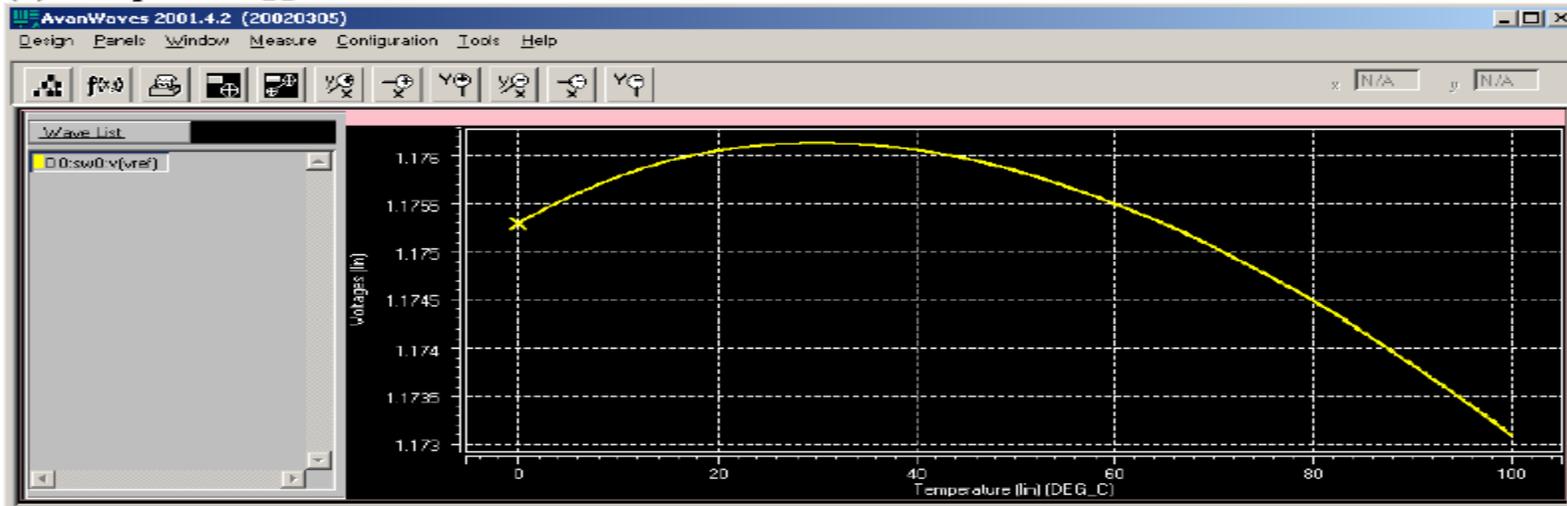


## (2) Supply-voltage dependence


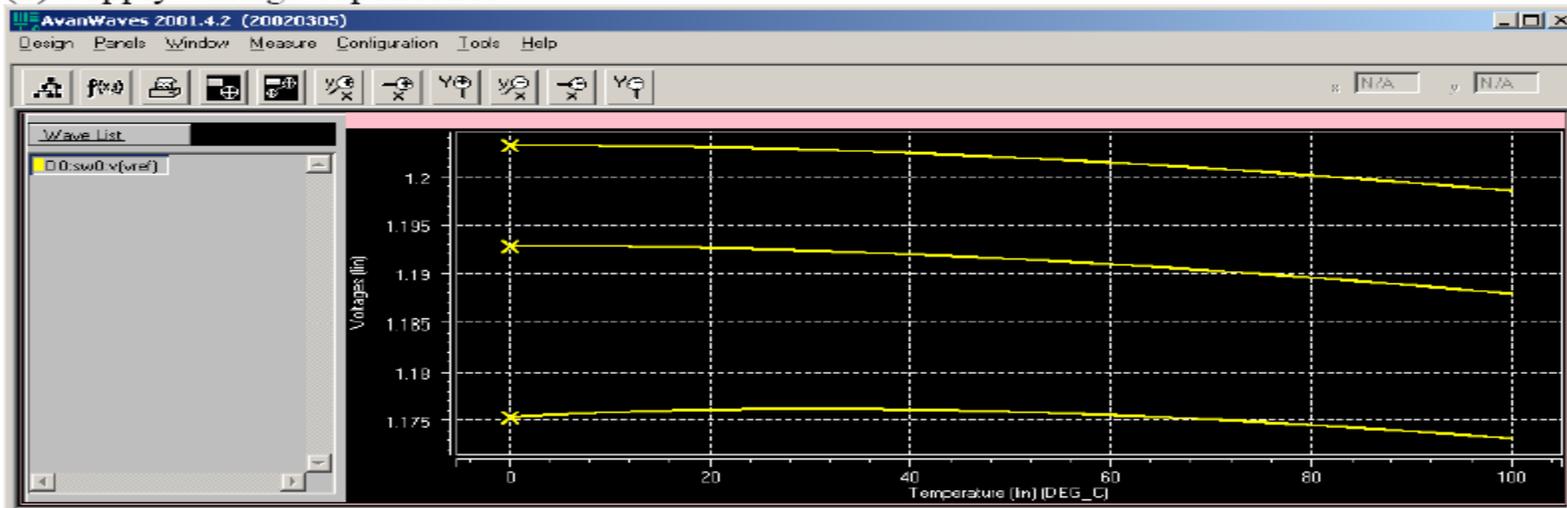



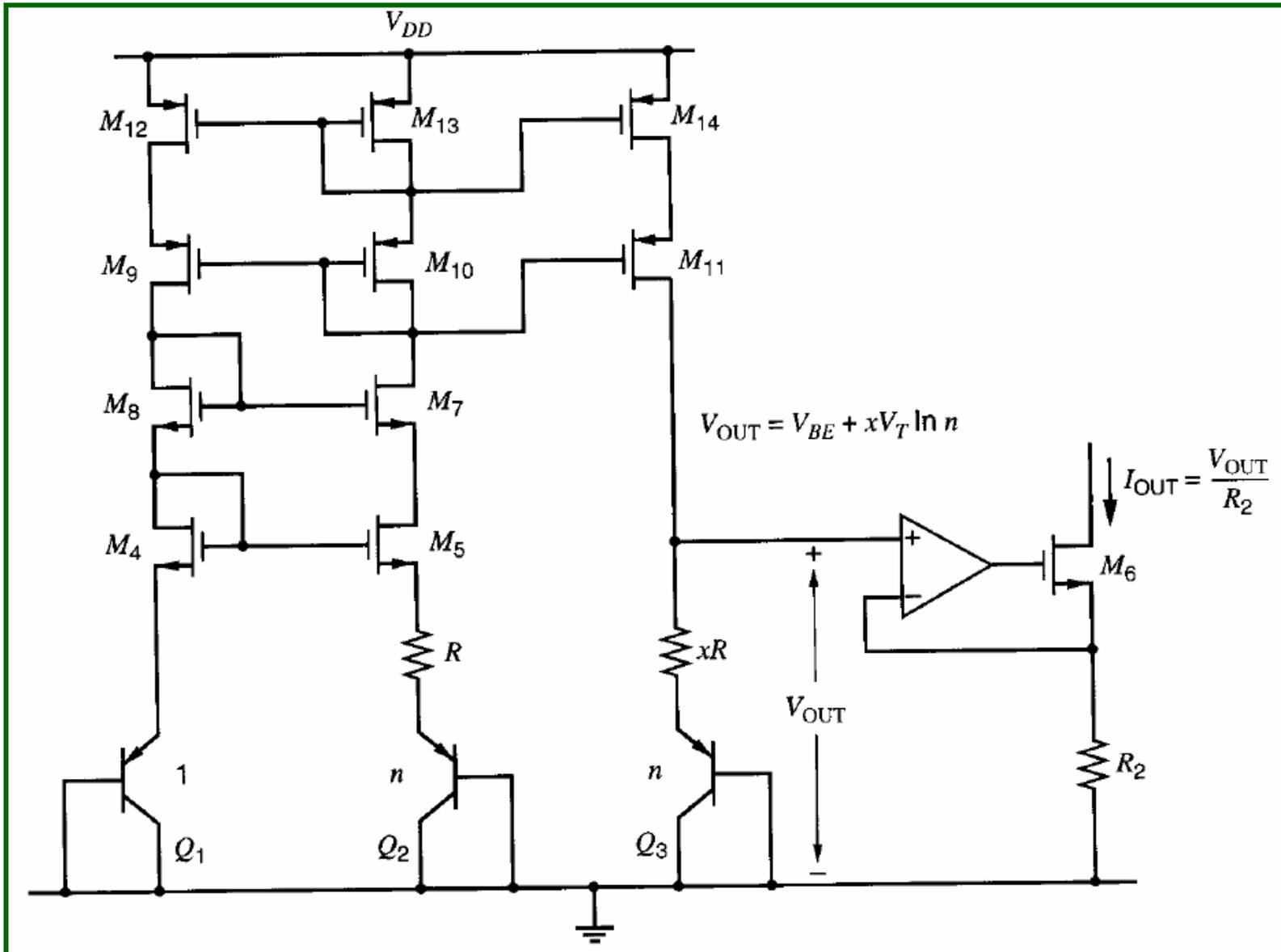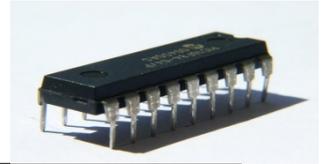
# Temperature Independent Current Reference


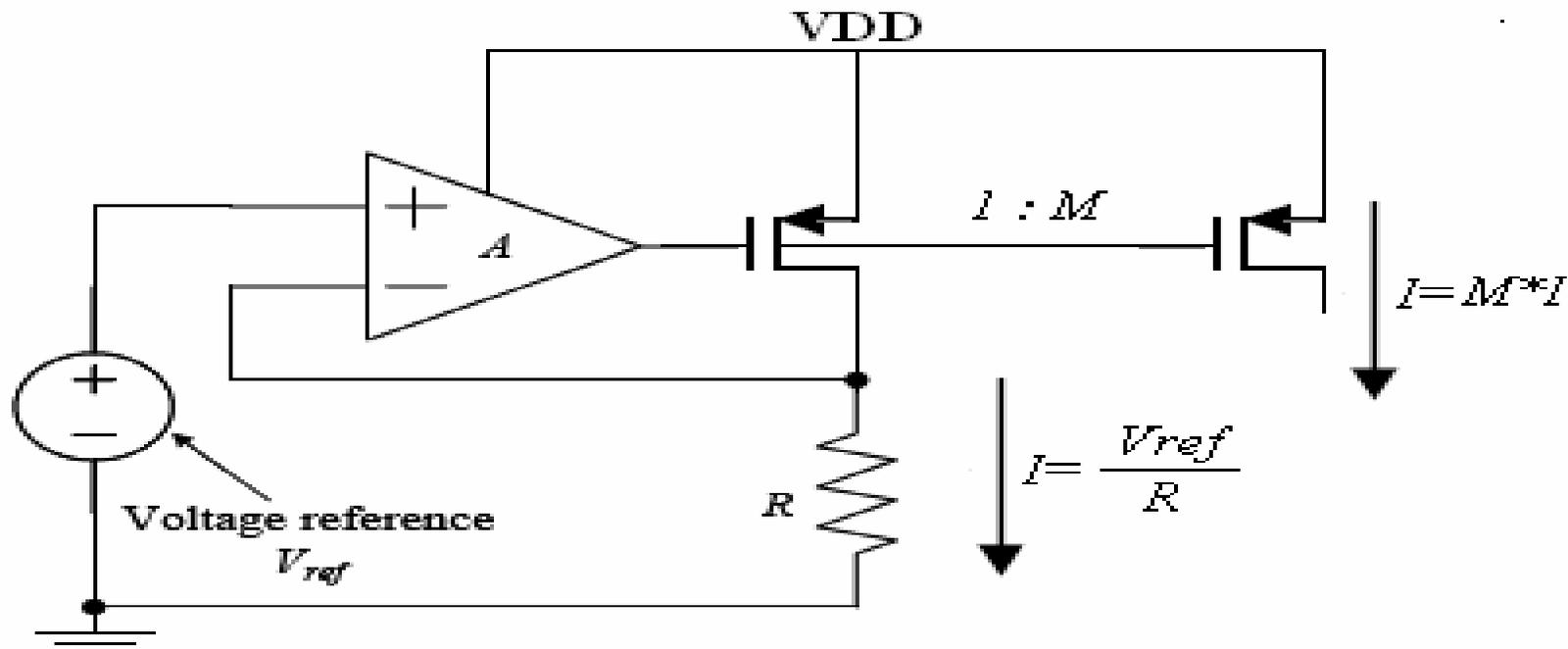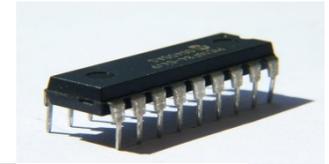
# Current reference generated from voltage reference




Resistor can be modeled

$$R(T) = R(T_r) \cdot [1 + k_1(T - T_r) + k_2(T - T_r)^2] \approx R(T_r) \cdot [1 + k_1(T - T_r)]$$


Material	n-well	poly	p-diffusion	n-diffusion	high-R poly
$k_1$	$6.60 \times 10^{-3} \text{K}^{-1}$	$0.75 \times 10^{-3} \text{K}^{-1}$	$1.80 \times 10^{-3} \text{K}^{-1}$	$1.65 \times 10^{-3} \text{K}^{-1}$	$-1.05 \times 10^{-3} \text{K}^{-1}$

↑  
*Lesser Temp co.*


# LAB Assignments

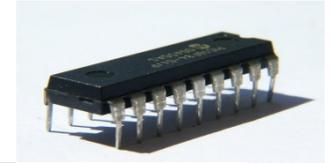

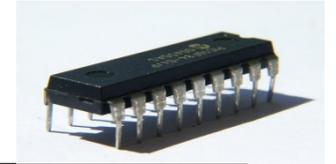- ❑ Design a 100uA current reference (Current Reference II).
- ❑ Design a band-gap reference which consumes 100uA current. Get a temperature compensated voltage at 27°C (Band gap Implementation- II).



Q & A

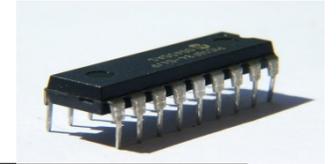

*Thank U!*