



Figure 1 A simple one-transformer dc/dc voltage doubler has cross-coupled RC networks from the collectors of Q_1 and Q_2 to the corresponding bases. These networks provide regenerative feedback.