



Find s_{12}

$$S_{22} = 0.33 < 0$$

$$S_{11} = 0.33 < 180$$

$$S_{21} = 0.67 < -90$$

My Solution:

$$v_2^+ = \frac{v_s}{2} < 0$$

$$v_2^- = \frac{v_s}{2} < 0 \times (s_{22}) = 0.165 v_s < 0$$

$$v_2 = v_2^+ + v_2^- = 0.665 v_s < 0$$

$$v_1^- = (v_2^+ - v_2^-) < -90 = 0.335 v_s < -90$$

$$\gamma_l = \frac{z_l - z_o}{z_l + z_o} = 0.33 < 180 \text{ (load reflection coefficient looking in port 2)}$$

$$v_1^+ = \gamma_l \times v_1^- = 0.11055 v_s < 90$$

$$v_1 = v_1^+ + v_1^- = 0.23 v_s < -90$$

$$s_{12} = \frac{v_1}{v_2} \times (1 + s_{22}) = 0.47 < -90$$

