

# EE5321/EE7321

# Semiconductor Devices and Circuits


Frequency Response Part1

# Impedance network transfer function

- Impedance network transfer function:

$$H(\omega) = \frac{V_{\text{out}}(\omega)}{V_{\text{in}}(\omega)}$$

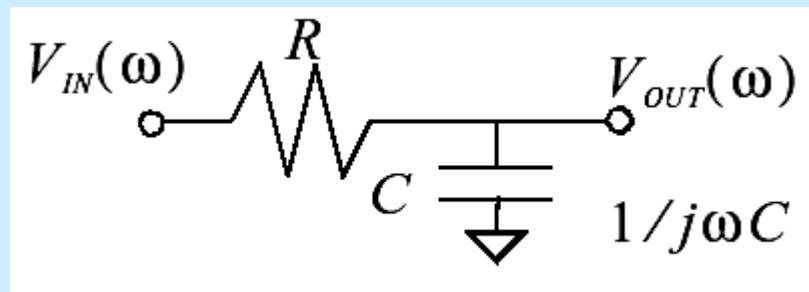where  $H(\omega)$ ,  $V_{\text{out}}(\omega)$  and  $V_{\text{in}}(\omega)$  are phasors



$$H(\omega) = \frac{V_{\text{out}}(\omega)}{V_{\text{in}}(\omega)} = \frac{\frac{1}{j\omega C}}{R + \left(\frac{1}{j\omega C}\right)} = \frac{1}{1 + j\omega RC}$$

# $H(\omega)$ in polar coordinates

- $H(\omega)$  is represented by its amplitude and phase
- Amplitude  $|H(\omega)|$

$$|H(\omega)| = \sqrt{H(\omega) \bullet H^*(\omega)}$$

- Phase  $\angle \theta$

$$\theta(\omega) = \arctan \left\{ \frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]} \right\}$$

- If  $H(\omega) = N(\omega) / D(\omega)$  then:

$$\text{Re}[H(\omega)] = \text{Re}[N(\omega) \cdot D^*(\omega)]$$

$$\text{Im}[H(\omega)] = \text{Im}[N(\omega) \cdot D^*(\omega)]$$

# $H(\omega)$ for the RC circuit

- Amplitude

$$\sqrt{H(\omega) \bullet H^*(\omega)} = \sqrt{\left( \frac{1}{1 + j \omega R C} \right) \bullet \left( \frac{1}{1 - j \omega R C} \right)}$$

$$\sqrt{H(\omega) \bullet H^*(\omega)} = \sqrt{\left( \frac{1}{1 + (\omega R C)^2} \right)}$$

- Amplitude in Decibels  $|H(\omega)|_{dB} = 20 \bullet \log [ |H(\omega)| ]$
- For a -3dB reduction on the magnitude

$$-3 = 20 \bullet \log [ |H(\omega_{3dB})| ] \quad \rightarrow \quad |H(\omega_{3dB})| = 0.7079$$


# Bode Plot RC circuit - Amplitude

$$|\mathcal{H}(\omega_{3dB})| = \sqrt{\left( \frac{1}{1 + (\omega_{3dB} R C)^2} \right)} = 0.7079 \quad \rightarrow \quad \omega_{3dB} = \omega_p = \frac{1}{R C}$$

$$|\mathcal{H}(\omega)| = \sqrt{\left( \frac{1}{1 + \left( \frac{\omega}{\omega_{3dB}} \right)^2} \right)}$$

For  $\omega \gg \omega_{3dB}$

$$|\mathcal{H}(\omega)| \approx \sqrt{\left( \frac{1}{\left( \frac{\omega}{\omega_{3dB}} \right)^2} \right)}$$

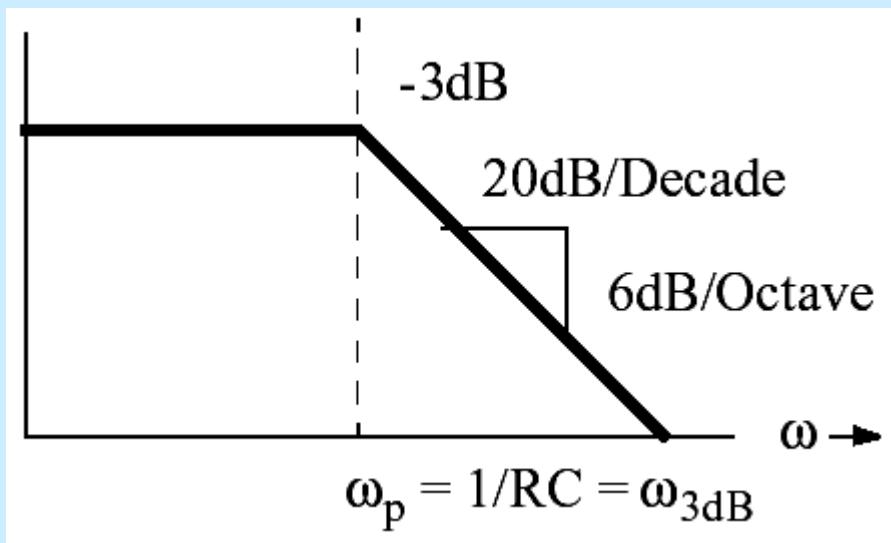

$$|\mathcal{H}(\omega)| \approx \frac{\omega_{3dB}}{\omega}$$

Amp drops by 2 when f doubles

Amp drops by 10 every decade

# Bode Plot RC circuit - Phase

- $H(\omega)$  phase

$$\theta(\omega) = \arctan \left\{ \frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]} \right\}$$

$$H(\omega) = \frac{1}{1 + j \frac{\omega}{\omega_{3dB}}} = \frac{1}{1 + j \frac{\omega}{\omega_{3dB}}} \bullet \frac{1 - j \frac{\omega}{\omega_{3dB}}}{1 - j \frac{\omega}{\omega_{3dB}}} = \frac{1 - j \frac{\omega}{\omega_{3dB}}}{1 + \left( \frac{\omega}{\omega_{3dB}} \right)^2}$$


$$\text{Re}\{ H(\omega) \} = \frac{1}{1 + \left( \frac{\omega}{\omega_{3dB}} \right)^2}$$

$$\text{Im}\{ H(\omega) \} = \frac{-j \frac{\omega}{\omega_{3dB}}}{1 + \left( \frac{\omega}{\omega_{3dB}} \right)^2}$$
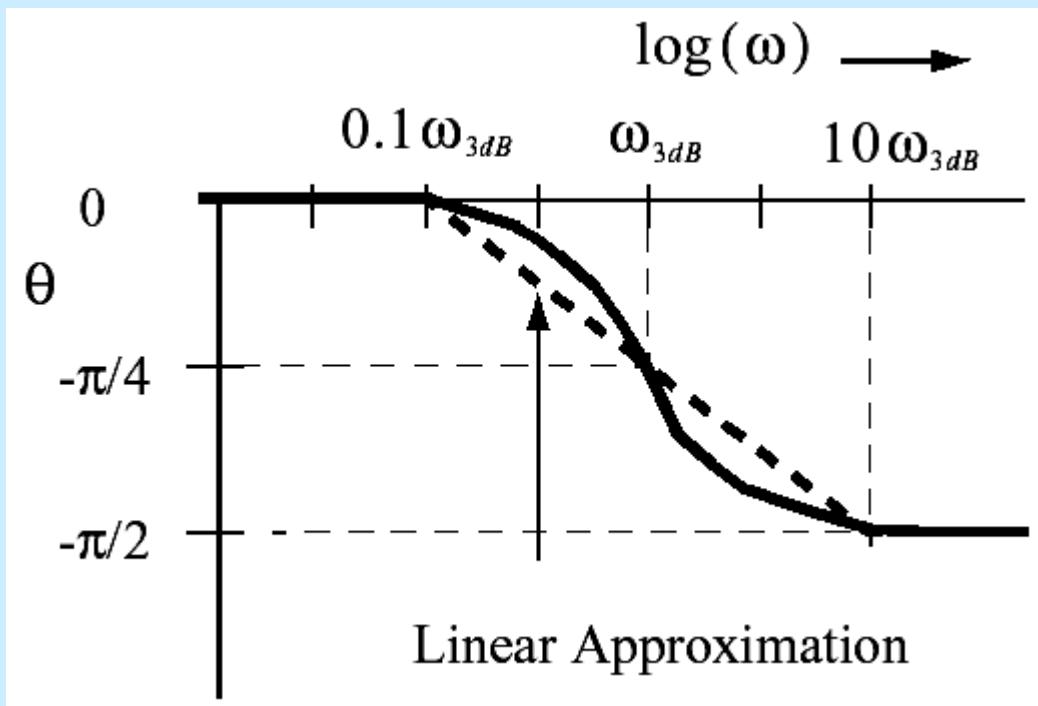
# Bode Plot RC circuit - Phase




- And the Phase is given by:

$$\theta(\omega) = \arctan \left\{ \frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]} \right\} = \arctan \left\{ -\frac{\omega}{\omega_{3dB}} \right\} = -\arctan \left\{ \frac{\omega}{\omega_{3dB}} \right\}$$


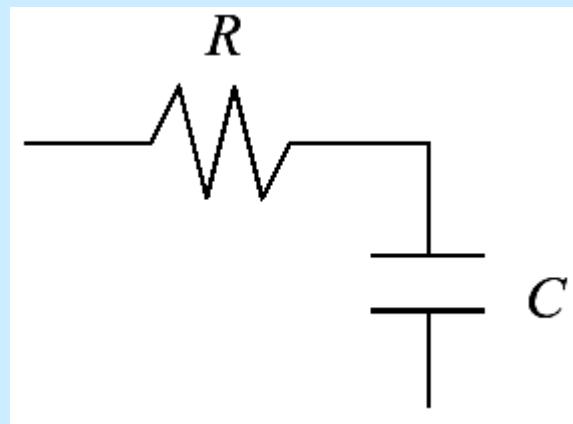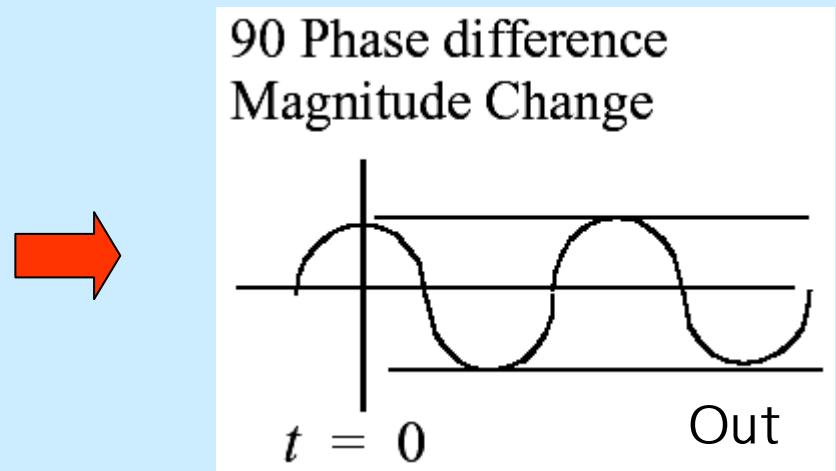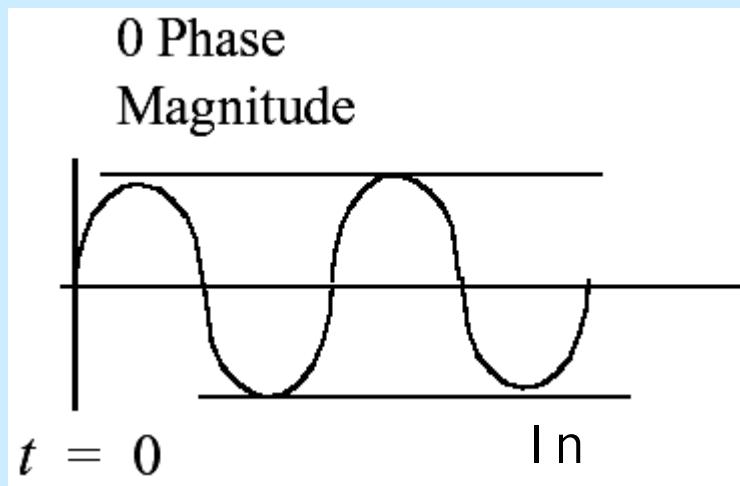
# RC circuit - sine wave

- The output wave has amplitude and phase altered by the circuit





$$H(\omega) = \frac{1}{1 + j \omega R C}$$
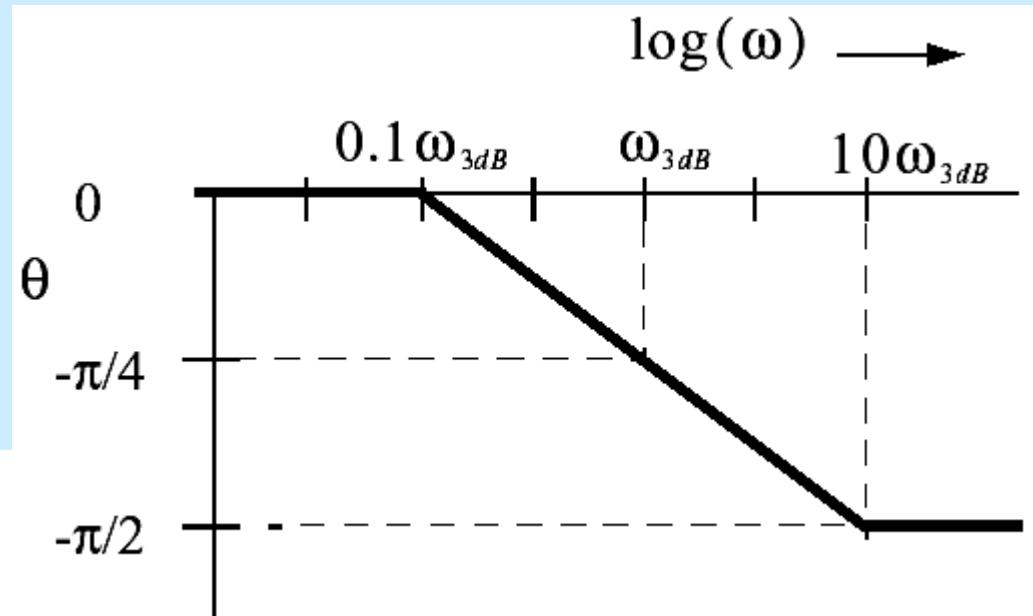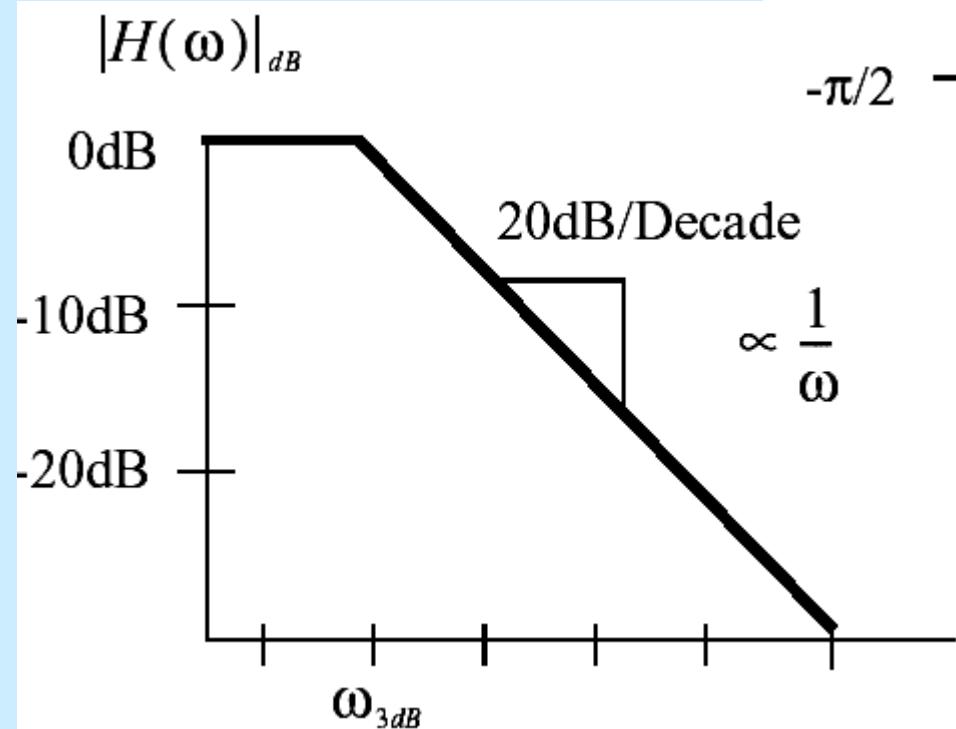
# Bode Plots – 1 pole

- RC circuit

$$\omega_{3dB} = \omega_p = \frac{1}{R C}$$




$$\theta(\omega) = -\arctan\left\{\frac{\omega}{\omega_{3dB}}\right\}$$

$$|H(\omega)| \approx \frac{\omega_{3dB}}{\omega}$$
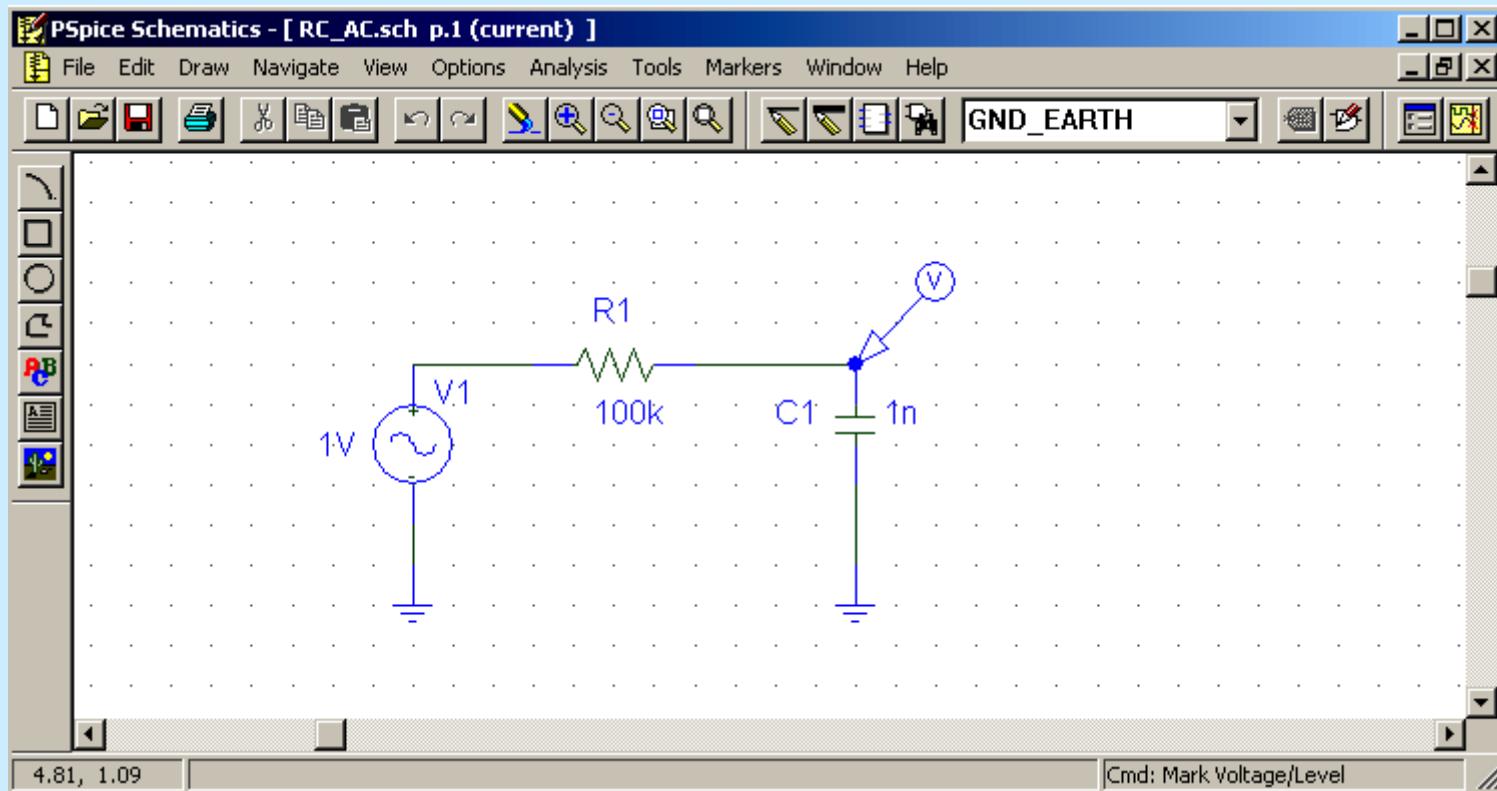
# SPICE SIM - RC circuit

- Run AC Sweep with 1V amplitude and freq: 10Hz to 100MHz
- Output DB[V2(C1)/V1(V1)] and P[V2(C1)]



# SPICE SIM - RC circuit

- $\omega_p = 1/RC = 10k \rightarrow f_p = 1.6\text{kHz}$




# RC circuits in series – 2 poles

- The combination of two RC circuits in series is going to result in 2 poles

$$H(\omega) = \frac{1}{1 + j \frac{\omega}{\omega_{p1}}} \bullet \frac{1}{1 + j \frac{\omega}{\omega_{p2}}}$$

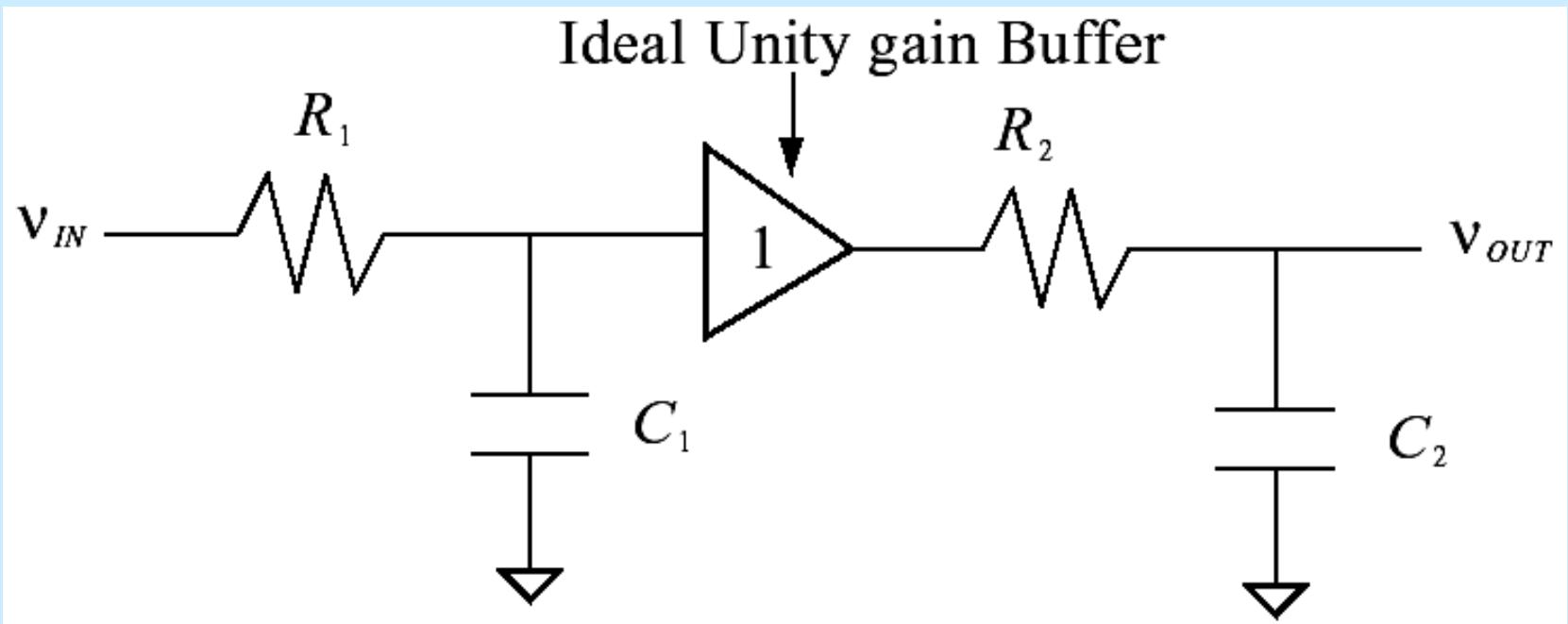where:  $\omega_{p1} = 1/R_1 C_1$  and  
 $\omega_{p2} = 1/R_2 C_2$



## RC circuits in series – 2 poles

- Overall transfer function  $H(\omega) = H\omega_{p1}(\omega) \bullet H\omega_{p2}(\omega)$

$$H(\omega) = [ |H_{\omega p1}| \bullet \exp(j\theta_{\omega p1}) ] \bullet [ |H_{\omega p2}| \bullet \exp(j\theta_{\omega p2}) ]$$

$$H(\omega) = |H_{\omega p1}| \bullet |H_{\omega p2}| \bullet \exp(j[\theta_{\omega p1} + \theta_{\omega p2}])$$

$$H(\omega) = |H(\omega)| \bullet \exp(j\theta(\omega))$$


$$\therefore |H(\omega)| = |H_{\omega p1}| \bullet |H_{\omega p2}| \text{ and } \theta(\omega) = \theta_{\omega p1} + \theta_{\omega p2}$$

# Amplitude Bode Plot - 2 poles

- Second pole "accelerates" the amplitude reduction

$$20 \cdot \log\{|\mathcal{H}(\omega)|\} = 20 \cdot \log\{|\mathcal{H}(\omega_{p1})| \cdot |\mathcal{H}(\omega_{p2})|\}$$


$$20 \cdot \log\{|\mathcal{H}(\omega)|\} = 20 \cdot \log\{|\mathcal{H}(\omega_{p1})|\} + 20 \cdot \log\{|\mathcal{H}(\omega_{p2})|\}$$

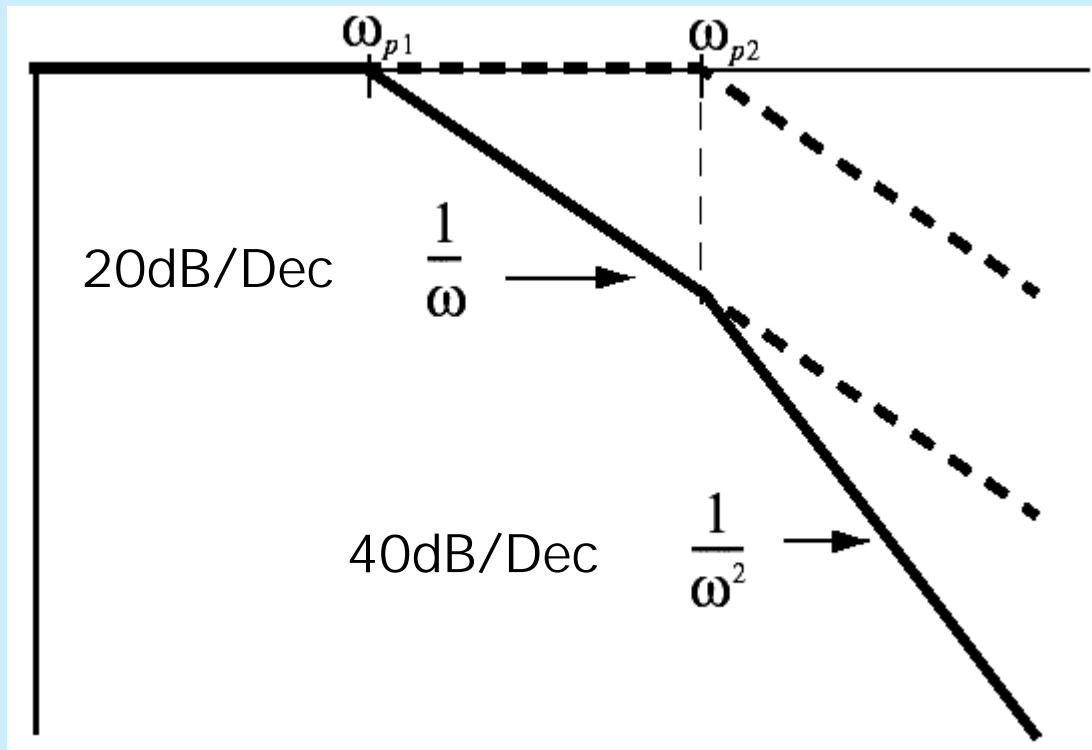
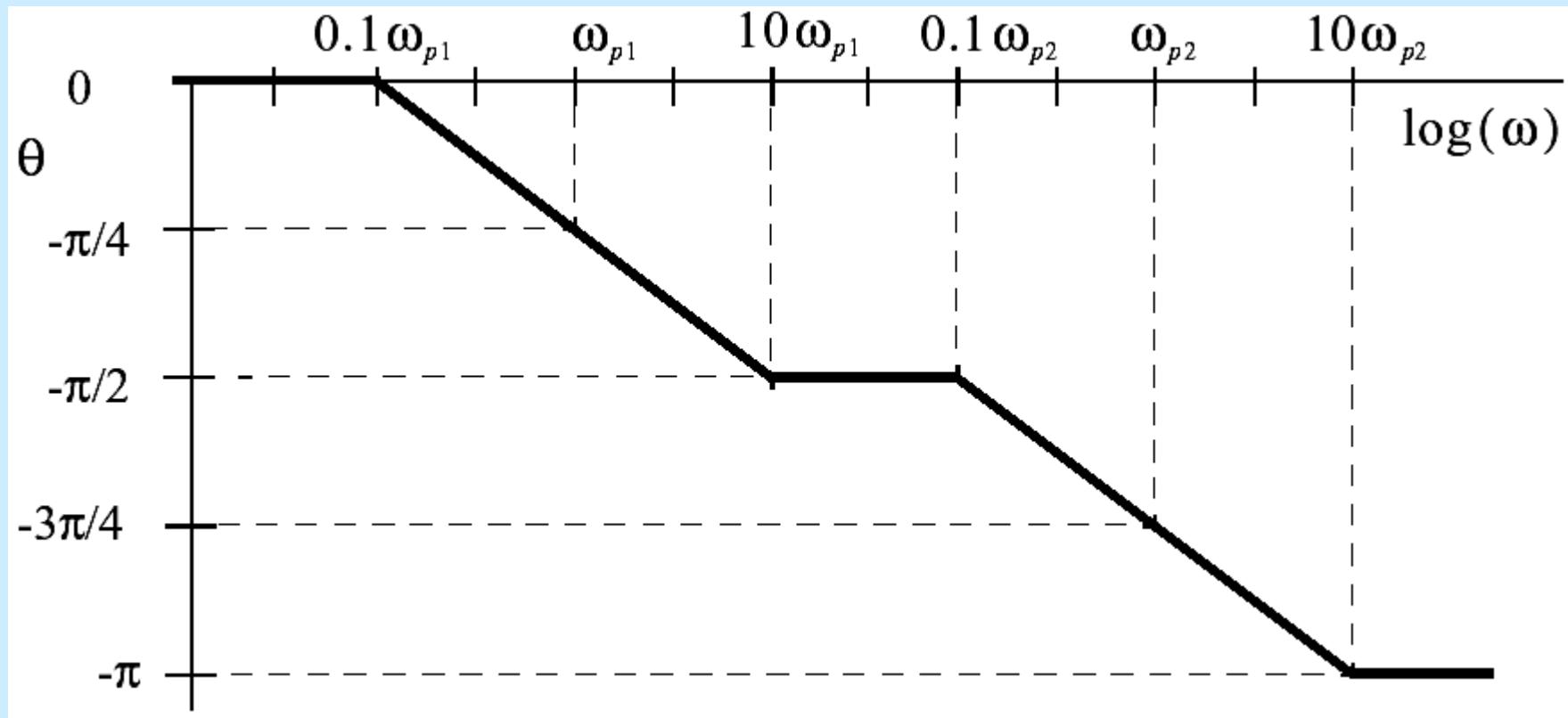
# Phase Bode Plot – 2 poles


- Second pole adds to the phase shift

$$\theta(\omega) = \theta_{\omega p_1} + \theta_{\omega p_2}$$



# 2 poles circuit – 180° phase shift


- A phase shift of 180° can be a problem

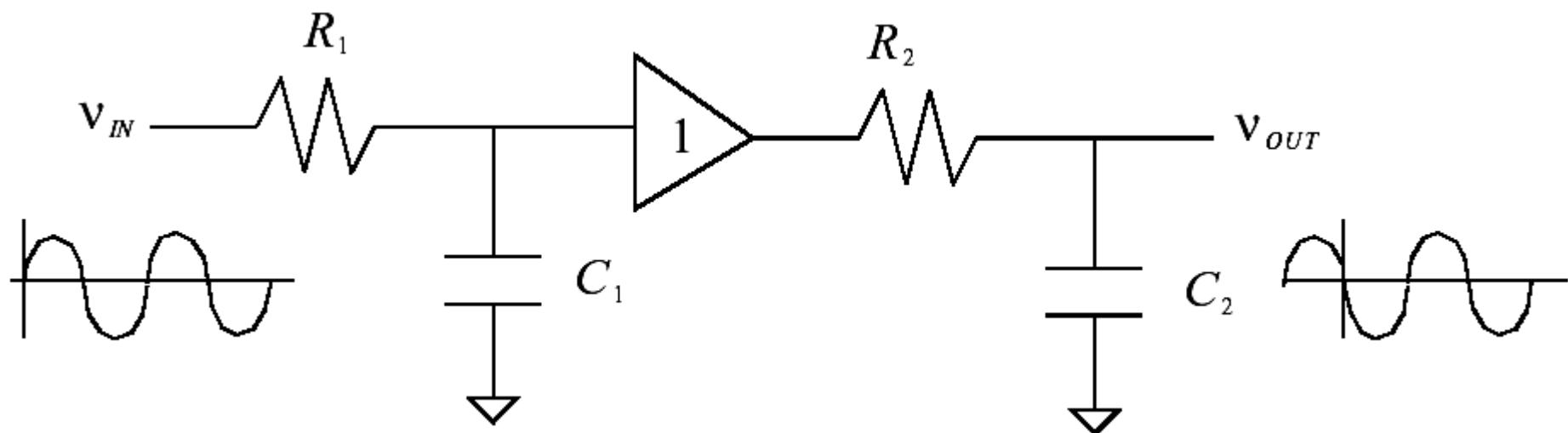

- If in a feedback loop, a 180° phase shift will turn a negative feedback into a positive feedback
- This results in an unstable system if the loop gain is  $> 1$
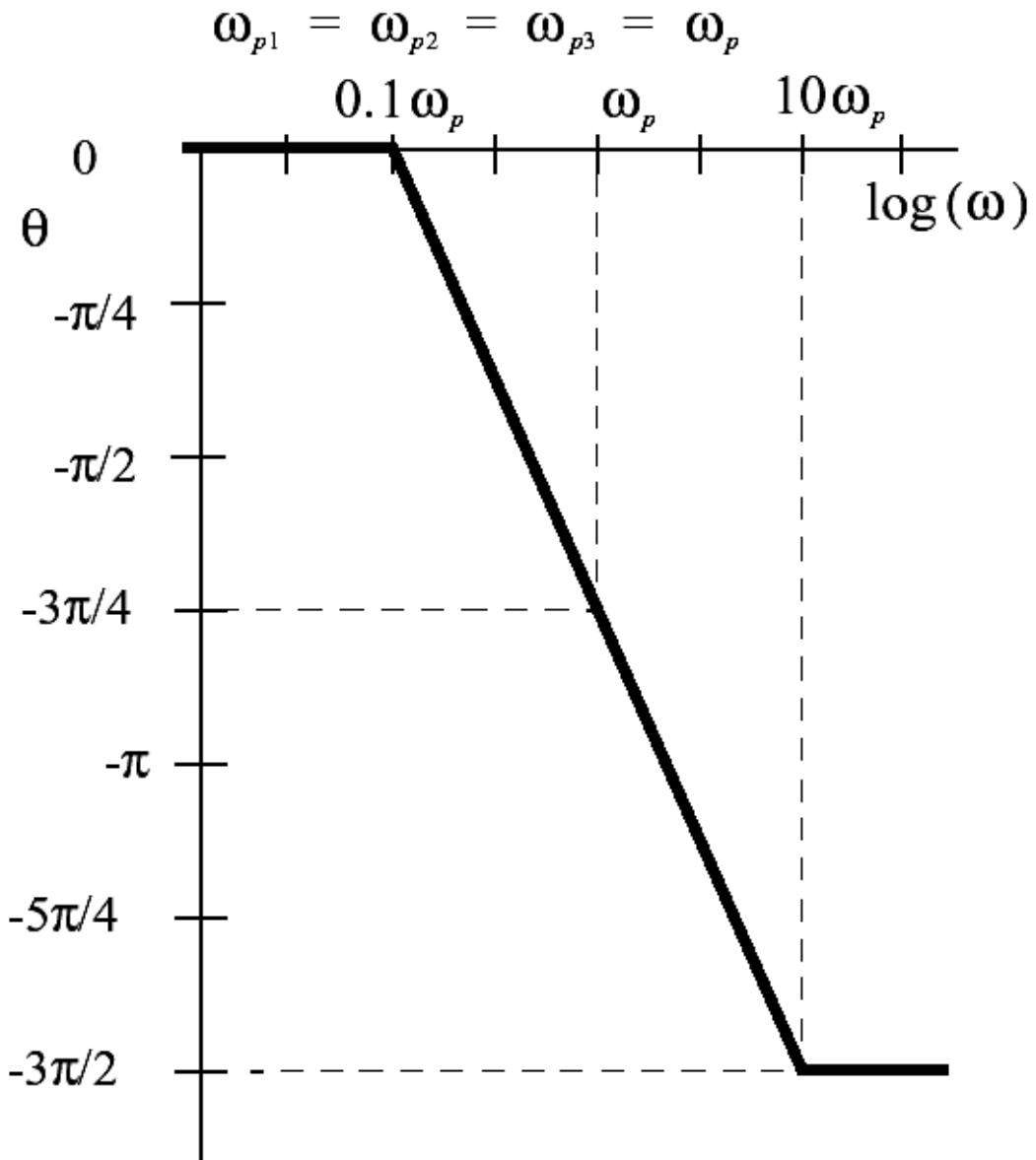
# Bode Plots – 3 Superimposed Poles

- The phase shift is quite “fast” and “strong”
- When used in a feedback loop will probably result in an unstable circuit




# C R circuit - $H(\omega)$

- Circuit has:

- 1 Zero at  $\omega = 0$

- 1 Pole at  $\omega = 1/R C$
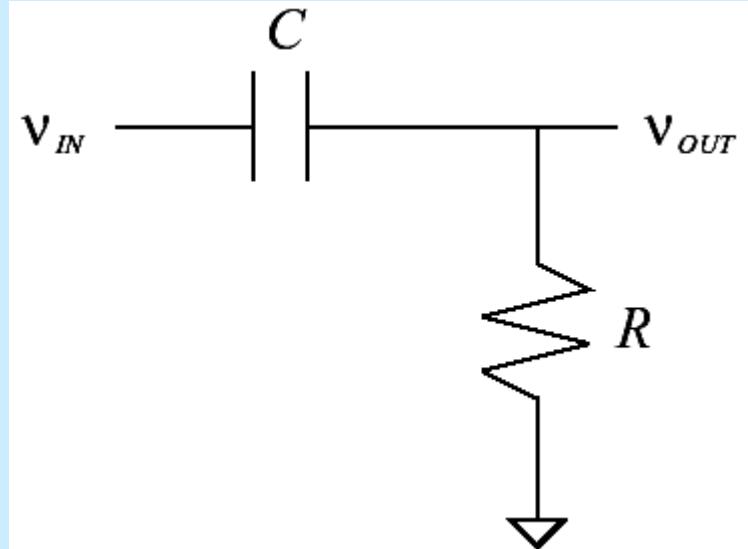
$$H(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)}$$



$$H(\omega) = \frac{R}{R + \left( \frac{1}{j\omega C} \right)} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega RC}{1 + j\frac{\omega}{1/RC}}$$


$$|H(\omega)| = \omega RC \cdot \sqrt{\frac{1}{1 + (\omega RC)^2}}$$

# C R circuit – Bode plot amplitude

- At  $\omega = 0 \rightarrow |H(\omega)| = 0$  and since  $|H(\omega)|_{dB} = 20 \cdot \log[|H(\omega)|]$

$$|H(\omega)|_{dB} = 20 \cdot \log\left(\omega R C \cdot \sqrt{\frac{1}{1 + (\omega R C)^2}}\right) \rightarrow -\infty$$


$$|H(\omega_p)|_{dB} = 20 \cdot \log\left(1 \cdot \sqrt{\frac{1}{1 + (1)^2}}\right) = -3\text{dB}$$

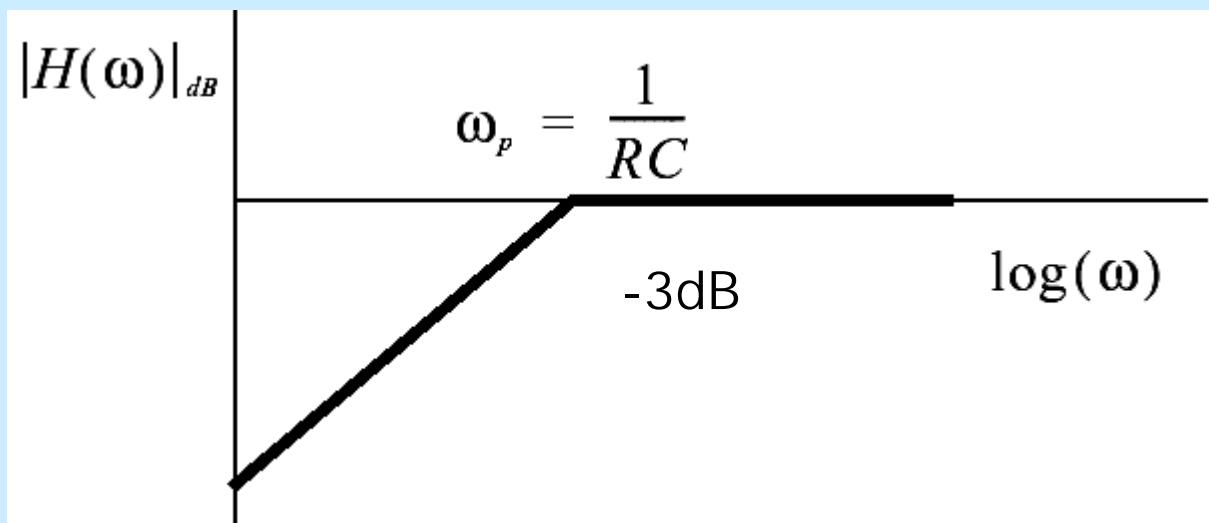

$$\begin{aligned}|H(\omega > \omega_p)|_{dB} &= 20 \cdot \log(1) \\ &= 0\end{aligned}$$

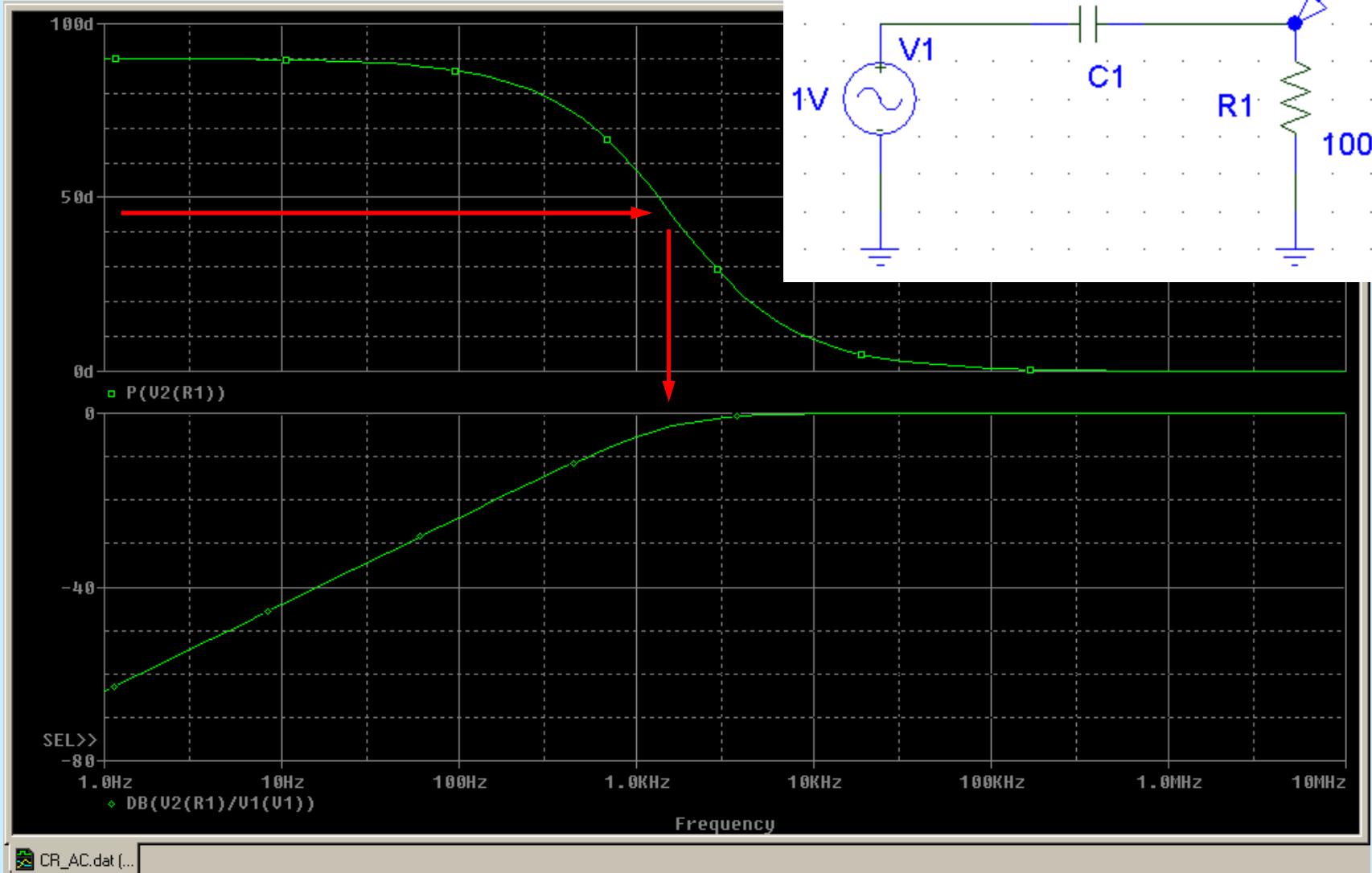
# SPICE SIM - C R circuit

- $\omega_p = 1/RC = 10k \rightarrow f_p = 1.6\text{kHz}$


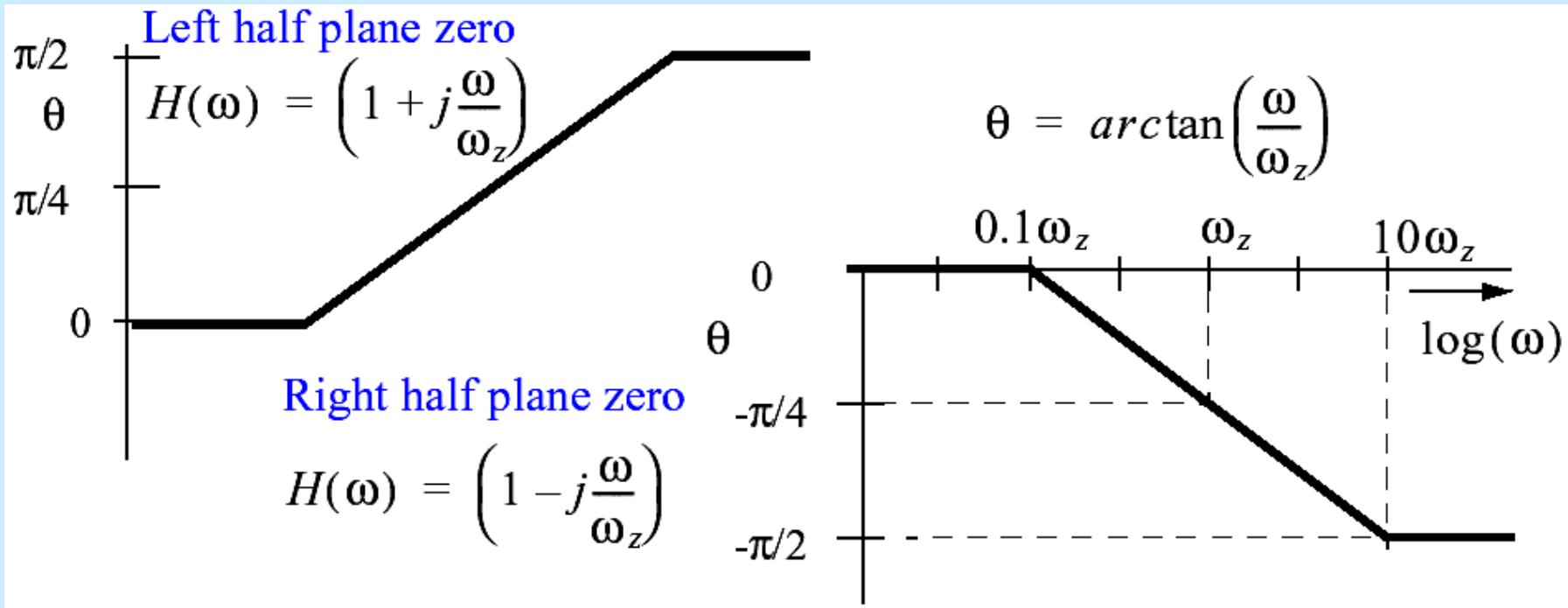
# Zero's phase response

- The phase response of a Zero depends on which half plane the Zero is located



$$H(s) = 1 - \frac{s}{s_z}$$


$$s_z = -j \omega_z$$

$$H(s) = 1 + \frac{s}{s_z}$$

# Zero's gain response


- For Zero in either half plane the amplitude response is the same

$$|H(\omega)| = \sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2} \quad \rightarrow \quad |H(\omega)|_{dB} = 10 \cdot \log \left( 1 + \left( \frac{\omega}{\omega_z} \right)^2 \right)$$

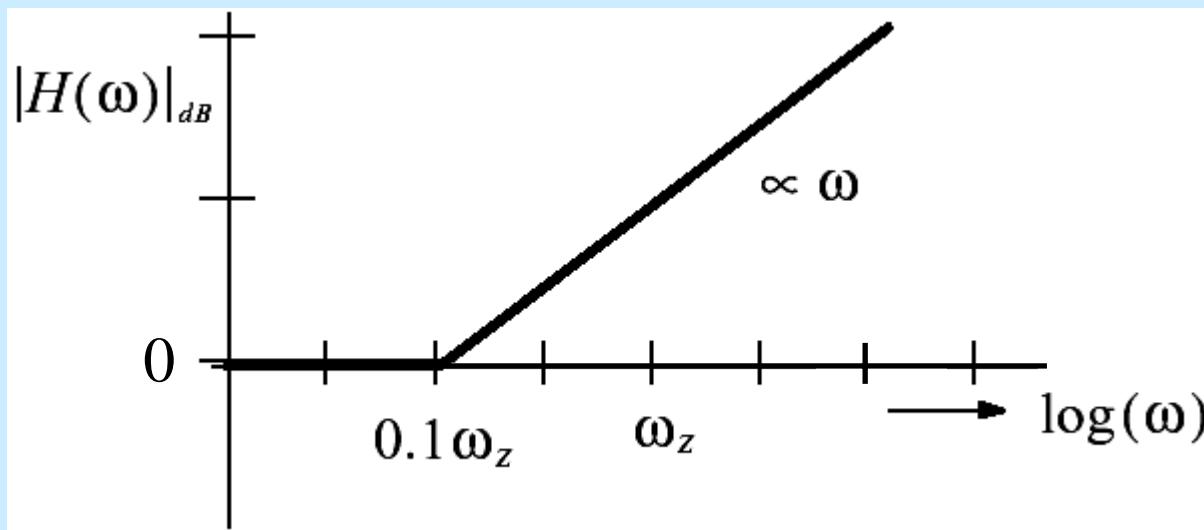


$$\begin{aligned} & |H(\omega \gg \omega_z)|_{dB} \\ & \approx 20 \cdot \log \left( \frac{\omega}{\omega_z} \right) \\ & 20 \text{dB/dec} \end{aligned}$$

# Transfer function – Other circuits

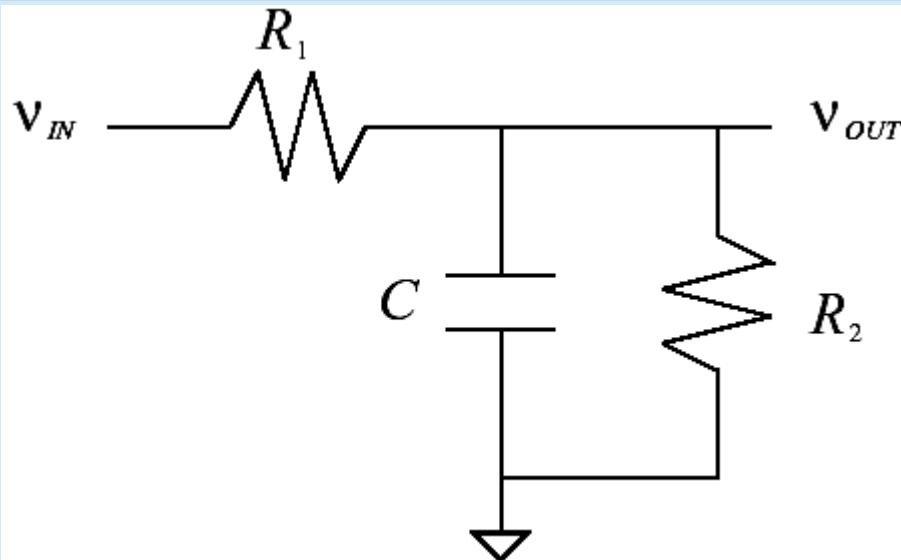

- 1 Pole

$$H(\omega) = \frac{R_2}{R_1 + R_2} \bullet \frac{1}{1 + j\omega(R_1 || R_2)C}$$

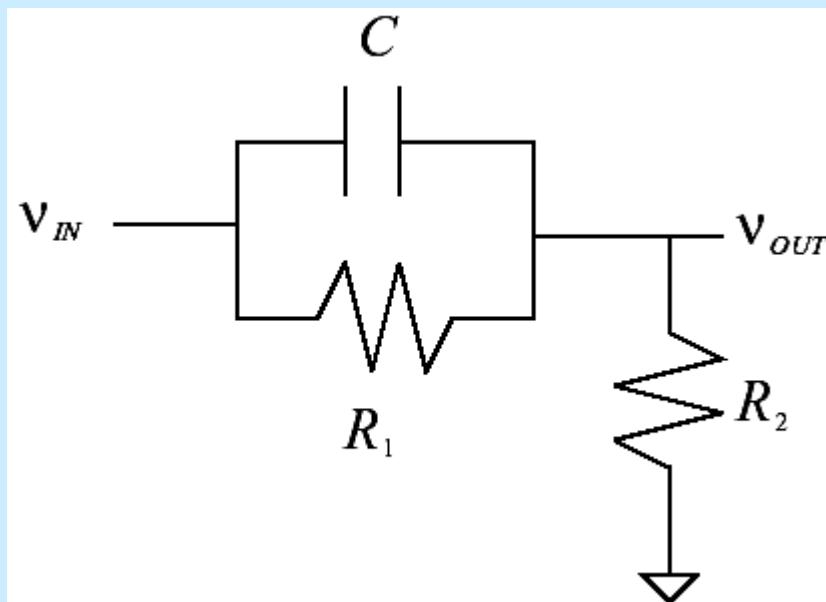


- 1 Pole, 1 Zero

$$H(\omega) = \frac{R_2}{R_1 + R_2} \bullet \frac{1 + j\omega R_1 C}{1 + j\omega(R_1 || R_2)C}$$
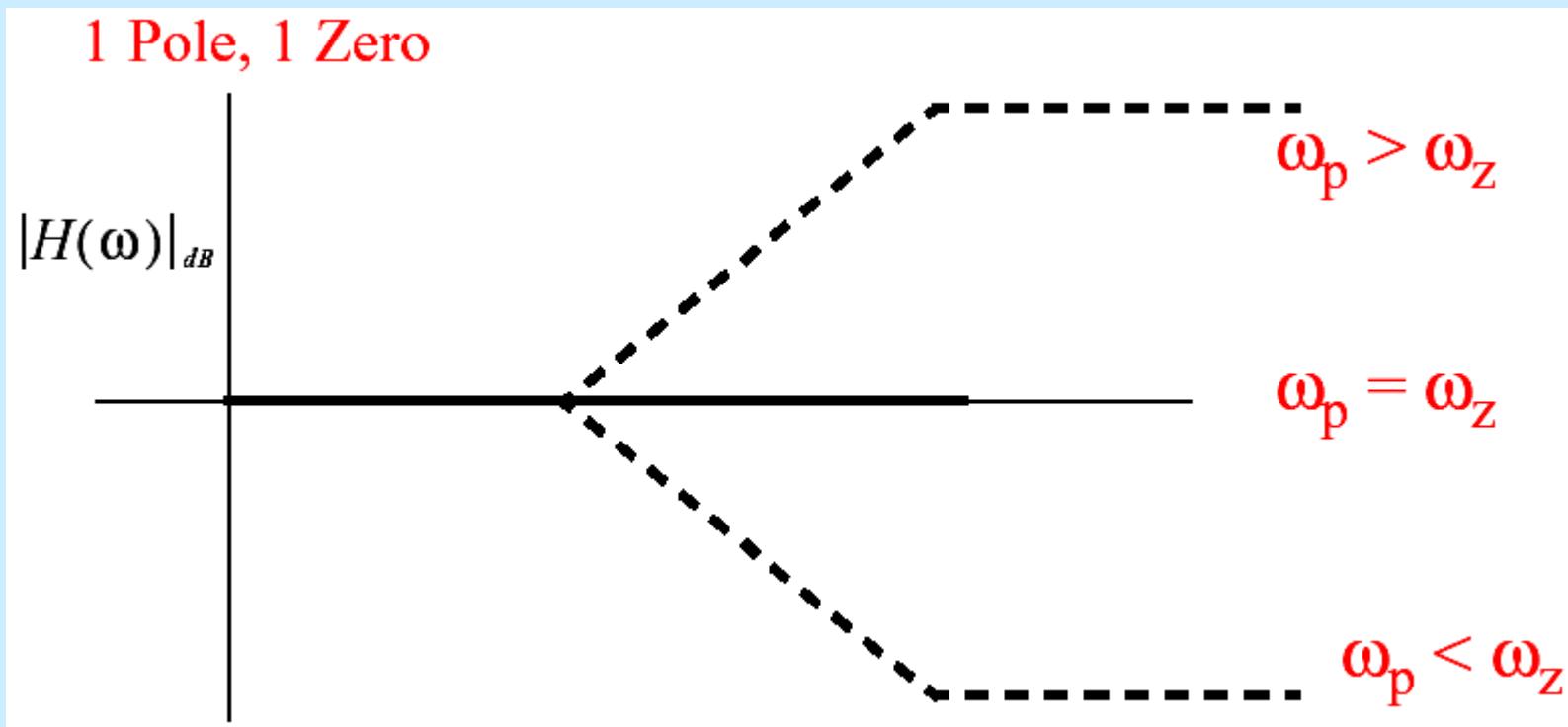
# 1 Pole, 1 Zero response

- The response depends on the relative location of the Pole and the Zero

$$H(\omega) = \frac{1 + j \frac{\omega}{\omega_z}}{1 + j \frac{\omega}{\omega_p}}$$



# MOSFET capacitances - circuit

- Specs: tox (Cox), CGSO, CGDO, CGBO, CJ, PB ( $\phi_B$ )

- Typical Values

$$C_{ox} = 10^{-4} \text{ F/m}^2$$


$$CGSO = 5 \times 10^{-10} \text{ F/m}$$

$$CGDO = 5 \times 10^{-10} \text{ F/m}$$

$$CGBO = 4 \times 10^{-10} \text{ F/m}$$

$$CJ = 10^{-4} \text{ F/m}^2$$

$$PB = 0.8 \text{ V}$$

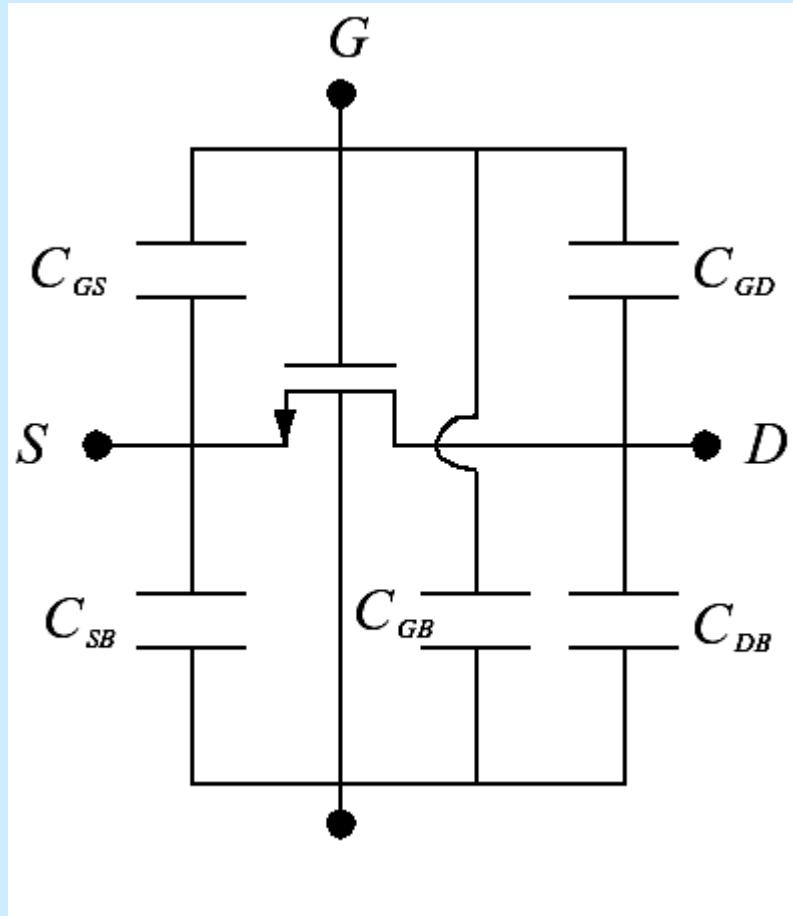

# MOSFET capacitances - equations

Saturation

$$C_{GS} = \frac{2}{3} \cdot C_{ox} \cdot L \cdot W + CGSO \cdot W$$

$$C_{GD} = CGDO \cdot W$$

Linear

$$C_{GS} = \frac{C_{ox} \cdot L \cdot W}{2} + CGSO \cdot W$$

$$C_{GD} = \frac{C_{ox} \cdot L \cdot W}{2} + CGDO \cdot W$$

with: PS = Perimeter of Source, AS = Area of Source

MJ =  $\frac{1}{2}$  (default), MJSW = 3 (default)


$$C_{SB} = \frac{CJ \cdot AS}{\left(1 + \frac{V_{BS}}{PB}\right)^{MJ}} + \frac{CJSW \cdot PS}{\left(1 + \frac{V_{BS}}{PB}\right)^{MJSW}}$$

a similar equation is used  
to calculate  $C_{DB}$

$$C_{GB} = CGBO \cdot L$$
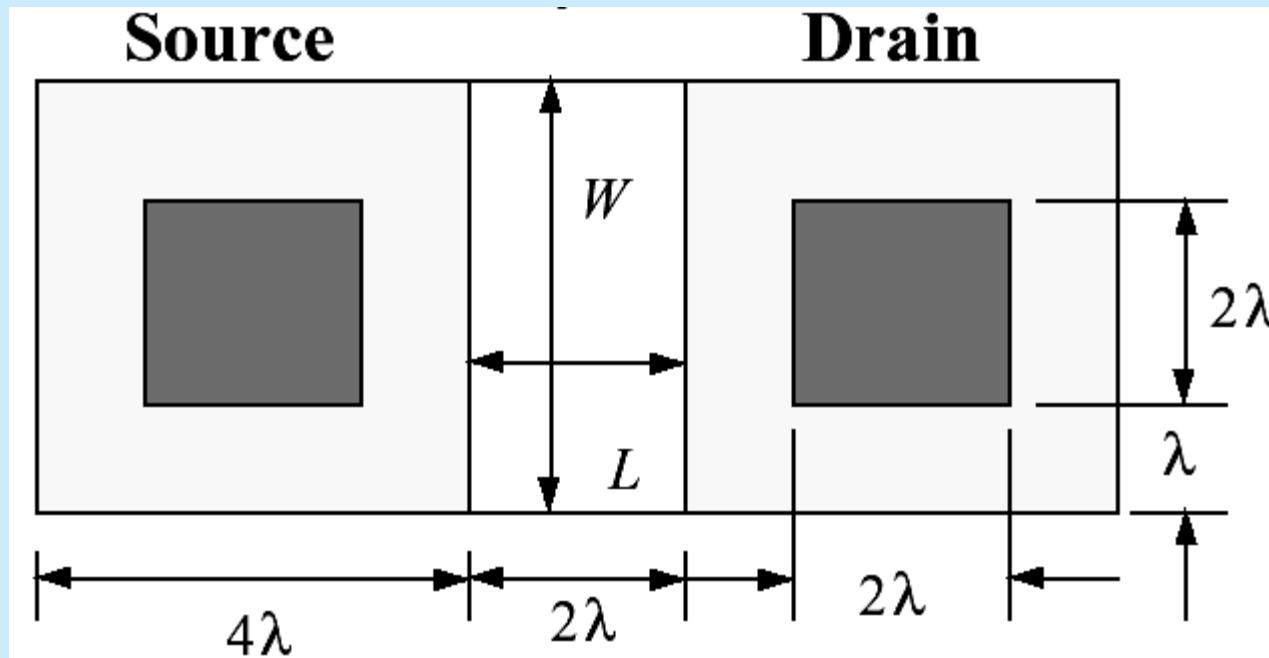
# MOSFET – classic layout


- Area of Source =  $AS = 4\lambda \cdot W$
- Area of Drain =  $AD = AS = 4\lambda \cdot W$
- Perimeter of Source =  $PS = 8\lambda + W$
- Perimeter of Drain =  $PD = 8\lambda + W$



# MOSFET – SPICE attributes

M1 1 2 3 4 NMOS L=2U W=2U

+ AS=4p AD=4p PS=6U PD=6U

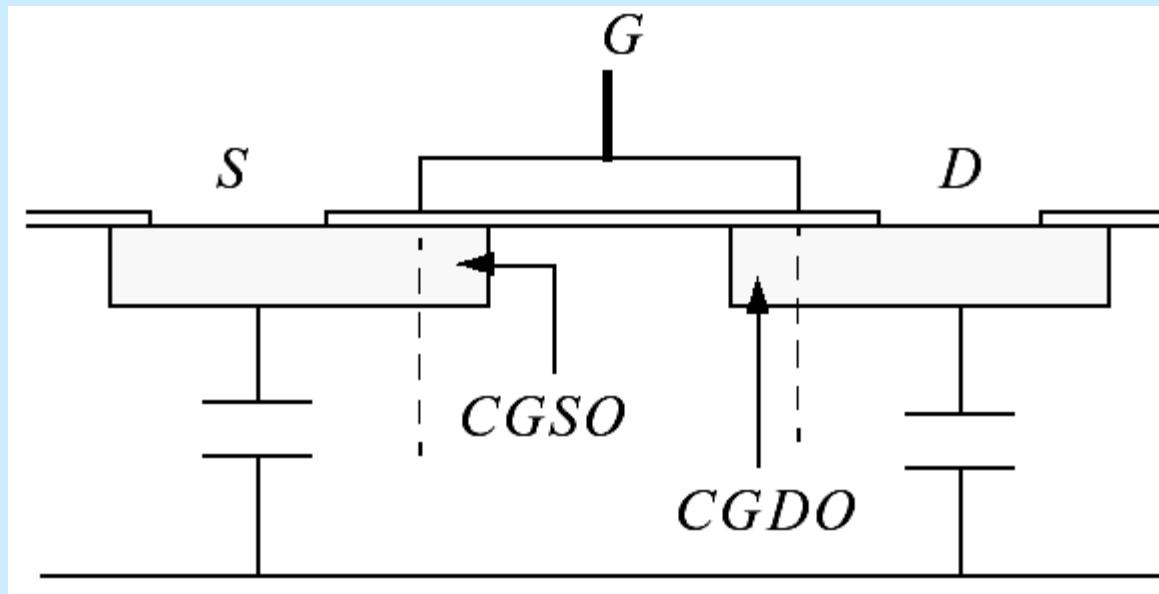

- Overlap capacitances are calculated using  $W$
- Capacitance to body have area and perimeter terms



# Miller approximation

- Capacitance between input and output appears multiplied by the gain at the input


$$i_c = C \cdot \frac{d}{dt} (v_{in} - v_{out})$$

$$i_c = C \cdot \frac{d}{dt} (v_{in} + A \cdot v_{in})$$
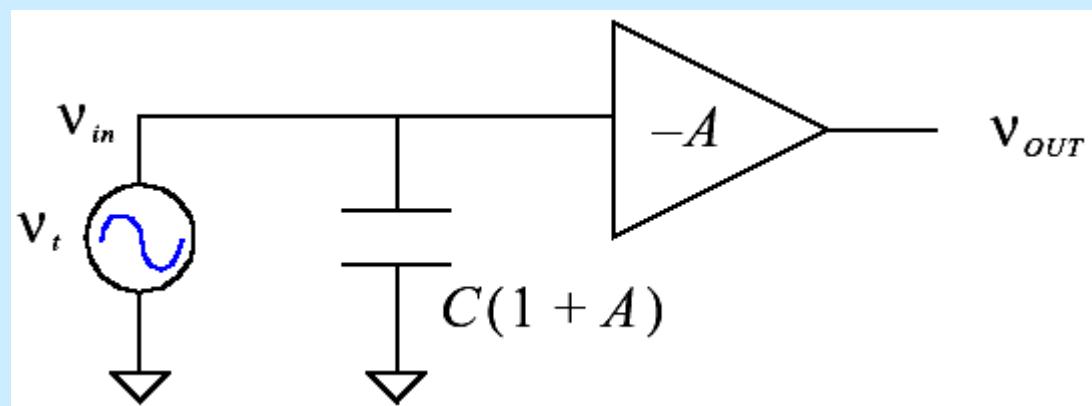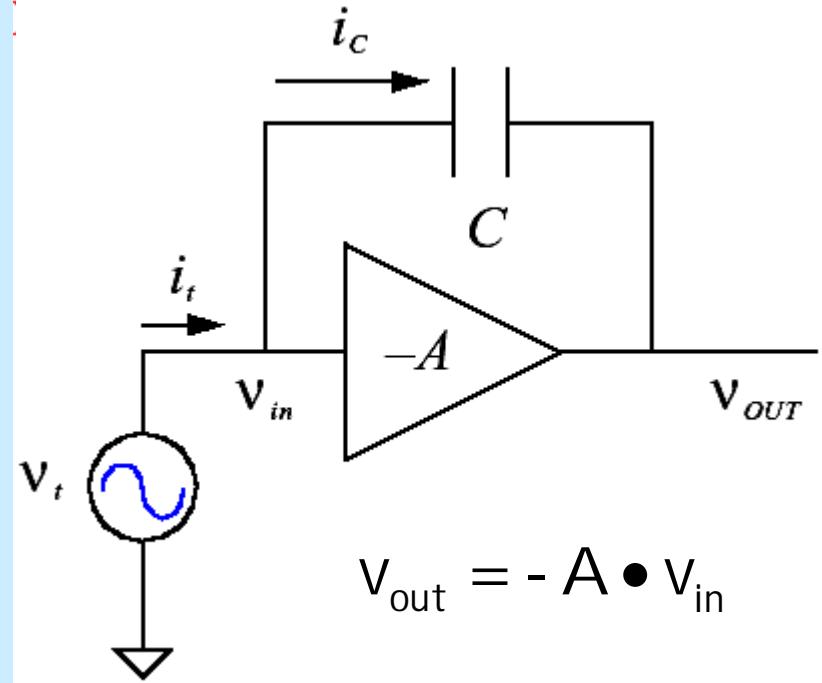
$$i_c = C \cdot (1 + A) \cdot \frac{dv_{in}}{dt}$$



# Miller approximation – Common source

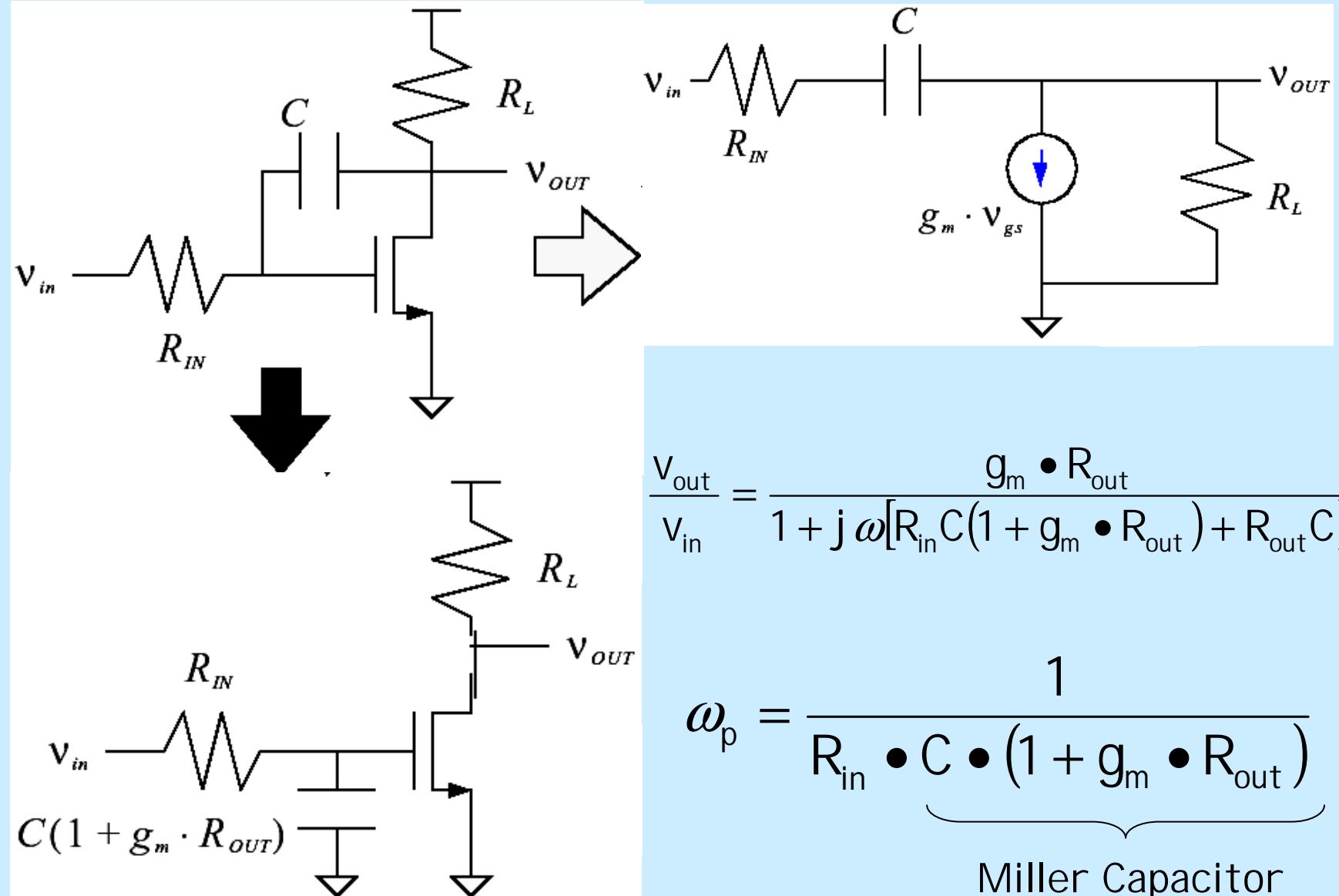



$$\frac{V_{out}}{V_{in}} = \frac{g_m \cdot R_{out}}{1 + j\omega[R_{in}C(1 + g_m \cdot R_{out}) + R_{out}C]}$$

$$\omega_p = \frac{1}{R_{in} \cdot C \cdot \underbrace{(1 + g_m \cdot R_{out})}_{\text{Miller Capacitor}}}$$

Miller Capacitor
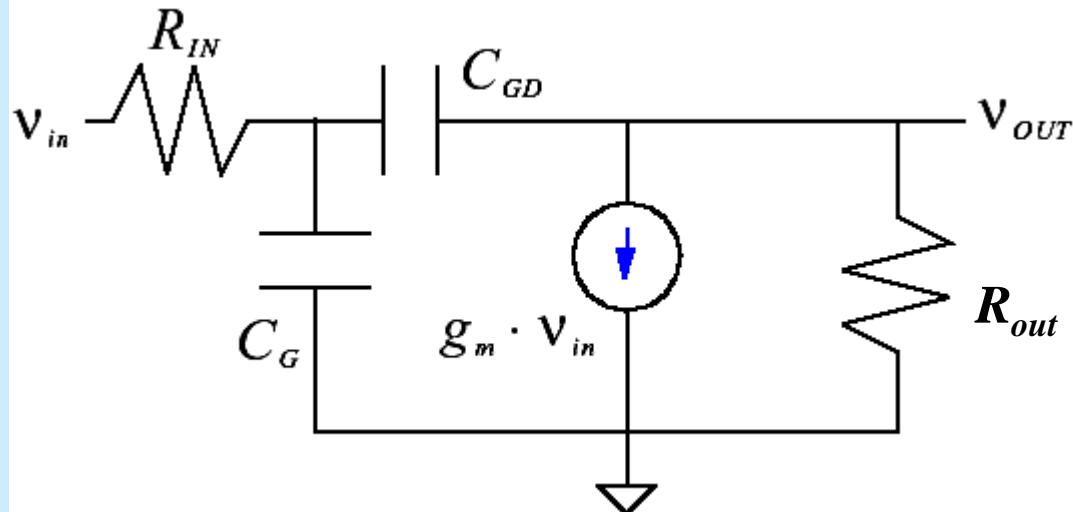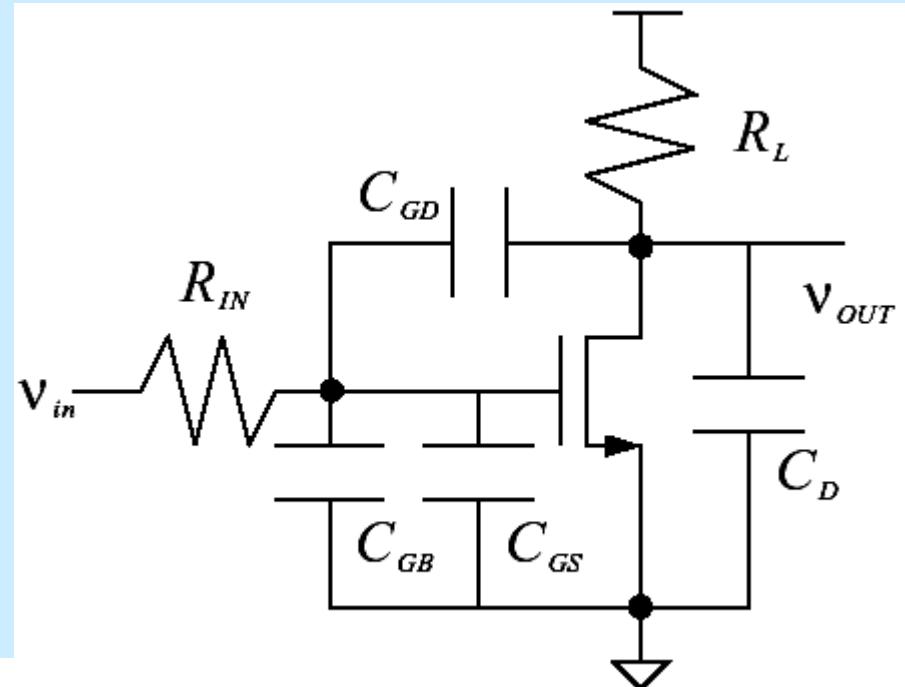
# Common Source


- $C_D$  can be ignored sometimes
- $R_{out} = R_L \parallel r_o$
- $C_G = C_{GB} + C_{GS}$


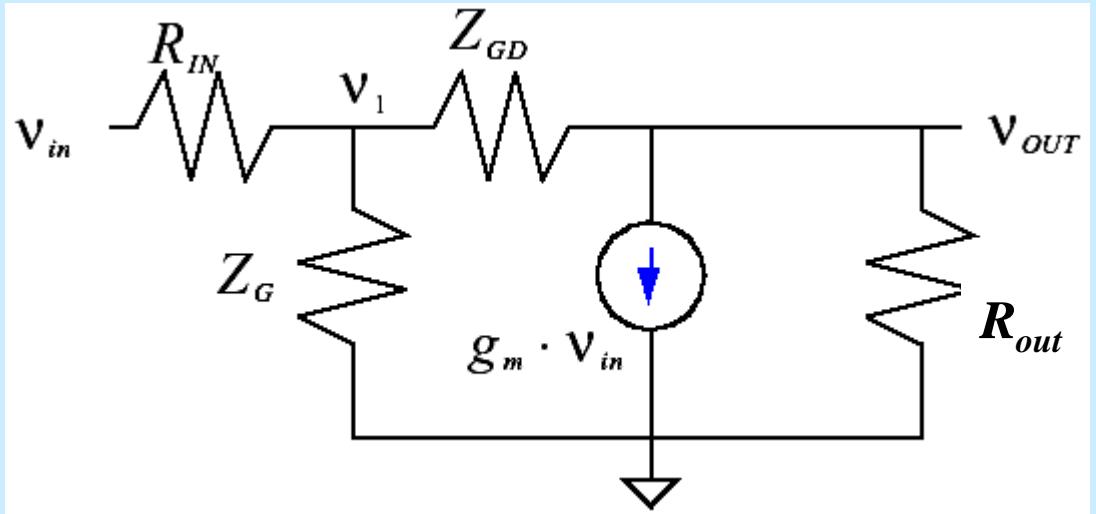
# Common source – small signal

- Using impedances

$$\frac{V_1 - V_{in}}{R_{in}} + \frac{V_1}{Z_G} + \frac{V_1 - V_{out}}{Z_{GD}} = 0$$



$$\frac{V_{out}}{V_{in}} = -g_m \bullet R_{out} \bullet \frac{1 - \frac{C_{GD}}{g_m}}{1 + j\omega \{ [C_{GD}(1 + g_m \bullet R_{out}) + C_G] \bullet R_{in} + R_L C_{GD} \} - \omega^2 R_{out} R_{in} C_G C_{GD}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 - j\omega \frac{C_{GD}}{g_m}}{\left(1 + j\frac{\omega}{\omega_{p1}}\right) \bullet \left(1 + j\frac{\omega}{\omega_{p2}}\right)} = \frac{1 - j\omega \frac{C_{GD}}{g_m}}{1 + j\omega \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) - \omega^2 \bullet \frac{1}{\omega_{p1}} \bullet \frac{1}{\omega_{p2}}}$$

# Common source - Poles and Zeros

- From the transfer function:

$$\omega_{p1} = -\frac{1}{R_{in} \bullet [C_{GD}(1 + g_m \bullet R_{out}) + C_G] + R_L C_{GD}}$$

$$\omega_{p2} = -\frac{1}{R_{out} C_{GD}} - \frac{1}{(R_{out} || R_{in} || \frac{1}{gm}) C_G}$$

$$\omega_z = \frac{g_m}{C_{GD}}$$


$$H(\omega) = \frac{\left(1 + j \frac{\omega}{\omega_z}\right)}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) + \left(1 + j \frac{\omega}{\omega_{p2}}\right)}$$

# Common source - Poles and Zeros



- Converting to s space:

$$S_z = -j\omega_z \quad S_{p1} = -j\omega_{p1} \quad S_{p2} = -j\omega_{p2}$$
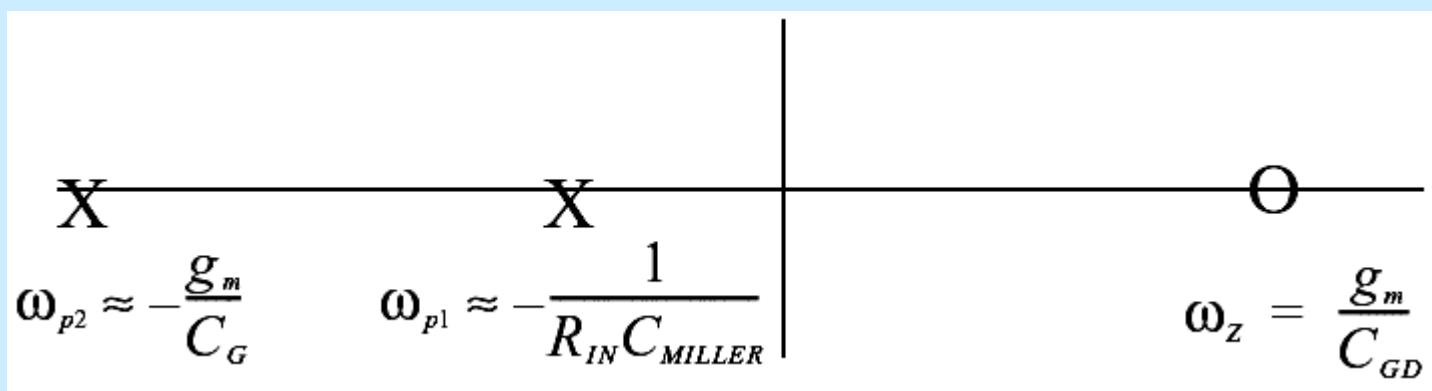
$$H(\omega) = \frac{\left(1 + j \frac{\omega}{\omega_z}\right)}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) + \left(1 + j \frac{\omega}{\omega_{p2}}\right)} \rightarrow H(s) = \frac{\left(1 - \frac{s}{s_z}\right)}{\left(1 - \frac{s}{s_{p1}}\right) + \left(1 - \frac{s}{s_{p2}}\right)}$$




# Diode connected and Pole Splitting

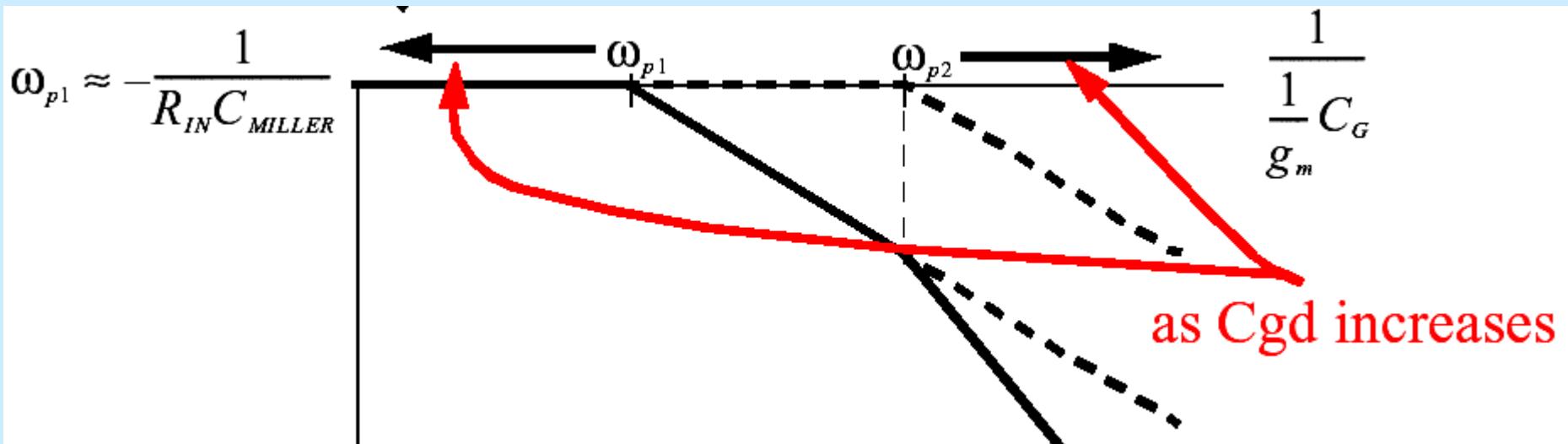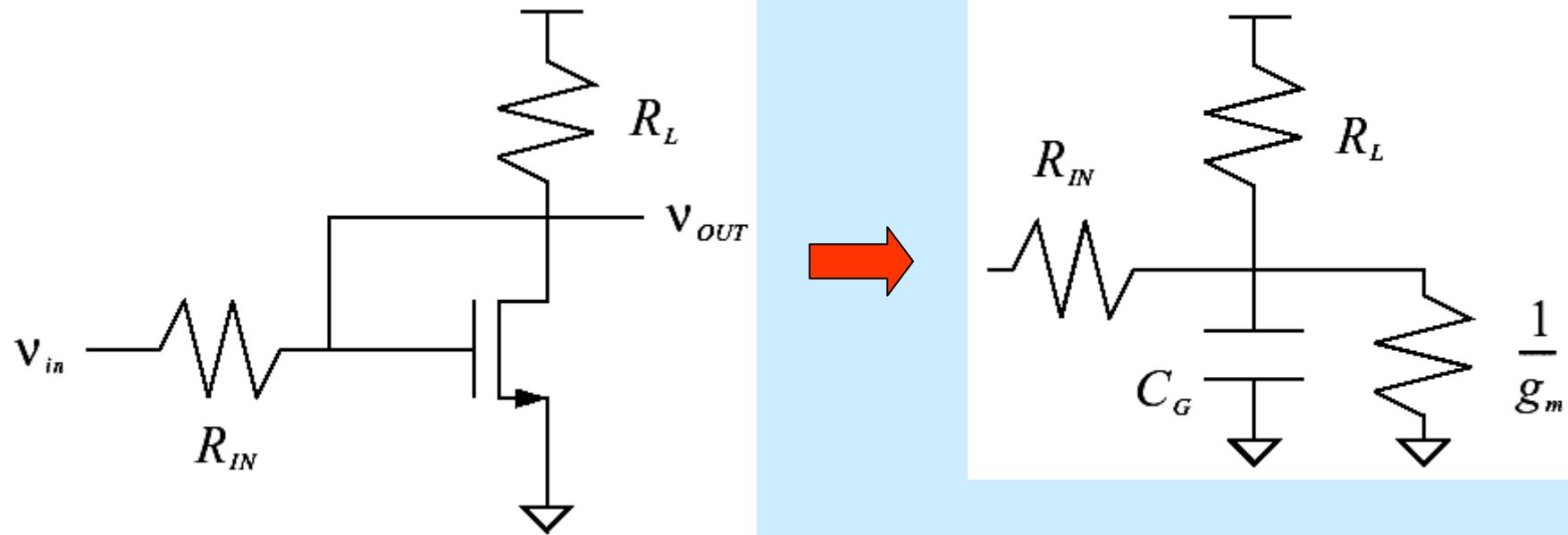
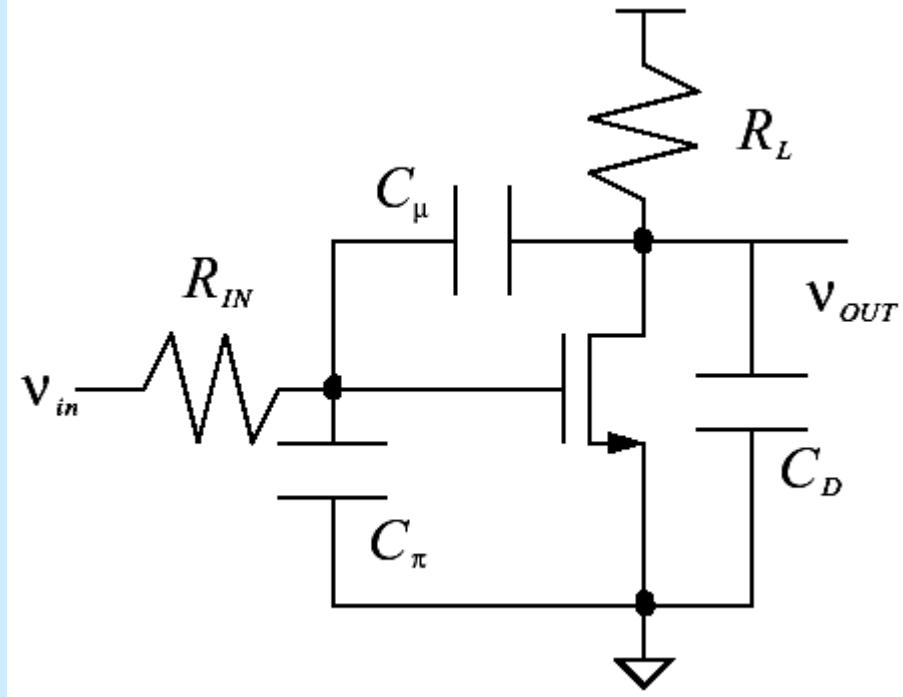
# Common source – Capacitance Cases

- Relative magnitude of the capacitors result in different scenarios
- Case1: Miller Cap small

$$R_{in}C_\pi, R_{out}C_D \gg R_{in}C_{Miller}$$




$$\omega_{p1} = \frac{1}{R_{in}C_\pi} \quad \omega_{p2} = \frac{1}{R_{out}C_D}$$

$$R_{out} = R_L || r_o$$
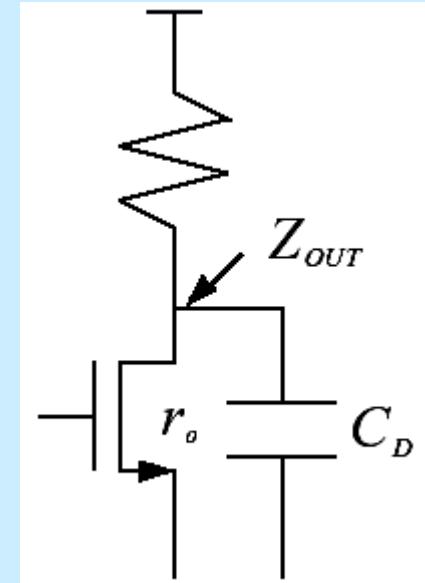
# Common source – Small Miller capacitance

- Output Impedance,  $Z_{out}$

$$Z_{out} = R_L \parallel r_o \parallel \frac{1}{j\omega C_D} = R_{out} \parallel \frac{1}{j\omega C_D}$$



- Stage gain,  $A_v$

$$A_v = -g_m \bullet Z_{out} = -g_m \bullet \frac{\frac{R_{out}}{j\omega C_D}}{R_{out} + \frac{1}{j\omega C_D}} = \frac{R_{out}}{1 + j\omega R_{out} C_D}$$


- Output pole

$$\omega_p = \frac{1}{R_{out} C_D}$$
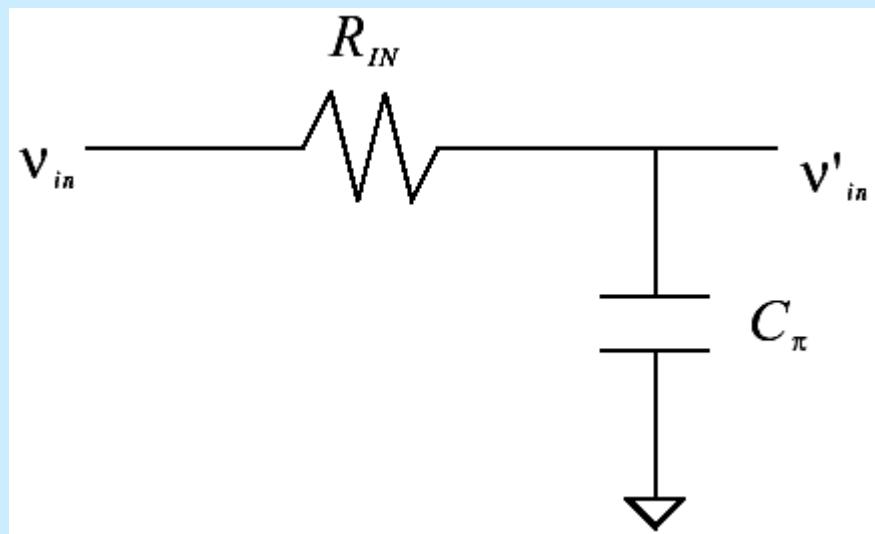
# Common source – Small Miller capacitance

- Input transfer function

$$\frac{V'_{in}}{V_{in}} = \frac{\frac{1}{j\omega C_\pi}}{R_{in} + \frac{1}{j\omega C_\pi}} = \frac{1}{1 + j\omega R_{in} C_\pi}$$



- Input pole

$$\omega_p = \frac{1}{R_{in} C_\pi}$$

## Common source - Other cases

- Case 2: Large  $C_D$

$$R_{out}C_D \gg R_{in}C_{Miller}, R_{in}C_\pi$$

$$\omega_{p1} = \frac{1}{R_{out}C_D}$$

$$\omega_{p2} = \frac{1}{R_{in}(C_\pi + C_\mu)}$$

- Case 3: Large  $C_\mu$

$$R_{in}C_{Miller} \gg R_{out}C_D, R_{in}C_\pi$$


$$\omega_{p1} = \frac{1}{R_{in} \underbrace{(1 + g_m R_{out})}_{C_{Miller}} C_\mu}$$

$$\omega_{p2} = \frac{1}{\frac{1}{g_m} (C_\pi + C_D)} = \frac{g_m}{(C_\pi + C_D)}$$
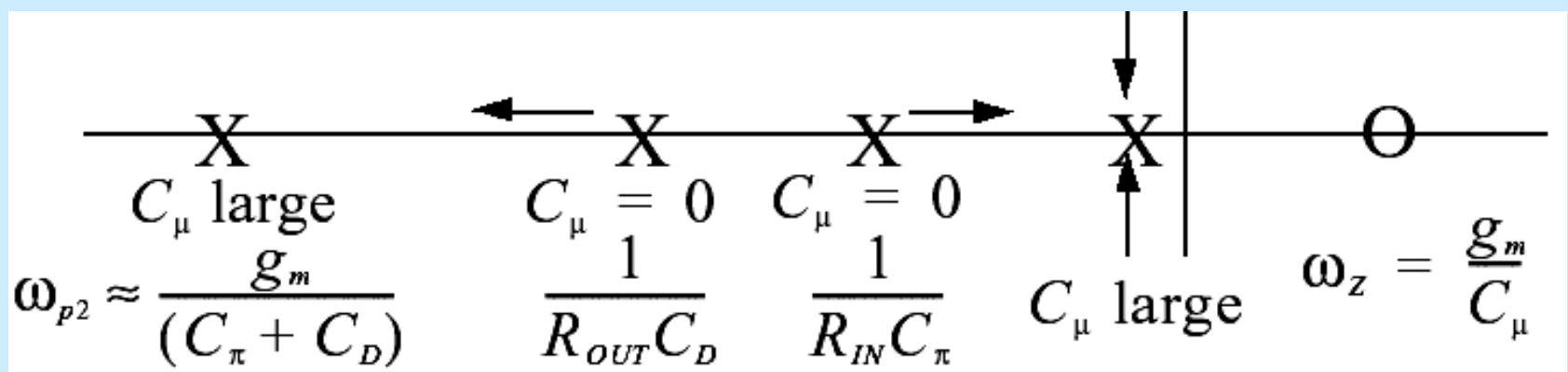
# Poles and Zeros

- Usually the multiplying factor on the Miller capacitor results in poles far apart from each other than in other cases.
- The pole splitting is used to compensate the circuit.


$$\omega_{p1} \approx \frac{1}{R_{in} C_{MILLER}}$$


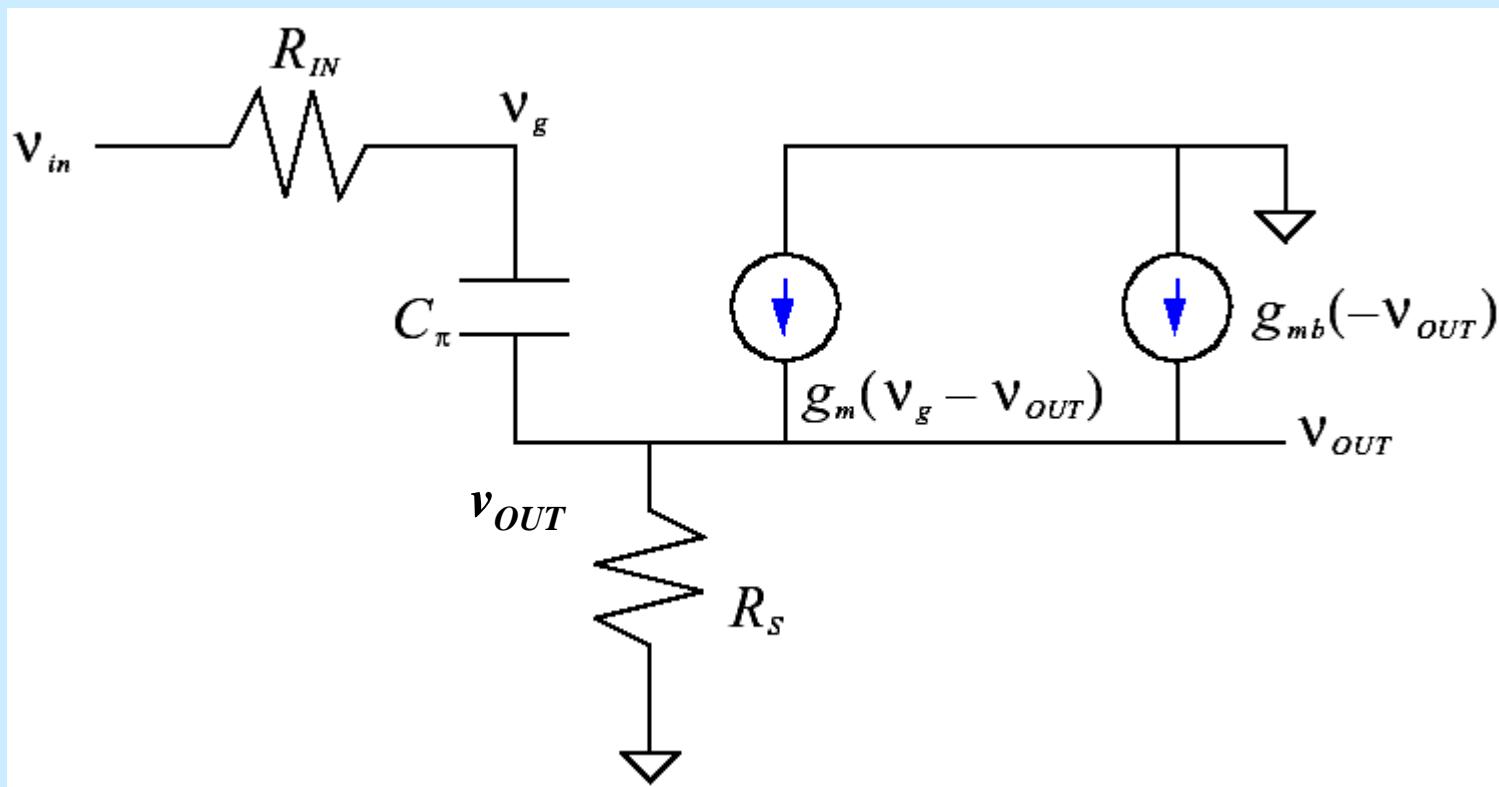
# Common drain (source follower)

- Small circuit analysis

$$v_g = \left( \frac{1}{1 + j\omega R_{in} C_\pi} \right) \bullet (v_{in} - v_{out}) + v_{out}$$



# Common drain – Small signal analysis

$$\frac{V_{out}}{R_s} = \frac{\frac{V_g - V_{out}}{1 + j\omega C_\pi} + g_m \cdot V_g - (1 + \chi) \cdot g_m \cdot V_{out}}{j\omega C_\pi}$$


$$V_{out} \cdot \left( \frac{1}{R_s} + (1 + \chi) \cdot g_m + j\omega C_\pi \right) = (j\omega C_\pi + g_m) \cdot V_g$$

$$\frac{V_{out}}{R_s} = \frac{g_m R_s}{1 + (1 + \chi) \cdot g_m R_s} \cdot \frac{\left( 1 + j\omega \frac{C_\pi}{g_m} \right)}{1 + j\omega R_{in} C_\pi \cdot \frac{1 + \chi \cdot g_m R_s}{1 + (1 + \chi) \cdot g_m R_s}}$$

$$\omega_z = \frac{g_m}{C_\pi} \quad \omega_{p1} = \frac{1}{R_{in} C_\pi (1 - A)} \quad A = \frac{g_m R_s}{1 + (1 + \chi) g_m R_s}$$
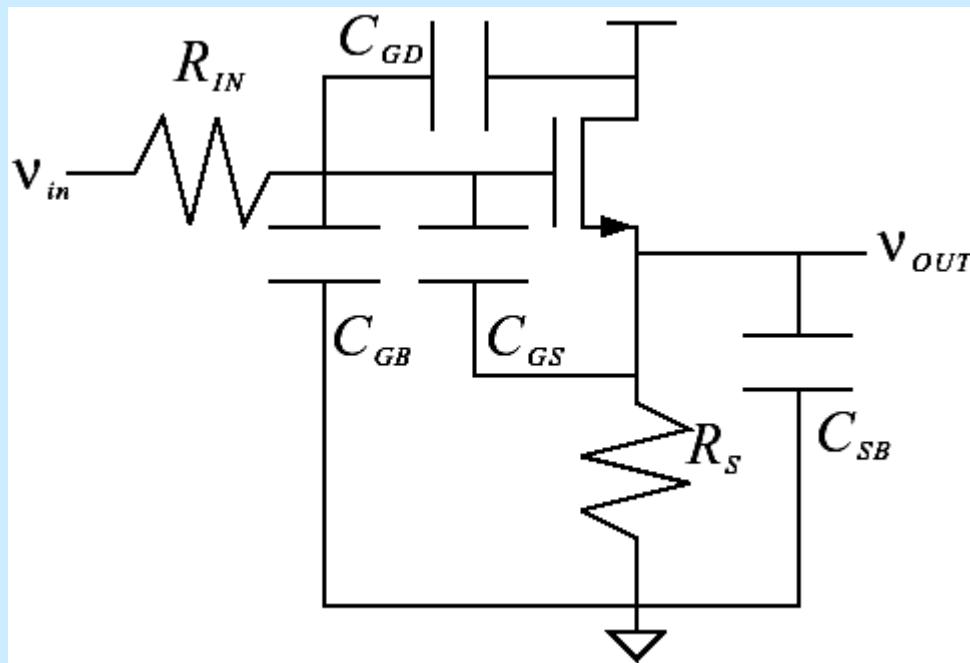
# Common drain (source follower)


- Effect of  $C_{SB}$
- The Body is Grounded


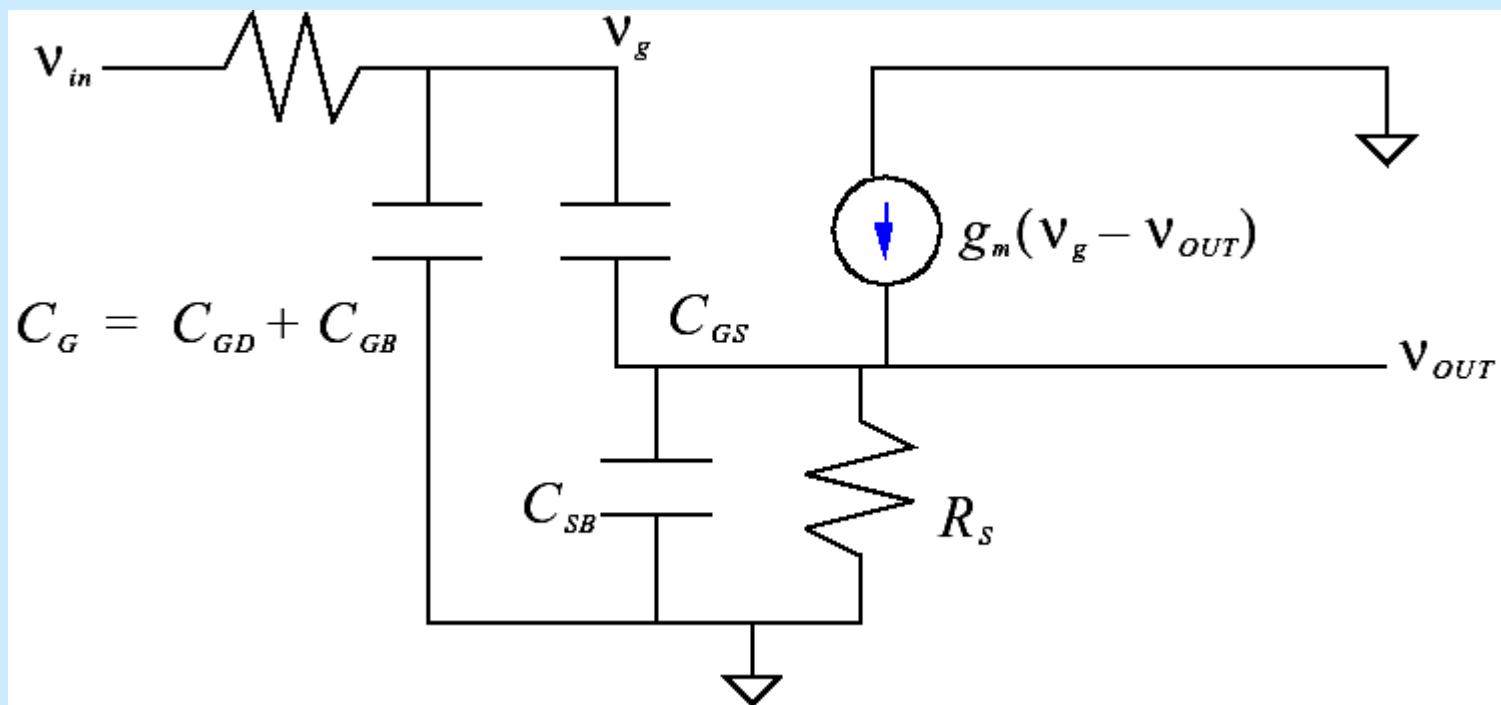
# Common drain – small signal

$$\frac{V_{in} - V_g}{R_{in}} = V_g \bullet j \omega C_G + (V_g - V_{out}) \bullet j \omega C_{GS}$$

$$(V_g - V_{out}) \bullet j \omega C_{GS} - g_m \bullet (V_g - V_{out}) = \frac{V_{out}}{R_s} + V_{out} \bullet j \omega C_{SB}$$



# Common drain – Small signal analysis

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\frac{g_m R_s}{1 + g_m R_s} \bullet \left(1 + j \omega \frac{C_{GS}}{g_m}\right)}{1 + j \omega \left[R_{\text{in}} C_G + \frac{R_{\text{in}} C_{GS}}{1 + g_m R_s} + \frac{R_s (C_{GS} + C_{SB})}{1 + g_m R_s}\right] - \omega^2 R_s R_{\text{in}} \left[\frac{C_{GS} C_G + C_{SB} (C_G + C_{GS})}{1 + g_m R_s}\right]}$$

- Having the denominator to be in the format:

$$\left(1 + j \frac{\omega}{\omega_{p1}}\right) \bullet \left(1 + j \frac{\omega}{\omega_{p2}}\right) = 1 + j \omega \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) - \frac{\omega^2}{\omega_{p1} \omega_{p2}}$$

- The poles are:

$$\omega_{p1} = \frac{1}{R_{\text{in}} C_G + \frac{R_{\text{in}} C_{GS}}{1 + g_m R_s} + \frac{R_s (C_{GS} + C_{SB})}{1 + g_m R_s}} = \frac{1}{R_{\text{in}} C_G + \frac{R_{\text{in}} C_{GS}}{1 + g_m R_s} + R_O (C_{GS} + C_{SB})}$$

$$\omega_{p2} = \frac{R_{\text{in}} C_G + \frac{R_{\text{in}} C_{GS}}{1 + g_m R_s} + R_O (C_{GS} + C_{SB})}{R_O R_{\text{in}} [C_{GS} C_G + C_{SB} C_G + C_{SB} C_{GS}]}$$

$$R_O = \frac{1}{g_m} || R_s$$

# Common drain - Cases


- Case 1:  $R_{in} \left( C_G + \frac{C_{GS}}{1 + g_m R_s} \right) \gg R_o (C_{GS} + C_{SB})$

$$\omega_{p1} = \frac{1}{R_{in} \left( C_G + \frac{C_{GS}}{1 + g_m R_s} \right)} \quad A = \frac{g_m R_s}{1 + g_m R_s} \quad C_{Miller} = C_{GS} \bullet (1 - A)$$


- Case 2:  $R_o (C_{GS} + C_{SB}) \gg R_{in} \left( C_G + \frac{C_{GS}}{1 + g_m R_s} \right)$

$$\omega_{p1} = \frac{1}{R_o (C_{GS} + C_{SB})}$$

# Common Gate

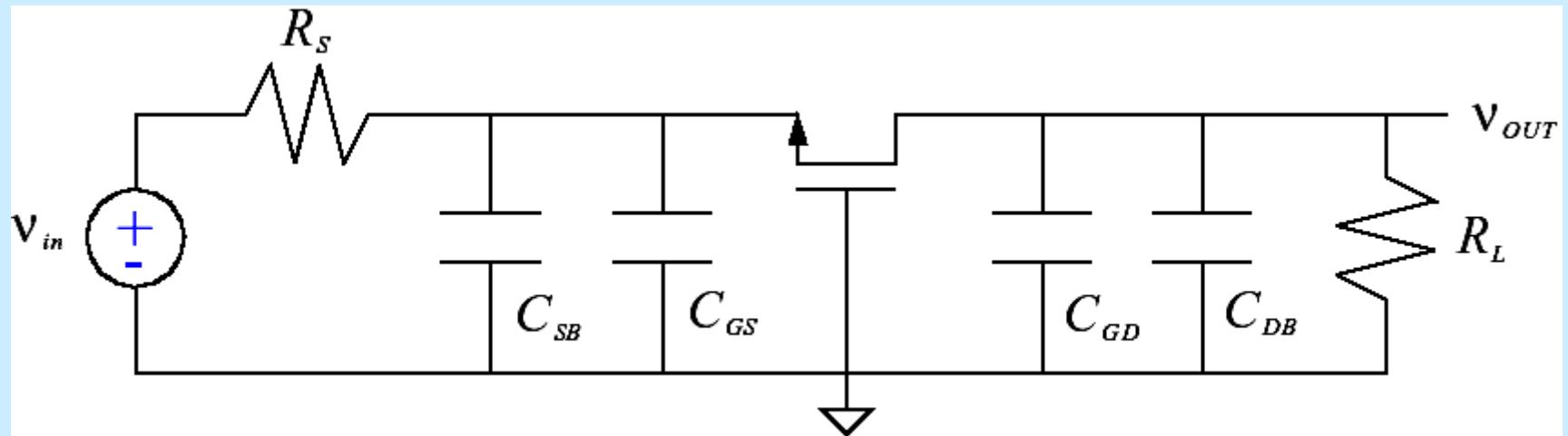

- Assuming  $r_o \rightarrow \infty$

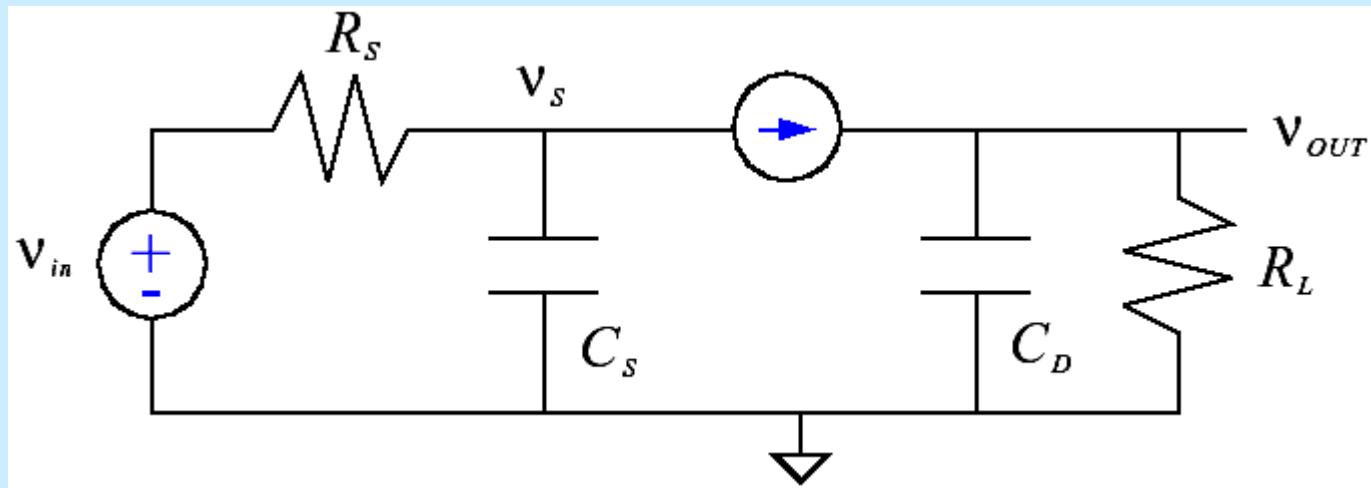

# Common gate - small signal

- Using KCL @  $v_s$  and @  $v_{out}$

$$\frac{V_{in} - V_s}{R_s} = v_s \bullet j\omega C_s + g_m v_s$$

$$g_m v_s = v_{out} \bullet j\omega C_D + \frac{V_{out}}{R_L}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{g_m R_L}{1 + g_m R_s}}{(1 + j\omega R_L C_D) \bullet \left( 1 + j\omega \frac{R_s C_s}{1 + g_m R_s} \right)}$$

- No Zeros

$$\omega_{p1} = \frac{1}{R_L C_D}$$

$$\omega_{p2} = \frac{1}{\frac{R_s}{1 + g_m R_s} C_s} = \frac{1}{\left( R_s || \frac{1}{g_m} \right) C_s}$$