

ECEN474: (Analog) VLSI Circuit Design

Fall 2012

Lecture 5: Layout Techniques



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements


- HW1 due today at 5PM
 - For grad students, confirm that you participated in the Analog IC Design Olympics on the first page of your homework 1 solution
 - Turn into my mailbox in WERC 315
- Exam 1 on Wednesday Sep. 26
 - Previous semester exams posted on website
 - One double-sided 8.5x11 notes page allowed
 - Bring your calculator

Agenda

- MOS Fabrication Sequence
- CMOS Design Rules
- Layout Techniques
- Layout Examples

- Reference Material
 - Razavi Chapter 17 & 18

 Fundamentals on Layout Techniques: N-Well CMOS Technologies



Substrate is always connected to the most negative voltage, and is shared by all N-type transistors


MOS Fabrication Sequence

[Razavi]




p -substrate

(a)

 


p -substrate

(b)

 

p -substrate

(c)

 


p -substrate


(d)

MOS Fabrication Sequence


[Razavi]

 


(e)

 

(f)

 


(g)

 

(h)

MOS Fabrication Sequence


[Razavi]

 

"Front-End"


"Back-End"

 - A "silicide" step, where highly conductive metal is deposited on the gate and diffusion regions, reduces transistor terminal resistance
- To prevent potential gate-source/drain shorting an "oxide spacer" is first formed before silicide deposition



Contact and Metal Fabrication


[Razavi]

 

(a)




(b)

 

(c)

Transistor Geometries


- λ -based design rules allow a process and feature size-independent way of setting mask dimensions to scale
 - Due to complexity of modern processing, not used often today
- Minimum drawing feature = λ
 - Assume w.c. mask alignment $< 0.75\lambda$
 - Relative misalignment between 2 masks is $< 1.5\lambda$
$$AGate = W * L$$
$$AD, AS = W * X$$
$$PS, PS = W + 2X \text{ (3 sides)}$$
- X depends on contact size
 - 5λ in this example

 


BASIC SCNA CMOS LAYERS

| Physical Layer |
|----------------------------------|
| N-well |
| Silicon Nitride |
| Polysilicon Layer 1 |
| Polysilicon Layer 2 |
| P+ Ion Implant |
| N+ Ion Implant |
| Contact cut to n+/p ₋ |
| Metal 1 |
| Via Oxide Cuts |
| Metal 2 |
| Pad Contact (Overglass) |


P-channel MOSFET

 


N-channel MOSFET

 


Design Rule Basics

 

Minimum width and spacing

 


(a) Mask definition

 


(b) After annealing


Patterning sequence for a doped n+ line.

 

 Depletion regions due to parallel n+ lines




(a) Contact size

 


(b) Side view

Geometry of a contact cut

 


(a) Masking Design

 


(b) Registration tolerance


Contact spacing rule

 


Nselect

 

Active

 

p-Substrate

 


p-Substrate

(a) Correct mask sizing

 
(b) Incorrect mask sizing

Formation of n+ regions in an n-channel MOSFET



Gate spacing form an n+ edge


Gate overhang in MOSFET layout

 


(a) No overhang

(b) With misalignment


Effect of misalignment without overhang

 

(a) Resist pattern

 

(b) Isotropic etch

 


(c) anisotropic etch


Effect of misalignment without overhang

| Mask Number | Mask Layer |
|-------------|----------------|
| 1 | NWELL |
| 2 | ACTIVE |
| 3 | POLY |
| 4 | SELECT |
| 5 | POLY CONTACT |
| 6 | ACTIVE CONTACT |
| 7 | METAL1 |
| 8 | VIA |
| 9 | METAL2 |
| 10 | PAD |
| 11 | POLY2 |


Design Rule Layers

 

 
Difference between the drawn and physical values for channel length and the channel width



Structure of a n-channel MOSFET

 



Example of Layout Rules

 

Perspective view of an n-channel MOSFET



- Minimum transistor width is set by minimum diffusion width
 - 2 or 3λ (check with TA)
- Often, we use a use a slightly larger “minimum” that is equal to the contact height (4λ in this example)

N-channel MOSFET

 
 


(a) Cross section

P-channel MOSFET

  


(b) Circuit symbol

  


(c) Top view



Stick Diagrams

 

(a) Definitions


 


(b) MOSFET

  


Stick diagrams for the CMOS Inverter

The CMOS Inverter

  



Basic Inverter Layout

 



Alternate Inverter Layout

Standard Cells: VDD, VSS and output run in Parallel

CMOS NAND2 logic gate

 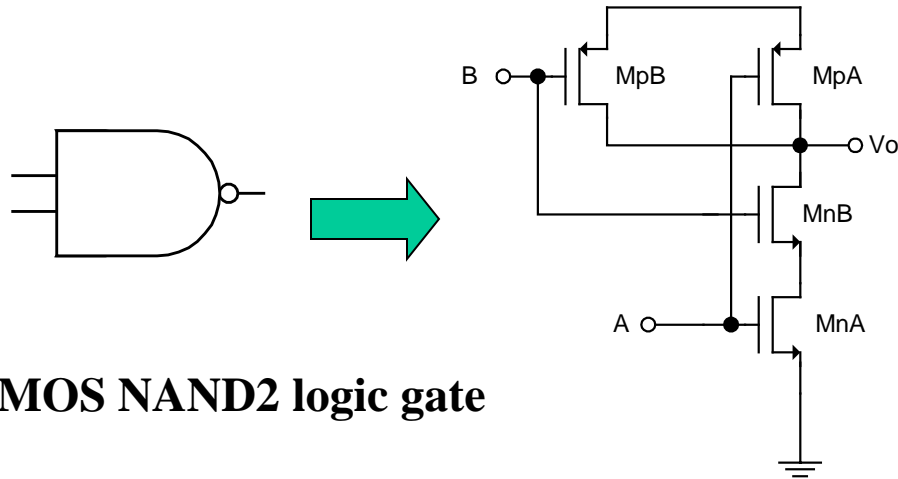



CMOS NOR2 logic gate

 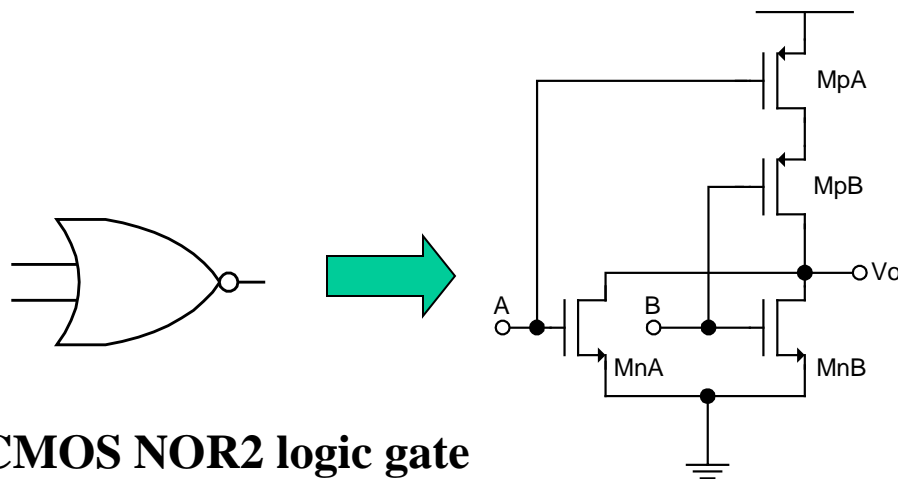


Wide Analog Transistor: Analog techniques

- Unacceptable drain and source resistance
- Stray resistances in transistor structure
- Contacts short the distributed resistance of diffused areas

  Most of the current will be shrunk to this side









Current is spread

 


Transistor orientation

      - Orientation is important in analog circuits for matching purposes



Stacked Transistors


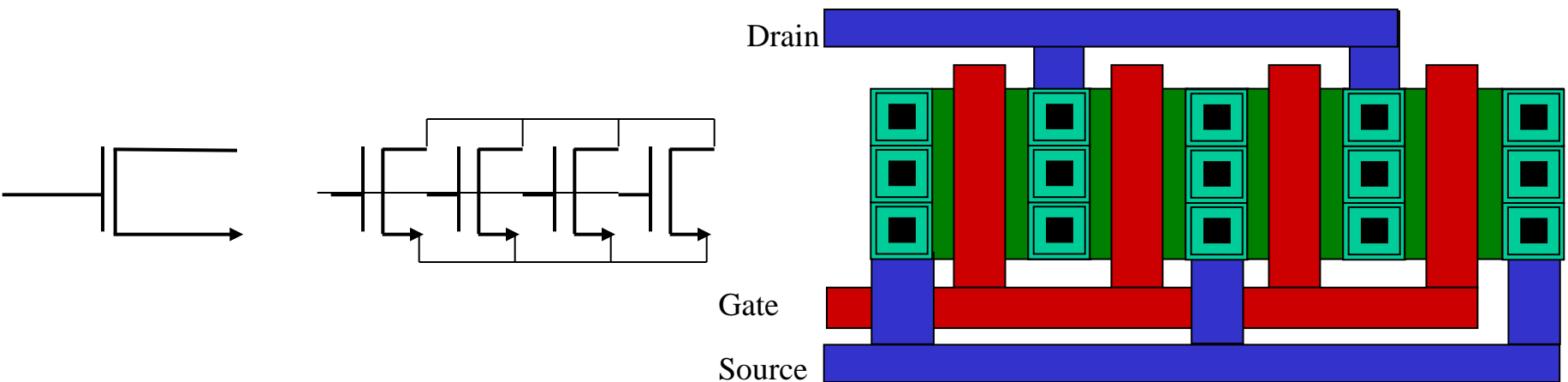
- Wide transistors need to be split
- Parallel connection of n elements ($n = 4$ for this example)
- Contact space is shared among transistors
- Parasitic capacitances are reduced (important for high speed)




Note that parasitic capacitors are lesser at the drain

Matched Transistors

  - Simple layouts are prone to process variations, e.g. V_T , K_P , C_{ox}
- Matched transistors require elaborated layout techniques




 Differential pair requiring “matched transistors”




Interdigitized Layout

 - Averages the process variations among transistors
- Common terminal is like a serpentine




Why Interdigitized?

 

- Process variations are averaged among transistors
 KPs for M1: $KP1+KP4+KP5+KP8$ M2: $KP2+KP3+KP6+KP7$
- Technique maybe good for matching dc conditions
- Uneven total drain area between M1 and M2. This is undesirable for ac conditions: capacitors and other parameters may not be equal
- A more robust approach is needed (**Use dummies if needed !!**)

 
A method of achieving good matching is shown in the following figure :



- Each transistor is split in four equal parts interleaved in two by two's. So that for one pair of pieces of the same transistor we have currents flowing in opposite direction.
- Transistors have the same source and drain area and perimeters, but this topology is more susceptible to gradients (not common centroid)

Common Centroid Layouts

Usually routing is more complex

 

CENTROID
(complex layout)

M1: 8 transistors

(0,3) (0,1)

(1,2) (1,0)

(2,3) (2,1)

(3,2) (3,0)

M2: 8 transistors

(0,2) (0,0)


(1,3) (1,1)

(2,2) (2,0)



(3,3) (3,1)

Common Centroid Layouts

 
- Split into parallel connections of even parts
- Half of them will have the drain at the right side and half at the left
- Be careful how you route the common terminal
- Cross talk (effect of distributed capacitors → RF applications)!



  - Many contacts placed close to one another reduces series resistance and make the surface of metal connection smoother than when we use only one contact; this prevents microcracks in metal;
- Splitting the transistor in a number of equal part connected in parallel reduces the area of each transistor and so reduces further the parasitic capacitances, but accuracy might be degraded!




Diffusion resistors

 


Diffused resistance

Diffused resistance

 

well resistance

 


Pinched n-well resistance

Integrated Resistors

- Highly resistive layers (p^+ , n^+ , well or polysilicon)
- R_{\square} defines the resistance of a square of the layer
- Accuracy less than 30%



Resistivity (volumetric
measure of material's
resistive characteristic)

$$\rho \text{ } (\Omega\text{-cm})$$

 

Sheet resistance (measure
of the resistance of a
uniform film with arbitrary
thickness t)

  
$$R_{\square} = \rho/t \text{ } (\Omega/\square)$$



$$R = 2R_{\text{contact}} + (L/W) R_{\square}$$

TYPICAL INTEGRATED RESISTORS
 
$$R = 2R_{\text{cont}} + \frac{L}{W} R_{\square}$$



| Type of layer | Sheet Resistance W/0 | Accuracy % | Temperature Coefficient ppm/°C | Voltage Coefficient ppm/V |
|------------------|----------------------|------------|--------------------------------|---------------------------|
| n + diff | 30 - 50 | 20 - 40 | 200 - 1K | 50 - 300 |
| p + diff | 50 - 150 | 20 - 40 | 200 - 1K | 50 - 300 |
| n - well | 2K - 4K | 15 - 30 | 5K | 10K |
| p - well | 3K - 6K | 15 - 30 | 5K | 10K |
| pinched n - well | 6K - 10K | 25 - 40 | 10K | 20K |
| pinched p - well | 9K - 13K | 25 - 40 | 10K | 20K |
| first poly | 20 - 40 | 25 - 40 | 500 - 1500 | 20 - 200 |
| second poly | 15 - 40 | 25 - 40 | 500 - 1500 | 20 - 200 |

Special poly sheet resistance for some analog processes might be as high as 1.2 KΩ/□


Large Resistors

In order to implement large resistors :

- Use of long strips (large L/W)
- Use of layers with high sheet resistance (bad performances)


Layout : rectangular “serpentine”
 
$$R = \frac{L}{W} R_{\square} = \frac{L}{W} \cdot \frac{\bar{\rho}}{x_j}$$



Well-Diffusion Resistor

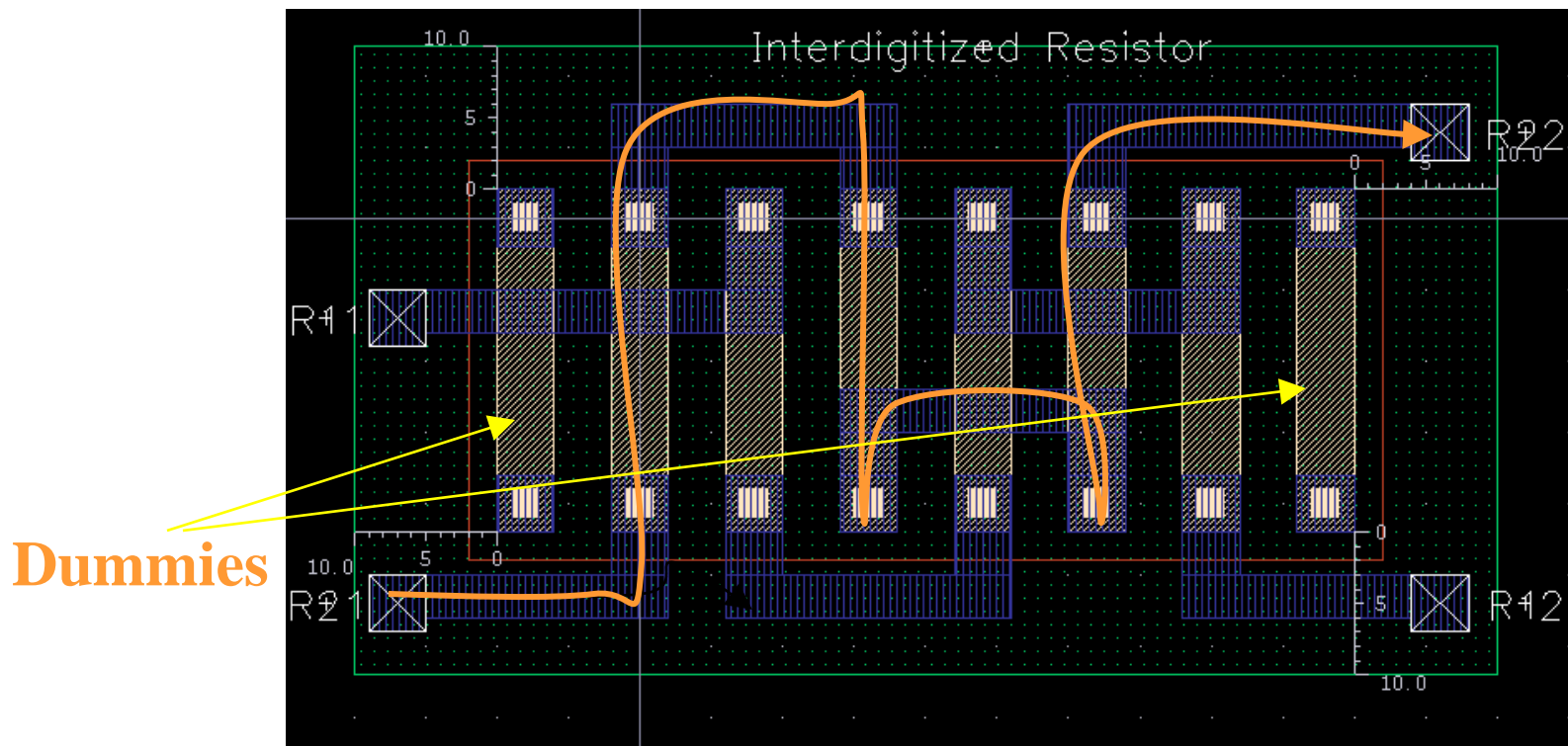- Example shows two long resistors for $K\Omega$ range
- Alternatively, “serpentine” shapes can be used
- Noise problems from the body
 - Substrate bias surrounding the well
 - Substrate bias between the parallel strips




Factors affecting accuracy :

Plastic packages cause a large pressure on the die (= 800 Atm.). It determines a variation of the resistivity.

For $\langle 100 \rangle$ material the variation is unisotropic, so the minimum is obtained if the resistance have a 45° orientation.

Temperature :

 Temperature gradient on the chip may produce thermal induced mismatch.



Etching


Wet etching : isotropic (undercut effect)

HF for SiO_2 ; H_3PO_4 for Al

Δx for polysilicon may be $0.2 - 0.4 \mu\text{m}$ with standard deviation $0.04 - 0.08 \mu\text{m}$.


Reactive ion etching (R.I.E.)(plasma etching associated to “bombardment”) : unisotropic.

 Δx for polysilicon is $0.05 \mu\text{m}$ with standard deviation $0.01 \mu\text{m}$




Boundary :

 The etching depends on the boundary conditions




- Use dummy strips

 Side diffusion effect : Contribution of endings




 Side Diffusion “widens” R
 R_{\square} is not constant with W




Impact of R_{cont} depends on relative geometry
 Best to always use a resistor W that is at least as large as the contact


Interdigitized structure :

 


Poly Resistors

 


e) **First polysilicon resistance**

 

 f) **First polysilicon resistance with a well shielding**



g) **Second polysilicon resistance**

 

h) **Second polysilicon resistance with a well shielding**


Typical Resistance Process Data

0.8 μm process

| | Sheet Resistance (Ω/\square) | Contact Resistance (Ω) |
|---------------|--|---------------------------------------|
| N+Actv | 52.2 | 66.8 |
| P+Actv | 75.6 | 37.5 |
| Poly | 36.3 | 30.6 |
| Poly 2 | 25.5 | 20.7 |
| Mtl 1 | 0.05 | 0.05 |
| Mtl 2 | 0.03 | |
| N-Well | 1513 | |

Gate oxide thickness 316 angstroms


TYPES OF INTEGRATED CAPACITORS

 

Electrodes : metal; polysilicon; diffusion

Insulator : silicon oxide; polysilicon oxide; CVD oxide

$$C = \frac{\epsilon_{ox}}{t_{ox}} WL$$

 

TOP VIEW

$$\left(\frac{\Delta C}{C}\right)^2 = \left(\frac{\Delta \epsilon_r}{\epsilon_r}\right)^2 + \left(\frac{\Delta t_{ox}}{t_{ox}}\right)^2 + \left(\frac{\Delta L}{L}\right)^2 + \left(\frac{\Delta W}{W}\right)^2$$

Factor affecting relative accuracy/matching

- Oxide damage
- Impurities
- Bias condition
- Bias history (for CVD)
- Stress
- Temperature

$$\left(\frac{\Delta \epsilon_{\text{ox}}}{\epsilon_{\text{ox}}} \right)$$

- Grow rate
- Poly grain size

$$\left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}} \right)$$

- Etching
- Alignment


$$\left(\frac{\Delta L}{L} \right); \left(\frac{\Delta W}{W} \right)$$

$$\frac{\Delta C}{C} \approx 1 - 0.1\%$$

$$\left(\frac{\Delta C}{C} \right)^2 = \left(\frac{\Delta \epsilon_r}{\epsilon_r} \right)^2 + \left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}} \right)^2 + \left(\frac{\Delta L}{L} \right)^2 + \left(\frac{\Delta W}{W} \right)^2$$


Note, the absolute C may vary as high as 20% due to process variations

Poly1 - Poly2 Capacitor

 

Poly 2

Poly 1

 

- Area is determined by poly2
- Problems
 - undercut effects
 - nonuniform dielectric thickness
 - matching among capacitors
 - Minimize the rings (inductors)

Accuracy of integrated capacitors

Perimeter effects led the total capacitance:

$$C = C_A A$$

$$A = (x - 2\Delta x)(y - 2\Delta y)$$

$$= (xy - 2x\Delta y - 2y\Delta x - 4\Delta x \Delta y)$$

Assuming that $\Delta x = \Delta y = \Delta e$

$$A = (xy - 2\Delta e(x + y) - 4\Delta^2 e)$$

$$A \approx xy - 2\Delta e(x + y)$$

$$\therefore C_e = -2\Delta e(x + y)$$


The relative error is

$$\varepsilon = C_e / C$$

$$= -2\Delta e(x + y) / xy$$


Then maximize the area and minimize the perimeter → use squares!!!

C_A = capacitance per unit area

 



Common Centroid Capacitor Layout

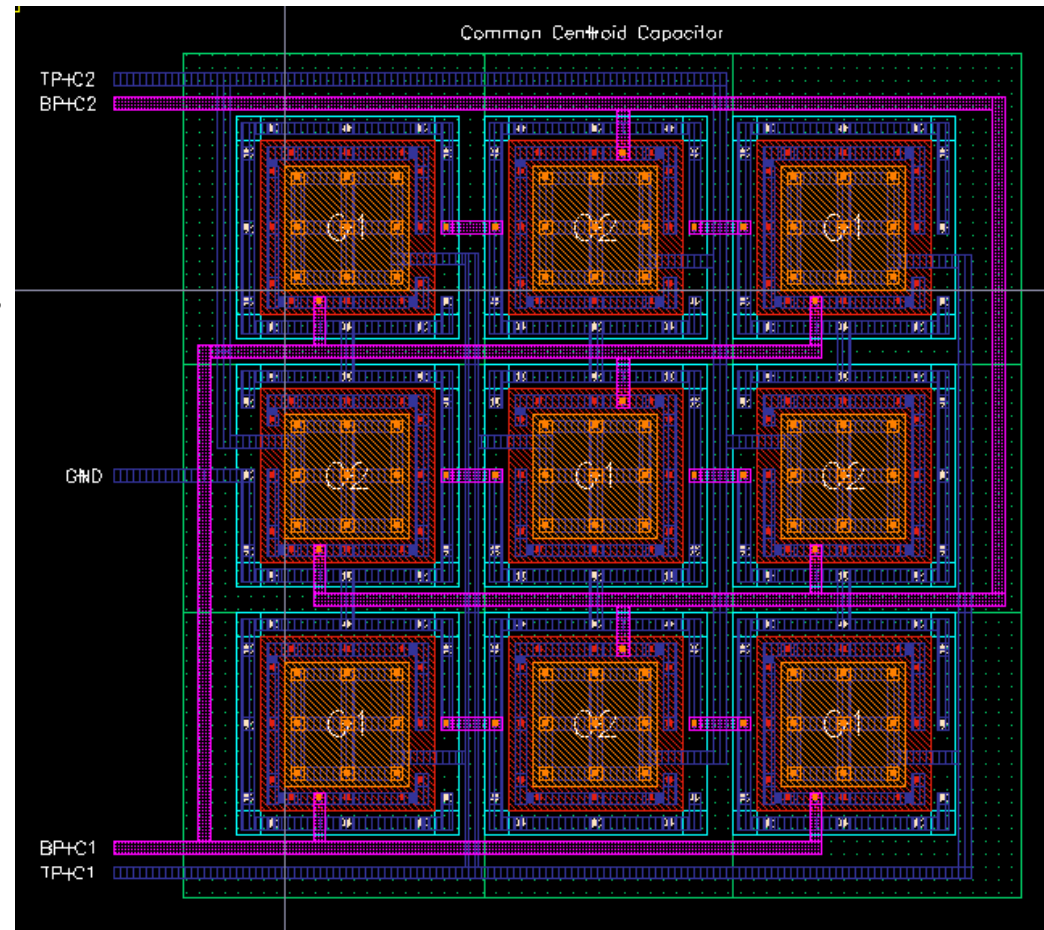- Unit capacitors are connected in parallel to form a larger capacitance
- Typically the ratio among capacitors is what matters
- The error in one capacitor is proportional to perimeter-area ratio
- Use dummies for better matching (See Johns & Martin Book, page 112)



Common centroid structures

Jose Silva-Martinez

  


$$\begin{aligned} C_2 &= C_1 \\ C_3 &= 2C_1 \\ C_4 &= 4C_1 \\ C_5 &= 8C_1 \end{aligned}$$


“Floating” Capacitors

Be aware of **parasitic capacitors**

 
Polysilicon-Polysilicon: Bottom plate capacitance is comparable (10-30 %) with the poly-poly capacitance



 → **Metal1-Metal2:** More clean, but the capacitance per micrometer square is smaller. Good option for very high frequency applications ($C \sim 0.1$ - 0.3 pF).



 $CP1$, $CP2''$ are very small (1-5 % of $C1$)
 $CP2'$ is around 10-50 % of $C1$



$CP2$ is very small (1-5 % of $C1$)

Typical Capacitance Process Data (See MOSIS webside for the AMI 0.6 CMOS process)

| Capacitance | N+Actv | P+Actv | Poly | Poly 2 | Mtl 1 | Mtl 2 | UNITS |
|--------------------|--------|--------|------|--------|-------|-------|---------------------|
| Area (substrate) | 292 | 290 | 35 | | 20 | 13 | aF/ μm^2 |
| Area (N+active) | | | 1091 | 684 | 49 | 26 | aF/ μm^2 |
| Area (P+active) | | | 1072 | 677 | | | aF/ μm^2 |
| Area (poly) | | | | 599 | 45 | 23 | aF/ μm^2 |
| Area (poly2) | | | 900 | | 45 | | aF/ μm^2 |
| Area (metal1) | | | | | | 42 | aF/ μm^2 |
| Fringe (substrate) | 80 | 170 | | | 36 | 25 | aF/ μm |
| Fringe (poly) | | | | | 59 | 39 | aF/ μm |


$$a=10^{-18}, f=10^{-15}, p=10^{-12}, n=10^{-9}, \mu=10^{-6}, m=10^{-3}$$

Stacked Layout for Analog Cells


- ➡ Stack of elements with the same width
- ➡ Transistors with even number of parts have the source (drain) on both sides of the stack
- ➡ Transistors with odd number of parts have the source on one end and the drain on the other. *If matching is critical use dummies*
- ➡ If different transistors share a same node they can be combined in the same stack to share the area of the same node (*less parasitics*)
- ➡ Use superimposed or side by side stacks to integrate the cell

Bipolar Transistors – Latchup

[Razavi]

 

Equivalent Circuit

 


- Potential for parasitic BJTs (Vertical PNP and Lateral NPN) to form a positive feedback loop circuit
- If circuit is triggered, due to current injected into substrate, then a large current can be drawn through the circuit and cause damage
- Important to minimize substrate and well resistance with many contacts/guard rings


Analog Cell Layout


- Use transistors with the same orientation
- Minimize S/D contact area by stacking transistors (to reduce parasitic capacitance to substrate)
- Respect symmetries
- Use low resistive paths when current needs to be carried (to avoid parasitic voltage drops)
- Shield critical nodes (to avoid undesired noise injection)
- Include guard rings everywhere; e.g. Substrate/well should not have regions larger than 50 μm without guard protections (latchup issues)

- ## Not the best floorplan

 

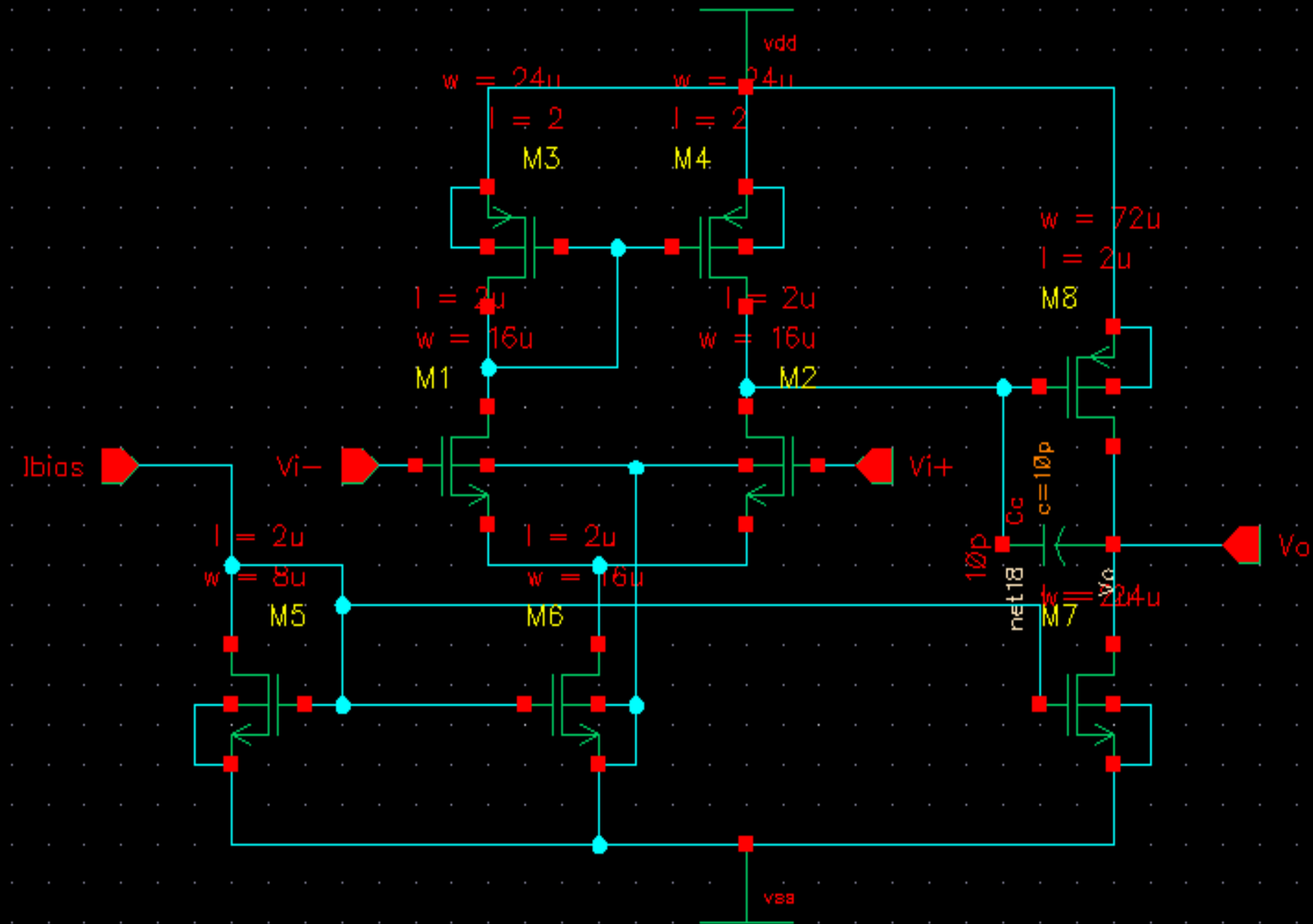Pay attention to your floor plan! It is critical for minimizing iterations: Identify the critical elements



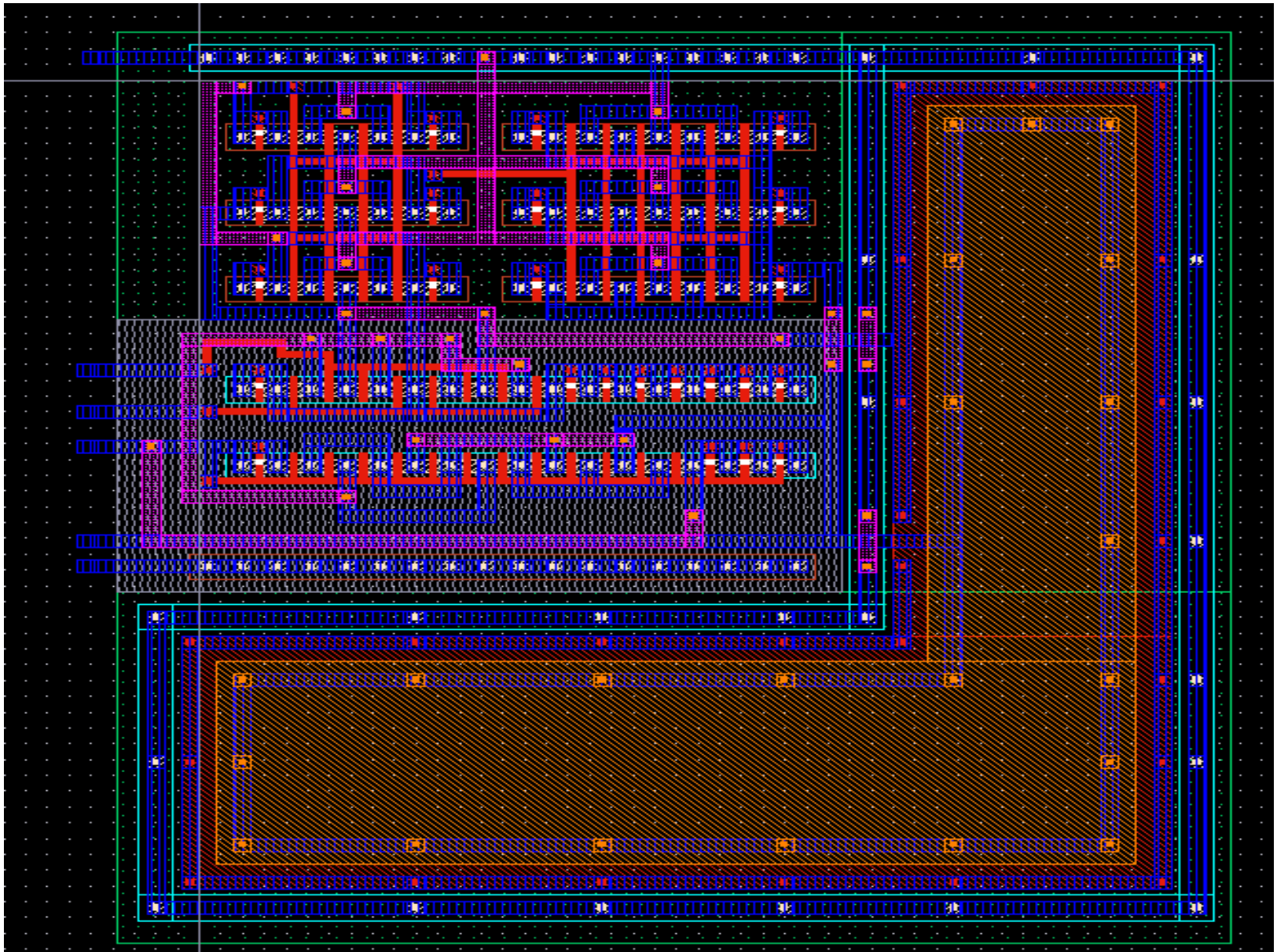

Layout (of something we should not do) example (cap related)⁵²

Following slides were provided by some of Dr. Silva's graduate students.

Special thanks to Fabian Silva-Rivas, Venkata Gadde, Marvin Onabajo, Cho-Ying Lu, Raghavendra Kulkarni and Jusung Kim

 


Figure: Layout of a single stage fully differential amplifier and its CMFB circuit.

1. I/p NMOS diff pair 2. PMOS (Interdigitated) 3. Resistors for V_{CM} 4. Capacitors (Common centroid)

Resistive network

Capacitive network
(Common centroid)

Fully differential
amplifier



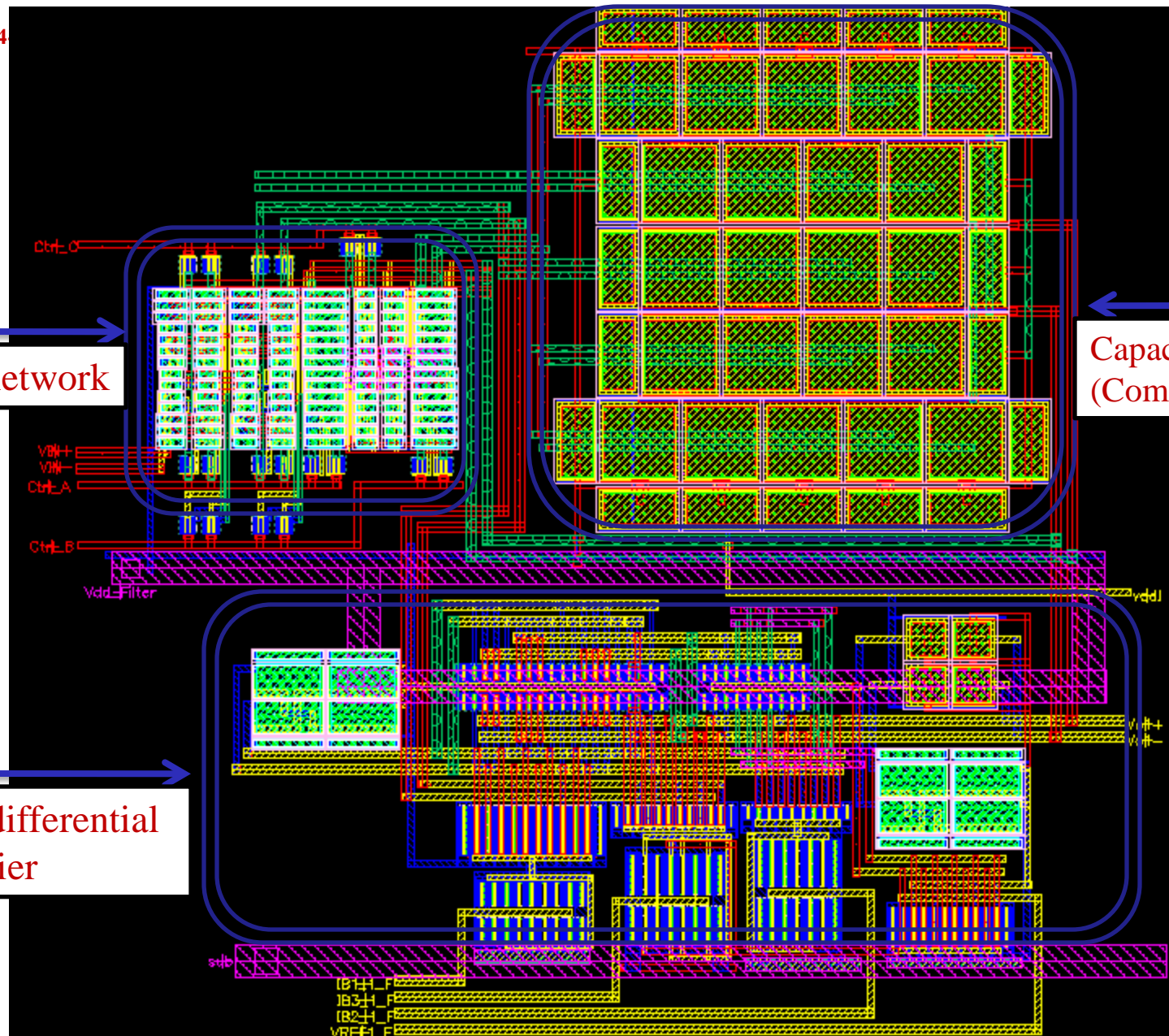



Figure: Layout of a second order Active RC low-pass Filter (Bi-quad)

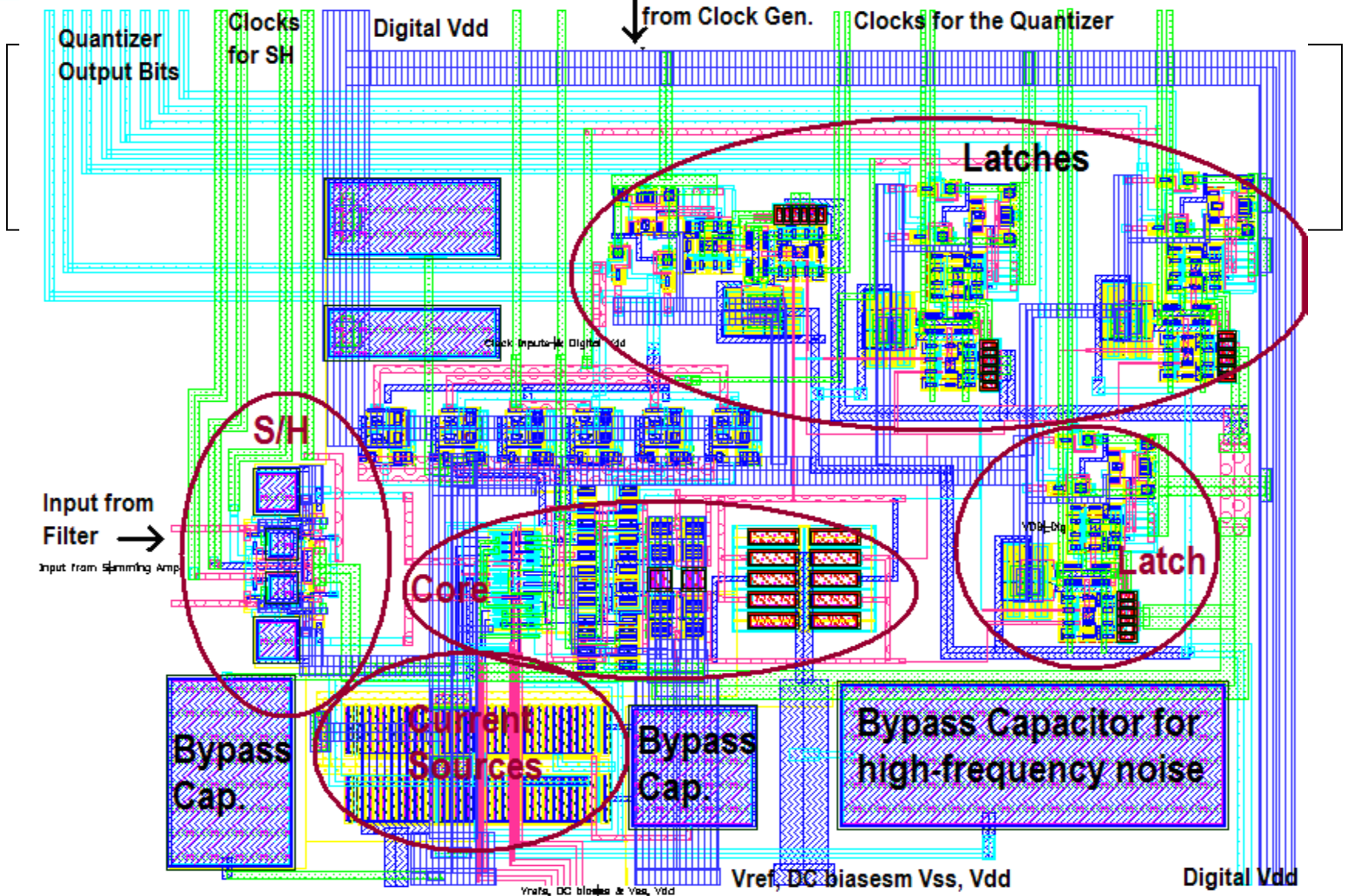

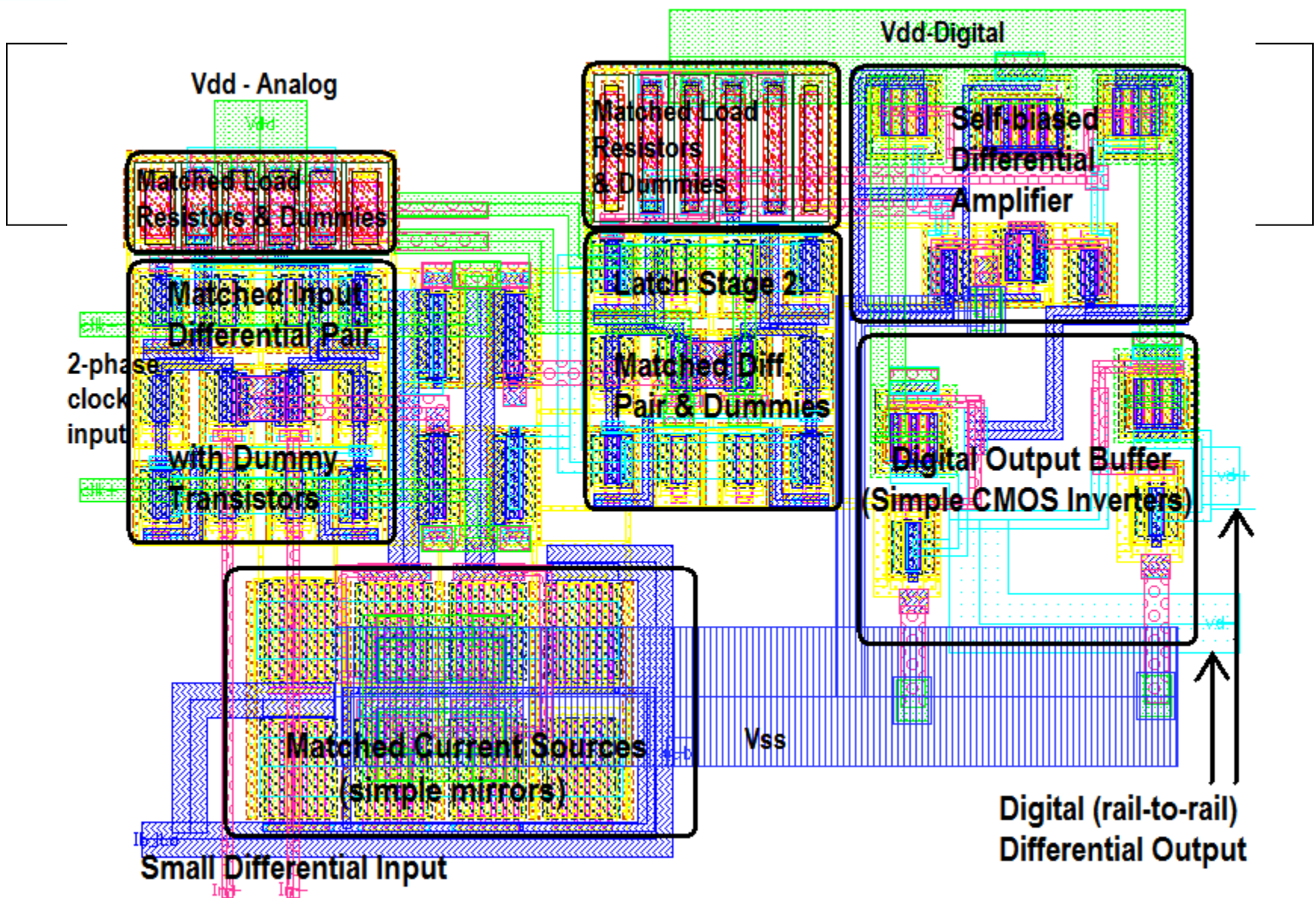- **3-bit quantizer in Jazz 0.18 μ m CMOS technology**
- S/H: sample-and-hold circuit that is used to sample the continuous-input signal
- Core: contains matched differential pairs and resistors to create accurate reference levels for the analog-to-digital conversion
- Latches: store the output bits; provide interface to digital circuitry with rail-to-rail voltage levels




- **High-speed D-Flip-Flop in Jazz 0.18 μm CMOS technology**
- Resolves a small differential input with $10\text{mV} < V_{p-p} < 150\text{mV}$ in less than 360ps
- Provides digital output (differential, rail-to-rail) clocked at 400MHz
- The sensitive input stage (1st differential pair) has a separate “analog” supply line to isolate it from the noise on the supply line caused by switching of digital circuitry

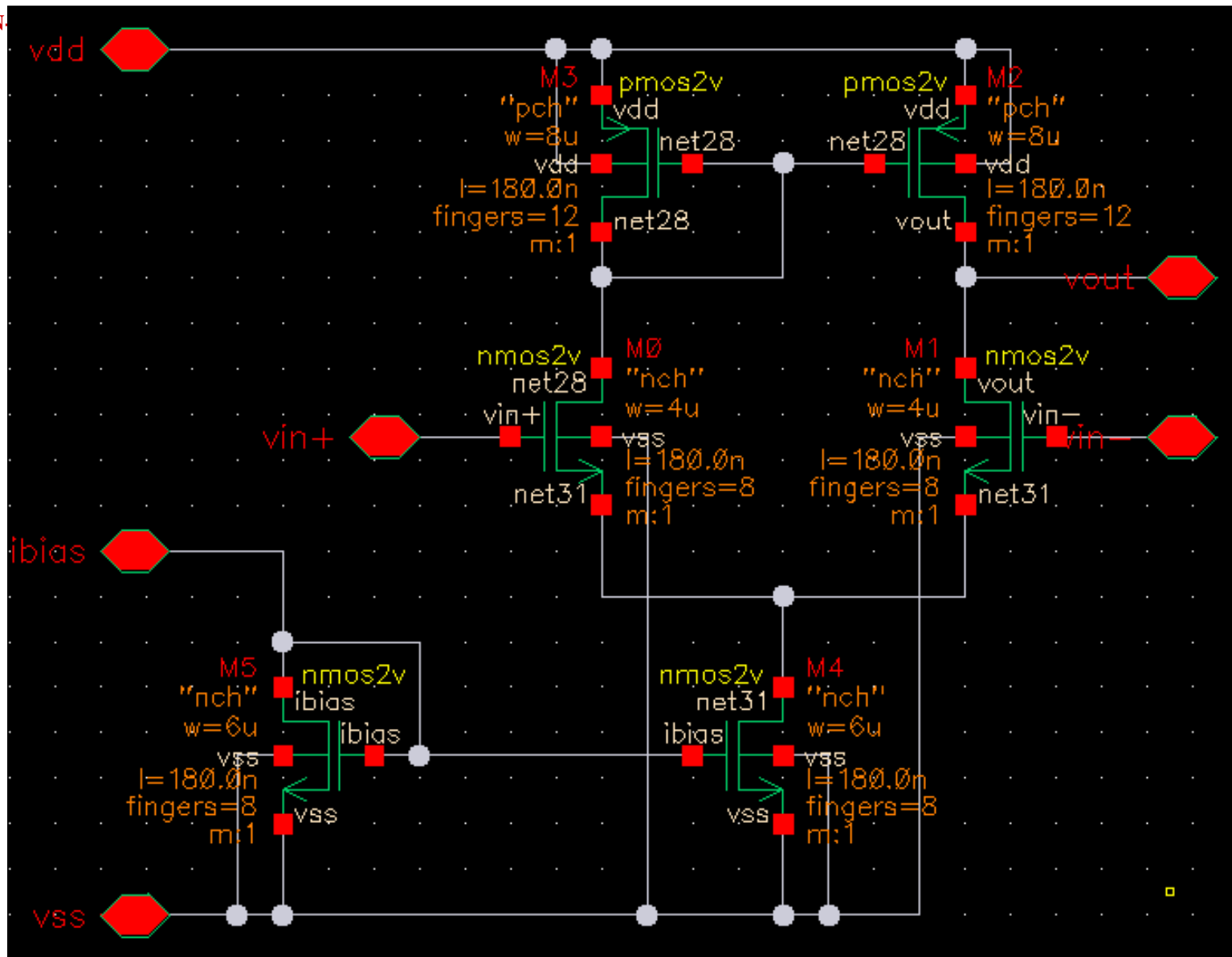


Design example (industrial quality): Simplest OTA



59


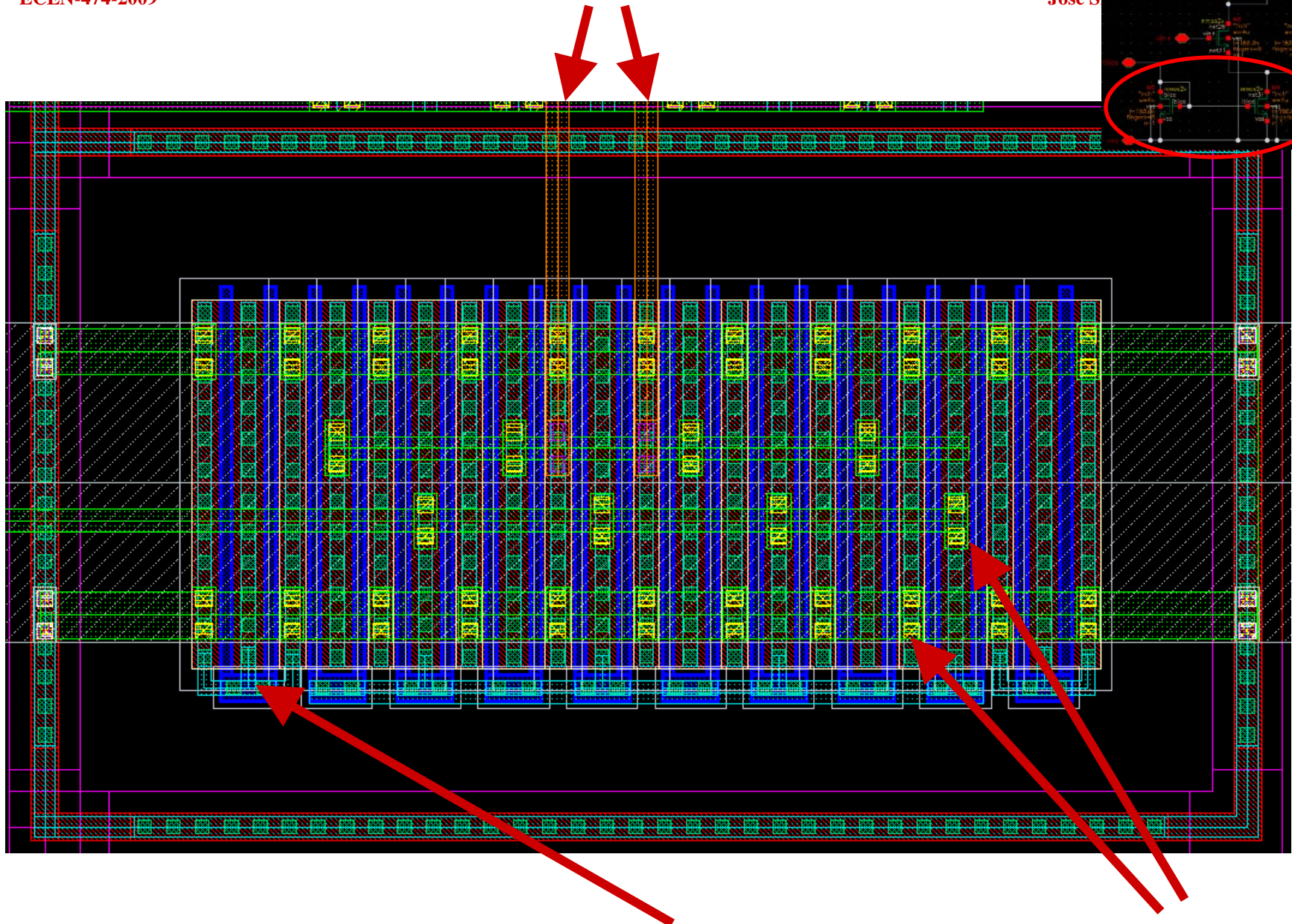



 
BIAS: you may be able to see the dummies, symmetry and S/D connections



From downstairs

Differential pair

  

  

Details on the P-type current mirrors

Q-value of Spiral Inductors in CMOS Process

Most of the following slides were taken from


Seminar by: Park, Sang Wook

TAMU, 2003

What is Q?



$$Q \equiv \omega \frac{\text{energy stored}}{\text{average power dissipated}}$$



Simple Inductor Model:

 


$$Q = \frac{\omega L_s}{R_s}$$

Integrated Spiral Inductor "Pi" Model

  


  

Equivalent Circuit & Calculation

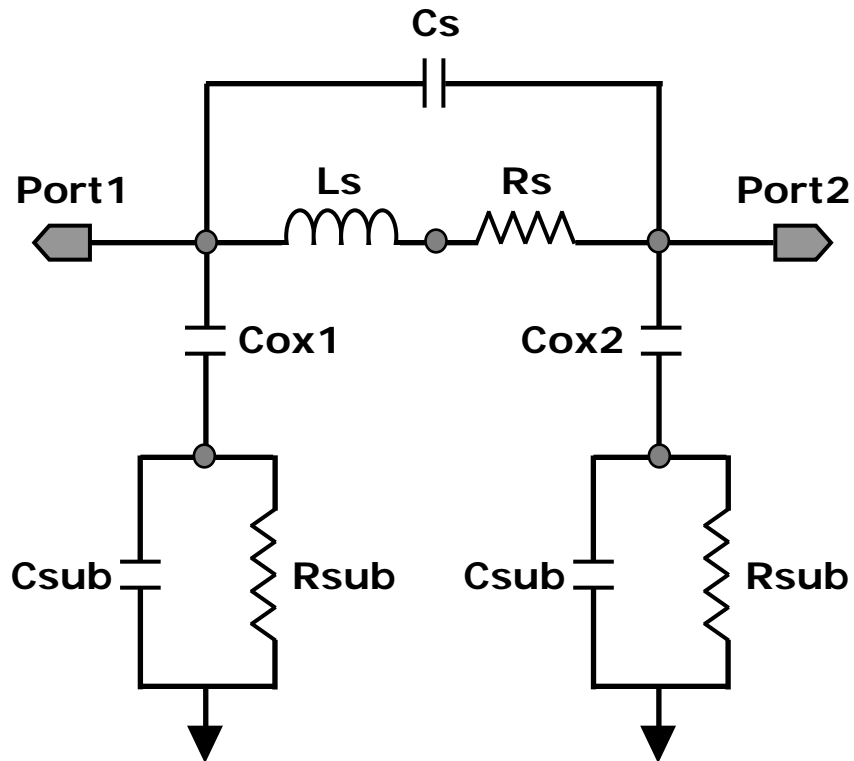


Equivalent Circuit


 


Parameter Calculation


Layout & Structure

 


Shape & Radius

  


square (R=60)

 

octagon (R=60)

 


square (R=30)

 




octagon (R=30)

"Shape" Octagon
"Radius" 60

 PGS (Patterned Ground Shield) material




PGS: Poly > Nwell

 

  
GS (Ground Shield) type

none

poly PGS(wide)

   Metal Stack

"Stack" M 5/6 > M 4/5/6

 

Chip was fabricated in 0.35um CMOS through MOSIS.

Total area 2mm×2mm.

It includes the monolithic PLL, standalone prescaler, loop filter and VCO, etc.

The chip was packaged in 48-pin TPFQ.

***Best student paper
award: Radio Frequency
Intl Conference 2003***

IEEE-JSSC-June 2003

Keliu Shu¹, Edgar Sánchez-Sinencio¹, Jose Silva-Martinez¹, and Sherif H. K. Embabi²

¹Texas A&M University

²Texas Instruments

Next Time

- Table-Based (g_m/I_D) Design Examples