

Problem 1:

Consider the waveform of some quantity $x(t)$ vs. time shown in Fig. 1 in the context of a **switch mode dc-dc power converter**. You may assume the components of the converter to be ideal.


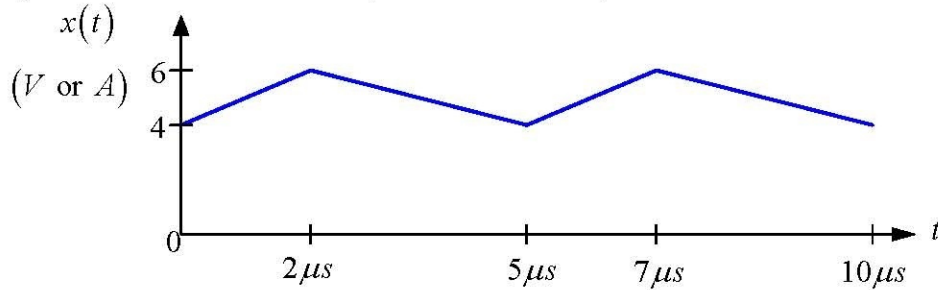


Fig. 1

- Can the waveform of Fig. 1 be that of the **voltage across a $100\ \mu\text{H}$ inductor** in steady state?
If Yes, calculate and plot the corresponding **current** through the same inductor.
If No, give a specific reason why it is not a valid waveform.
- Can the waveform of Fig. 1 be that of the **current through a $100\ \mu\text{H}$ inductor** in steady state?
If Yes, calculate and plot the corresponding **voltage** across the same inductor.
If No, give a specific reason why it is not a valid waveform.
- Can the waveform of Fig. 1 be that of the **voltage across a $100\ \mu\text{F}$ capacitor** in steady state?
If Yes, calculate and plot the corresponding **current** through the same capacitor.
If No, give a specific reason why it is not a valid waveform.
- Can the waveform of Fig. 1 be that of **current through a $100\ \mu\text{F}$ capacitor** in steady state?
If Yes, calculate and plot the corresponding **voltage** through the same capacitor.
If No, give a specific reason why it is not a valid waveform.
- Can the waveform of Fig. 1 be that of the **voltage across a MOSFET** in steady state?
If Yes, calculate and plot the corresponding **current** through the same MOSFET.
If No, give a specific reason why it is not a valid waveform.

Problem 2

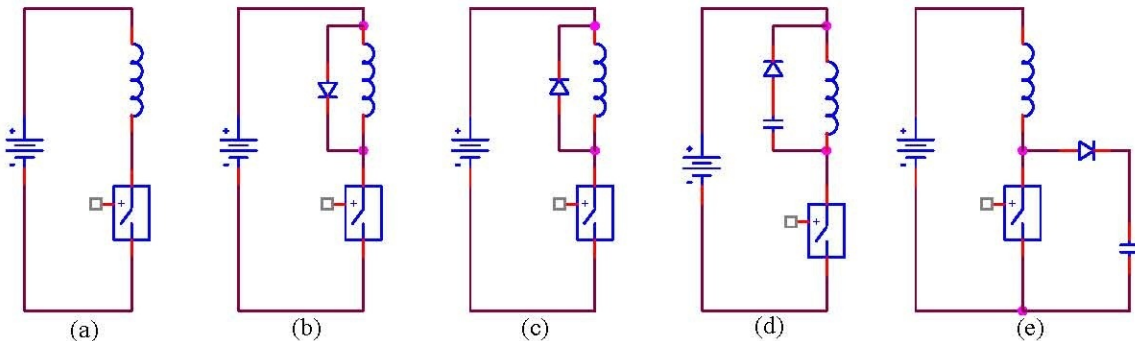


- (a) In the above circuits all the components are assumed ideal. The value of inductance is $25\ \mu H$ and the capacitance is $10\ \mu F$. The switching frequency is 100 kHz and the duty ratio is 0.5 . Which of the above circuit(s) result in valid *steady-state* operation? Justify your answers.
- (b) If the inductor is assumed to have a series resistance of $50\ \Omega$ (all other components still ideal), which of the above circuits will result in valid steady-state operation?


Problem 3

For each of the four circuits shown below, determine if steady state operation is possible. If yes, calculate V_o in steady-state (for each). If not, explain why steady state operation is not possible.


(a)

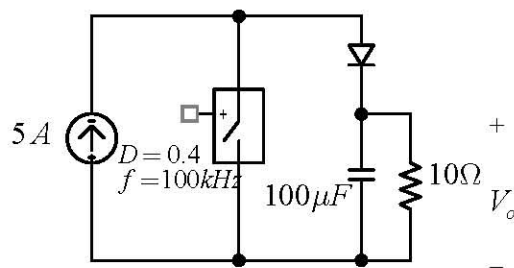


(b)

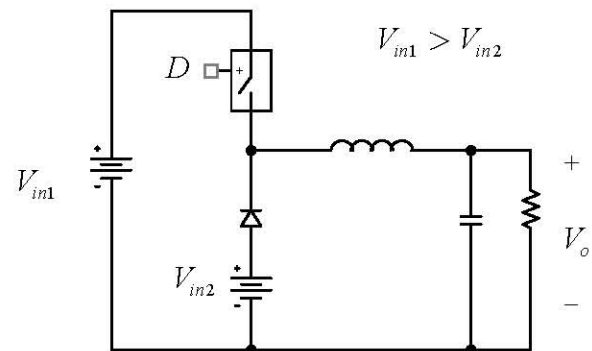

(c)

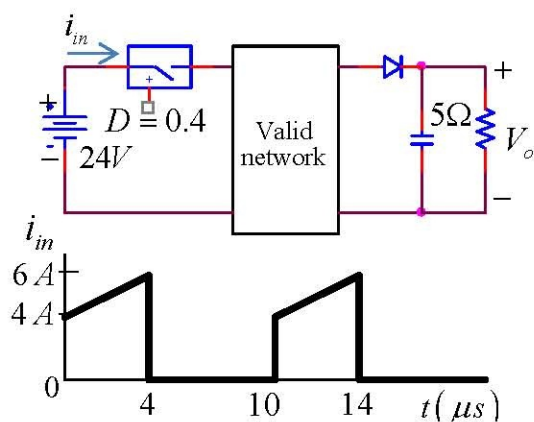

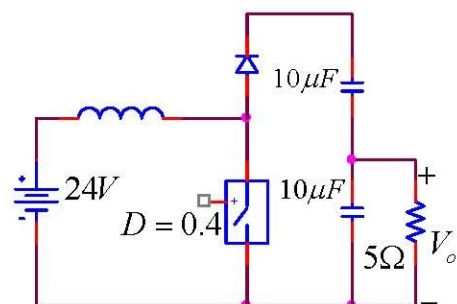(d)

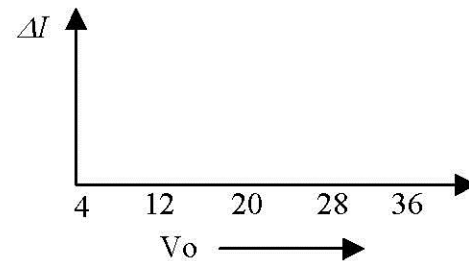
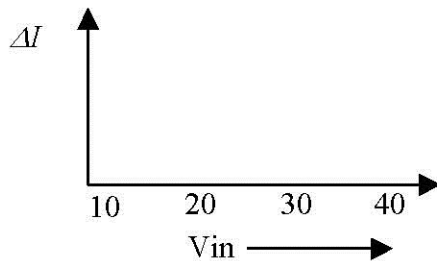


Problem 4

A buck converter has the following parameters.

$$L = 100\mu H, \quad C = 100\mu F \text{ (neglect ESR)}, \quad f_s = 100\text{ kHz}$$

- (a) If the above converter is used in an application where the input voltage, V_{in} can vary in the range of 10V to 40V dc and the output voltage is regulated at 8V, plot the peak-to-peak inductor ripple current ΔI_L as a function of V_{in} .
- (b) If the above converter is used in an application where the input voltage remains constant at 40 V dc, and the output voltage, V_o needs to be controlled in the range of 4 V to 36 V dc, plot the peak-to-peak inductor ripple current ΔI_L as a function of V_o .

**Problem 5 (25 points)**

Design a power electronic converter to meet the following specifications. Neglect ESR.

$$V_{in} = 36V - 72Vdc; \quad V_o = 28Vdc; \quad I_{o_{max}} = 10A; \quad I_{o_{min}} = 1A$$

$$f_s = 200\text{ kHz}; \quad \Delta I_L \leq 2A \text{ (pk - pk)}; \quad \Delta V_o \leq 200mV \text{ (pk - pk)}$$