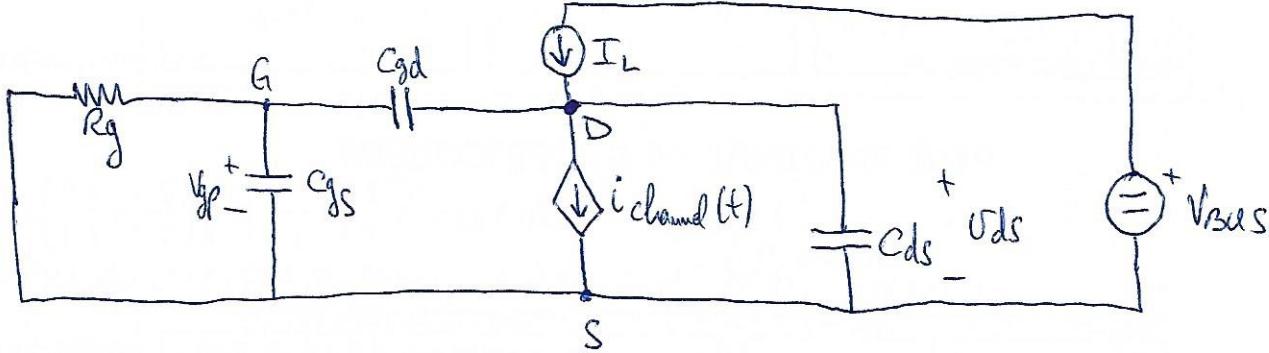


TURN OFF Miller Plateau equivalent circuit:



$$V_{gp} = V_{gd} + V_{ds} \Leftrightarrow 0 = \frac{dV_{gd}}{dt} + \frac{dV_{ds}}{dt} \Leftrightarrow \boxed{\frac{dV_{gd}}{dt} = \frac{dV_{ds}}{dt}}$$

KCL at node D: $I_L - C_{gd} \frac{dV_{gd}}{dt} = i_{\text{channel}}(t) + C_{ds} \frac{dV_{ds}}{dt} \Leftrightarrow \boxed{i_{\text{channel}}(t) = I_L - \underbrace{(C_{gd} + C_{ds})}_{C_{oss}} \frac{dV_{ds}}{dt}}$

E_{sw} during Miller Plateau for turn OFF = $\int_{t_1}^{t_2} v_{ds}(t) \cdot i_{\text{channel}}(t) dt = \int_{t_1}^{t_2} V_{ds}(t) \cdot \left[I_L - C_{oss} \frac{dV_{ds}}{dt} \right] dt =$

 $= \int_{t_1}^{t_2} V_{ds}(t) \cdot I_L dt + \int_0^{V_{bus}} -V_{ds} \cdot C_{oss} \cdot dV_{ds} = \underbrace{\int_{t_1}^{t_2} v_{ds}(t) \cdot I_L dt}_{\text{Overlap between drain voltage and } I_L} - \underbrace{\int_0^{V_{bus}} V_{ds}(t) \cdot C_{oss} dV_{ds}}_{E_{oss} @ V_{bus}}$

$\cancel{I_L \neq \text{channel current}}$

$$\Rightarrow E_{\text{sw}} \text{ Miller Plateau for turn OFF} = \underbrace{\int_{t_1}^{t_2} v_{ds}(t) \cdot I_L dt}_{\frac{1}{2} \cdot V_{bus} \cdot I_L \cdot (t_2 - t_1)} - E_{oss} @ V_{bus}$$

Assuming $V_{ds}(t)$ rises linearly and I_L is constant